

In class problem (Feb 21st 2013)

Problem 5.26

The transistor shown in Figure P5.26 has $\beta = 120$. Determine I_C and V_{EC} . Plot the load line and the Q -point.

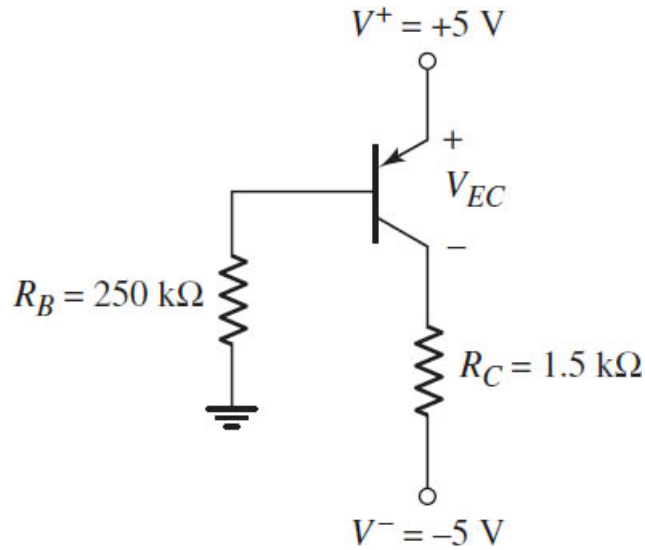


Figure P5.26