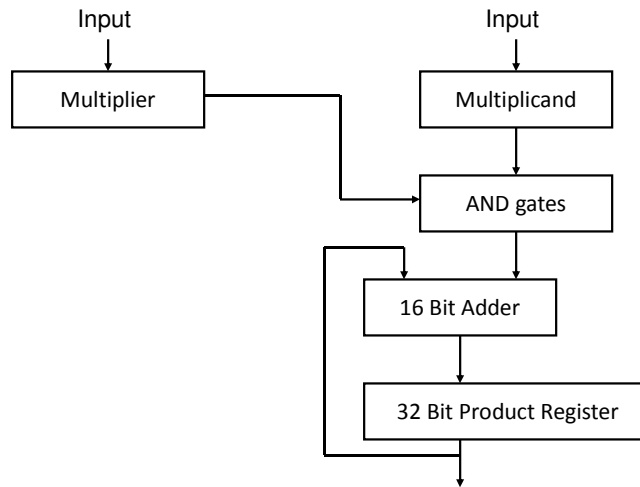


## Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)



## Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)

- Step 1:
  - Clear Product Register
  - Clear Counter
  - Load Multiplicand
  - Load Multiplier
- Step 2: (repeat 16 times)
  - Increment Counter
  - Load Product Register
  - Shift Multiplier
- Step 3:
  - Done

## VHDL: Use Processes, Buses to Implement Registers, Logic

- Process construct for registers: clear, clock activities
- Test conditions in system (both data path and control) with 'if' constructs
- Implement logic as needed in either process or signal assignment statements

## Port in Entity

```
entity MULTIPLIER is
  port (
    MIER_VAL : in  STD_LOGIC_VECTOR ( 15 downto 0 );
    MCND_VAL : in  STD_LOGIC_VECTOR ( 15 downto 0 );
    PROD_VAL : out STD_LOGIC_VECTOR ( 31 downto 0 );
    SYS_CLK  : in  STD_LOGIC;
    SYS_RST  : in  STD_LOGIC;
    GO       : in  STD_LOGIC;
    DONE     : out STD_LOGIC
  );
end entity MULTIPLIER;
```

## Multiplicand is Simple Register

```

in declaration area:

    signal MCAND : STD_LOGIC_VECTOR ( 15 downto 0 );

in work area:

process ( SYS_CLK, SYS_RST ) is
begin
    if SYS_RST = '1' then
        MCAND <= ( others => '0' );
    elsif RISING_EDGE ( SYS_CLK ) then
        if PSR = S1 then
            MCAND <= MCND_VAL;
        end if;
    end if;
end process;

```

## Multiplier is Shift Register with Parallel Load

```

in declaration area:
    signal MIER : STD_LOGIC_VECTOR ( 15 downto 0 );
in work area:

process ( SYS_CLK, SYS_RST ) is
begin
    if SYS_RST = '1' then
        MIER <= ( others => '0' );
    elsif RISING_EDGE ( SYS_CLK ) then
        if PSR = S1 then
            MIER <= MIER_VAL;
        elsif PSR = S2 then
            MIER <= '0' & MIER ( 15 downto 1 );
        end if;
    end if;
end process;

```

## AND Function, Adder as Signal Assignment Statements

in declaration area:

```
signal AND_OUT : STD_LOGIC_VECTOR ( 15 downto 0 );
signal ADDER   : STD_LOGIC_VECTOR ( 16 downto 0 );
```

in work area;

```
AND_OUT <= MCAND when MIER(0) = '1' else
           ( others => '0' );
```

```
ADDER <= ( '0' & PRODUCT ( 31 downto 16 ) ) +
          ( '0' & AND_OUT                               );
```

## Product is Simple Register


in declaration area:

```
signal PRODUCT : STD_LOGIC_VECTOR ( 31 downto 0 );
```

in work area:

```
process ( SYS_CLK, SYS_RST ) is
begin
  if SYS_RST = '1' then
    PRODUCT <= ( others => '0' );
  elsif RISING_EDGE ( SYS_CLK ) then
    if PSR = S1 then
      PRODUCT <= ( others => '0' );
    elsif PSR = S2 then
      PRODUCT <= ADDER & PRODUCT ( 15 downto 1 );
    end if;
  end if;
end process;
```

## State Machine Implements Sequence

 

## Define States as Enumeration Type

in declaration area:

```
type PSR_TYPE is ( IDLE, S1, S2, S3 );  
signal PSR : PSR_TYPE;
```

## Implement State Machine as Process

```

process ( SYS_CLK, SYS_RST ) is
begin
    if SYS_RST = '1' then
        PSR <= IDLE;
    elsif RISING_EDGE ( SYS_CLK ) then
        case PSR is
            when IDLE =>
                if GO = '1' then PSR <= S1; end if;
            when S1 => PSR <= S2;
            when S2 => if COUNT = 15 then PSR <= S3; end if;
            when S3 => if GO = '0' then PSR <= IDLE; end if;
        end case;
    end if;
end process;

```

## Implement Counter as Process


```

in declaration area:
    signal COUNT : STD_LOGIC_VECTOR ( 4 downto 0 );
in work area:

process ( SYS_CLK, SYS_RST ) is
begin
    if SYS_RST = '1' then
        COUNT <= ( others => '0' );
    elsif RISING_EDGE ( SYS_CLK ) then
        if PSR = S1 then
            COUNT <= ( others => '0' );
        elsif PSR = S2 then
            COUNT <= COUNT + 1 ;
        end if;
    end if;
end process;

```
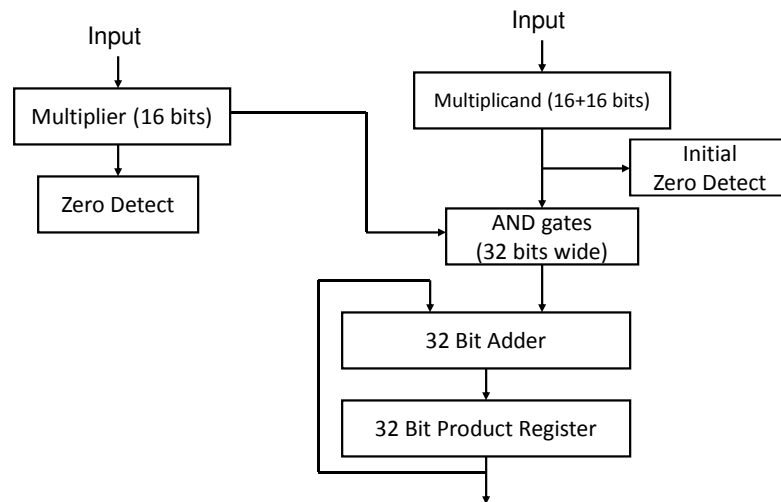
## Implement the Modified Gradeschool Multiplication Algorithm



## Multiplication – Modified Gradeschool Algorithm for 16 Bits (32 Bit Result)

Step 1:

Clear Product Register

Load Multiplicand

Load Multiplier

Step 2:

If MIER = 0 OR MCAND = 0, done

Step 3:

Load Product Register


Shift Multiplier and Multiplicand

Step 4:


If MIER = 0, then Done

else Go to Step 3

## State Machine Implements Sequence

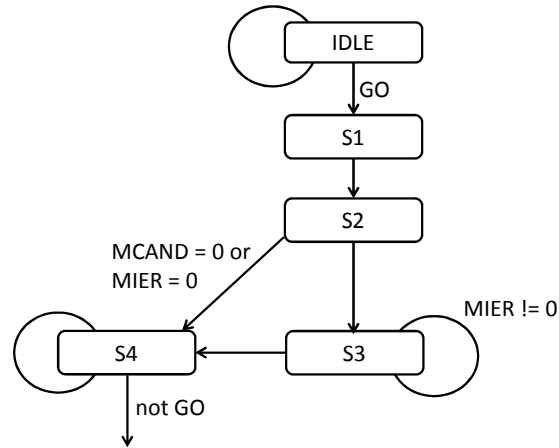

## Timing for Multiply

 



## Multiplicand Is Load/Shift Register

```

in declaration area:
    signal MCAND : STD_LOGIC_VECTOR ( 31 downto 0 );
in work area:

process ( SYS_CLK, SYS_RST ) is
begin
    if SYS_RST = '1' then
        MCAND <= ( others => '0' );
    elsif RISING_EDGE ( SYS_CLK ) then
        if PSR = S1 then
            MCAND <= ZEROS & MCND_VAL;
        elsif PSR = S3 then
            MCND <= MCND ( 30 downto 0 ) & '0';
        end if;
    end if;
end process;

```

## Multiplier Is Again Shift Register with Parallel Load

```

in declaration area:
    signal MIER : STD_LOGIC_VECTOR ( 15 downto 0 );
in work area:

process ( SYS_CLK, SYS_RST ) is
begin
    if SYS_RST = '1' then
        MIER <= ( others => '0' );
    elsif RISING_EDGE ( SYS_CLK ) then
        if PSR = S1 then
            MIER <= MIER_VAL;
        elsif PSR = S3 then
            MIER <= '0' & MIER ( 15 downto 1 );
        end if;
    end if;
end process;

```

## AND Function, Adder as before - Signal Assignment Statements

```

in declaration area:

    signal AND_OUT : STD_LOGIC_VECTOR ( 31 downto 0 );
    signal ADDER   : STD_LOGIC_VECTOR ( 31 downto 0 );

in work area;

    AND_OUT <= MCAND when MIER(0) = '1' else
                ( others => '0' );

    ADDER <=  PRODUCT + AND_OUT;

```

## Product Is Again Simple Register

```

in declaration area:
    signal PRODUCT : STD_LOGIC_VECTOR ( 31 downto 0 );
in work area:

process ( SYS_CLK, SYS_RST ) is
begin
    if SYS_RST = '1' then
        PRODUCT <= ( others => '0' );
    elsif RISING_EDGE ( SYS_CLK ) then
        if PSR = S1 then
            PRODUCT <= ( others => '0' );
        elsif PSR = S3 then
            PRODUCT <= ADDER;
        end if;
    end if;
end process;

```

## Testing for Zero: Conditional Signal Assignment Statements

```
in declaration area:
```

```
signal MCND_ZRO : STD_LOGIC;  
signal MIER_ZRO : STD_LOGIC;
```

```
in work area;
```

```
MIER_ZRO <= '1' when MIER = X"0000" else '0';
```

```
MCND_ZRO <= '1' when MCAND ( 15 downto 0 ) =  
                           X"0000" else '0';
```