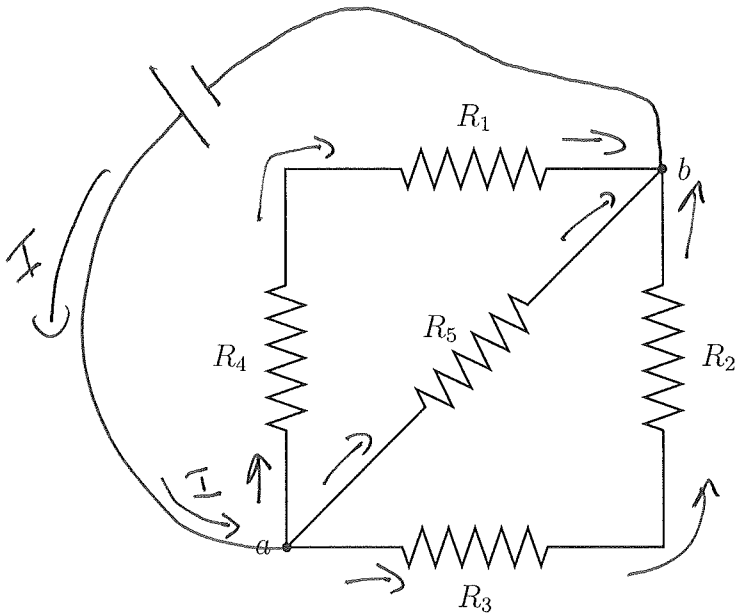




PHYSICS 161 TEST 4



$R_1 = 50 \Omega$
$R_2 = 150 \Omega$
$R_3 = 300 \Omega$
$R_4 = 200 \Omega$
$R_5 = 350 \Omega$

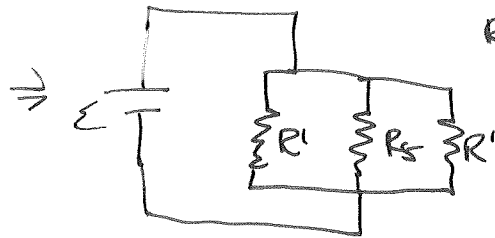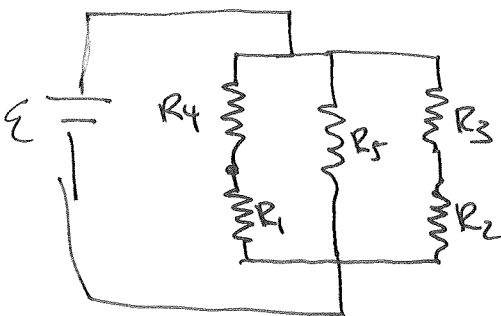- (a) If a battery is connected to the points a and b , what is the equivalent resistance for this circuit? (5pts)

With this battery connection R_1 & R_4 are in series, R_2 & R_3 in series, R_5 in parallel with $1/4$ and $2/3$ combo, i.e.,



$$R' = \frac{200}{50} \Omega + 50 \Omega = 250 \Omega$$

$$R'' = 300 \Omega + 150 = 450 \Omega$$

R', R_5, R'' in parallel

$$\Rightarrow \frac{1}{R_{eq}} = \frac{1}{250 \Omega} + \frac{1}{350 \Omega} + \frac{1}{450 \Omega}$$

$$\Rightarrow R_{eq} = 110 \Omega$$


- (b) Assuming the battery's emf is 10 V , what is the power supplied by the battery? (2pts)

$P = I \mathcal{E}$ From \mathcal{E} R_{eq}



$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{10 \text{ V}}{110 \Omega} = 0.0909 \text{ A}$$

$$\therefore P = (0.0909 \text{ A})(10 \text{ V}) = \underline{\underline{0.908 \text{ Watt}}}$$

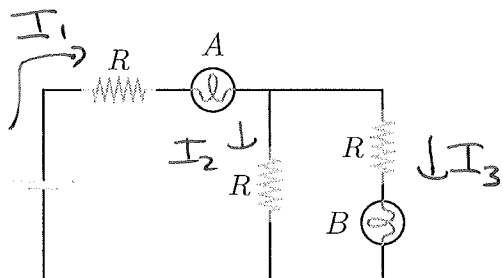- (c) In the circuit below, bulbs A and B have identical resistances. Initially both are glowing. If bulb B is removed from its socket, what happens to bulb A ? Does it get brighter, dimmer, stay the same, or go out? Explain. **Hint:** Assume that the current flowing through a light bulb determines its brightness. Also, removing a light bulb prevents current from flowing through that part of the circuit. (3pts)



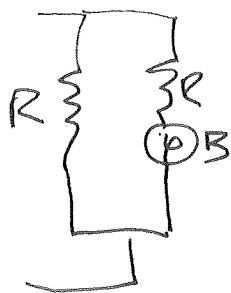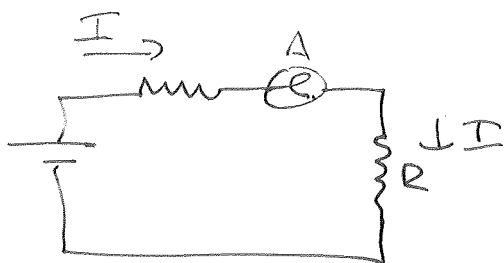At First there are 3 Current values.
 Removing B stops I_3
 And now everything is in series
 with Current I



These guys were in Parallel before \Rightarrow Their equivalent Resistance had to be smaller than R .

So removing B MADE the Resistance bigger

$\Rightarrow I$ must be less than I_1

$\Rightarrow A$ must get DIMMER when B is removed.