

3. (20 points) Determine the width of the depletion region and the junction capacitance of a PN^+ junction when it is connected to a 1V reverse bias potential. The doping concentration of P and N+ are $N_A=10^{15} \text{ cm}^{-3}$ and $N_D=10^{19} \text{ cm}^{-3}$, respectively, and the junction area is $0.25\mu\text{m} \times 0.25\mu\text{m}$. The relative permittivity of silicon is 11.9, $V_{th}=25.9 \text{ mV}$ at 300°K, $n_i=1.45 \times 10^{10} \text{ cm}^{-3}$ at 300°K, and $\epsilon_0=8.854 \times 10^{-14} \text{ F/cm}$.

Hint: You may use the following equations:

$$V_{bi} = V_{th} \ln \left(\frac{N_A \cdot N_D}{n_i^2} \right) \quad W = \sqrt{\frac{2\epsilon_{si}}{q} \frac{N_A + N_D}{N_A \cdot N_D} (V_{bi} - V_D)}$$

$$V_{bi} = 25.9 \text{ mV} \times \ln \left(\frac{10^{15} \times 10^{19}}{(1.45 \times 10^{10})^2} \right) \Rightarrow V_{bi} = 0.815 \text{ V}$$

$$W = \sqrt{\frac{2 \times 11.9 \times 8.854 \times 10^{-14}}{1.602 \times 10^{-19}} \frac{10^{19} + 10^{15}}{10^{19} \times 10^{15}} (0.815 - (-1))} = 1.545 \times 10^{-4} \text{ cm}$$


$$\Rightarrow \underline{W = 1.545 \text{ } \mu\text{m}}$$

$$C = \frac{\epsilon A}{d} = \frac{\epsilon_{si} A}{W} = \frac{11.9 \times 8.854 \times 10^{-14} \times (0.25 \times 10^{-4})^2}{1.545 \times 10^{-4}} \Rightarrow \underline{C = 4.26 \times 10^{-18} \text{ F}}$$

6. (20 points) The following circuit is called "current mirror". Assume that the physical parameters of M_2 is the same as M_1 , except that M_2 is N times larger than M_1 (i.e. $(W/L)_2 = N \cdot (W/L)_1$).
- Determine the region of operation for M_1 .
 - Based on your answer to part (a), find V_x as a function of K'_n , I_{Ref} , V_T , $(W/L)_1$.
 - Assume that R_L is chosen such that M_2 is in saturation region. Find I_L as a function of V_x , then use your V_x equation from part (b) to simplify the result.
 - Determine the range of R_L that guarantees saturation region for M_2 .

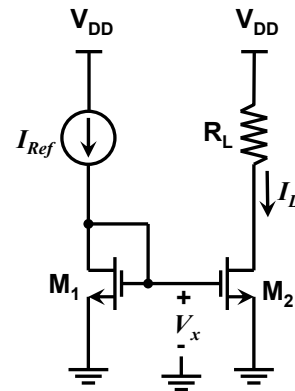a) M_1 in Saturation

$$\begin{aligned}
 b) \quad I_{D5} &= \frac{K'_n}{2} \left(\frac{W}{L}\right)_1 (V_{G5} - V_T)^2 \\
 &\Rightarrow I_{Ref} = \frac{K'_n}{2} \left(\frac{W}{L}\right)_1 (V_x - V_T)^2 \\
 &\Rightarrow V_x = V_T + \sqrt{\frac{2 I_{Ref}}{K'_n \left(\frac{W}{L}\right)_1}}
 \end{aligned}$$



$$\begin{aligned}
 c) \quad I_{D5} &= \frac{K'_n}{2} \left(\frac{W}{L}\right)_2 (V_{G5} - V_T)^2 \\
 &\Rightarrow I_L = \frac{K'_n}{2} \left(\frac{W}{L}\right)_2 (V_x - V_T)^2 = \frac{K'_n}{2} \left(\frac{W}{L}\right)_2 \left[V_x + \sqrt{\frac{2 I_{Ref}}{K'_n \left(\frac{W}{L}\right)_1}} - V_x \right]^2 \\
 &\Rightarrow I_L = \frac{K'_n}{2} \left(\frac{W}{L}\right)_2 * \frac{2 I_{Ref}}{K'_n \left(\frac{W}{L}\right)_1} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1} \cdot I_{Ref} = N I_{Ref} \\
 &\Rightarrow \underline{I_L = N I_{Ref}}
 \end{aligned}$$

$$\begin{aligned}
 d) \quad \text{In the worst case: } V_{DS2} &= V_{GS2} - V_T \Rightarrow V_{DD} - I_L R_L = V_x - V_T \\
 &\Rightarrow R_{L, \max} = \frac{V_{DD} - V_x + V_T}{I_L} = \frac{V_{DD} - V_x + V_T}{N I_{Ref}} \\
 &\Rightarrow \underline{R_{L, \max} = \frac{1}{N I_{Ref}} \cdot \left[V_{DD} - \sqrt{\frac{2 I_{Ref}}{K'_n \left(\frac{W}{L}\right)_1}} \right]}
 \end{aligned}$$