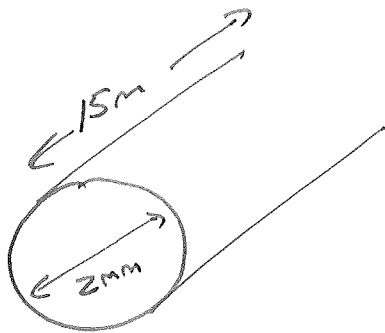


Physics 161, Hw #4

#1



$$R = 0.5 \Omega$$

Circular cross section of Diameter

$$2\text{mm} \Rightarrow \text{radius } r = 1\text{mm} = 1 \times 10^{-3}\text{m}$$

$$A = \pi r^2 = \pi (1 \times 10^{-3}\text{m})^2 = \pi \times 10^{-6}\text{m}^2 = 3.14 \times 10^{-6}\text{m}^2$$

a) WHAT is Resistivity?

$$R = \frac{\rho L}{A} \Rightarrow \rho = \frac{RA}{L} = \frac{(0.5 \Omega)(\pi \times 10^{-6}\text{m}^2)}{15\text{m}} \Rightarrow \boxed{\rho = 1.05 \times 10^{-7} \Omega \cdot \text{m}}$$

b) IF  $E = 1.75\text{V/m}$ , what is total current?

$$E = \rho J \Rightarrow J = \frac{E}{\rho} = \frac{1.75\text{V/m}}{1.05 \times 10^{-7} \Omega \cdot \text{m}} = 1.67 \times 10^7 \text{A/m}^2$$


$$J = \frac{I}{A} \Rightarrow I = JA = (1.67 \times 10^7 \text{A/m}^2)(\pi \times 10^{-6}\text{m}^2) \Rightarrow \boxed{I = 52.5\text{A}}$$

c) IF  $n = 9.5 \times 10^{28}$  free electrons/m<sup>3</sup>, Find Drift Velocity

$$J = nev_d \Rightarrow v_d = \frac{J}{ne} = \frac{1.67 \times 10^7 \text{A/m}^2}{(9.5 \times 10^{28}/\text{m}^3)(1.6 \times 10^{-19}\text{C})}$$

$$\Rightarrow \boxed{v_d = 0.0011 \text{m/s} = 1.1 \text{mm/s}}$$

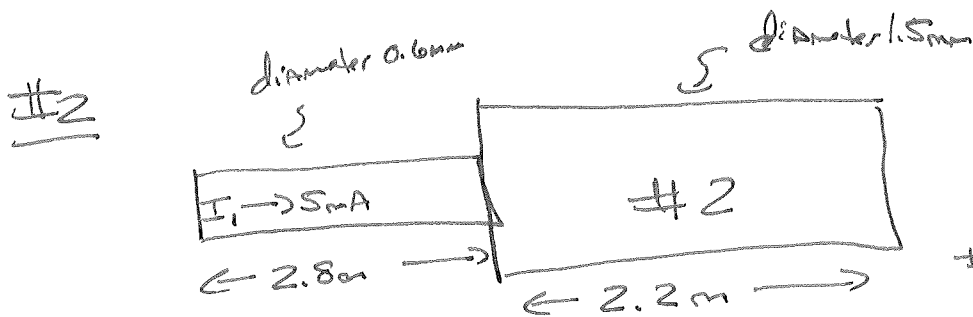Even for very large current, drift velocity is small.



Let first section be #1  $\Rightarrow$   
 $l_1 = 2.8 \text{ m}, d_1 = 0.6 \text{ mm}, I_1 = 5 \text{ mA}$

#2  $\Rightarrow l_2 = 2.2 \text{ m}, d_2 = 1.5 \text{ mm}$

a) What is  $I_2$ ? Every charge that leaves #1 must enter #2 (or vice versa)  $\Rightarrow$  #1 AND #2 ARE CONNECTED IN SERIES  $\therefore \boxed{I_2 = 5 \text{ mA}}$

b) What is  $E_1$ ?  $E = \rho J$ , Copper at  $20^\circ\text{C} \Rightarrow \rho = 1.72 \times 10^{-8} \Omega \cdot \text{m}$

$$\therefore E_1 = \rho J_1 = \rho \left( \frac{I_1}{A_1} \right) \quad A_1 = \pi r_1^2 = \pi \left( \frac{0.6}{2} \times 10^{-3} \text{ m} \right)^2 = \pi (0.3 \times 10^{-3} \text{ m})^2$$


radius!

$$\therefore E_1 = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(5 \times 10^{-3} \text{ A})}{\pi (0.3 \times 10^{-3} \text{ m})^2} \Rightarrow \boxed{E_1 = 3.04 \times 10^{-4} \text{ V/m}}$$

c) What is  $E_2$ ?  $E_2 = \rho \frac{I_2}{A_2} \quad A_2 = \pi r_2^2 = \pi \left( \frac{1.5}{2} \times 10^{-3} \text{ m} \right)^2 = \pi (0.75 \times 10^{-3} \text{ m})^2$

$$\therefore E_2 = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(5 \times 10^{-3} \text{ A})}{\pi (0.75 \times 10^{-3} \text{ m})^2} \Rightarrow \boxed{E_2 = 4.87 \times 10^{-5} \text{ V/m}}$$

Definitely UNEQUAL Electric Fields

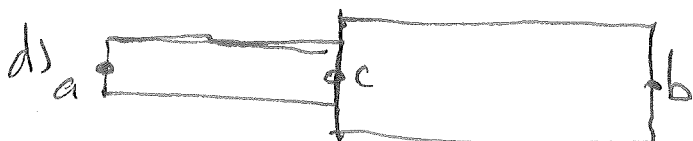

$V_{ab} = ?$

Let connection point be "c"

$$V_{ac} = V_a - V_c, \quad V_{cb} = V_c - V_b, \quad V_{ab} = V_a - V_b$$


$$\Rightarrow \boxed{V_{ab} = V_{ac} + V_{cb}}$$

Assuming uniform  $E_1$  &  $E_2 \Rightarrow V_{ac} = E_1 l_1, \quad V_{cb} = E_2 l_2$

$$\therefore V_{ac} = (3.04 \times 10^{-4} \text{ V/m})(2.8 \text{ m}) = 8.512 \times 10^{-4} \text{ V}, \quad V_{cb} = (4.87 \times 10^{-5} \text{ V/m})(2.2 \text{ m}) = 1.0714 \times 10^{-4} \text{ V}$$

$$\therefore \boxed{V_{ab} = 9.58 \times 10^{-4} \text{ V} = 0.958 \text{ mV}}$$

13

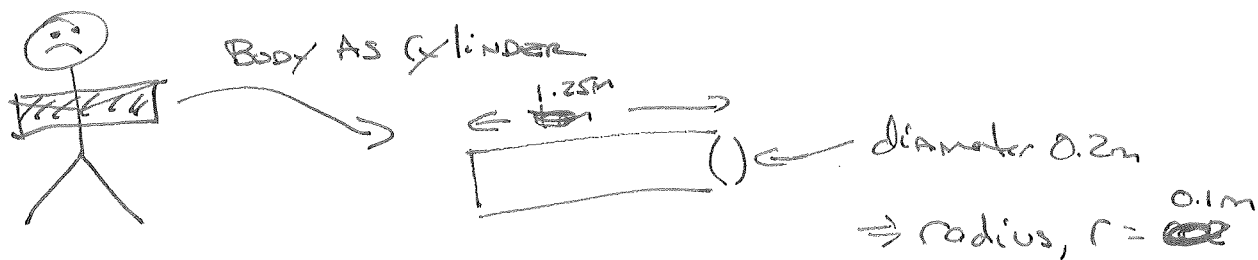

a) What is Resistance?

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2}$$

↑  
Cross-section  
Area  $\Rightarrow \pi r^2$

$$\therefore R = \frac{(52 \cdot m)(1.25m)}{\pi (0.1m)^2} \Rightarrow \boxed{R = 199\Omega \approx 200\Omega}$$

only one sig fig for  
such a calculation

b)  $V = ?$  to produce  $I = 100mA = 0.1A$

$$V = IR = (0.1A)(200\Omega) = 20V$$


← much less than the  
120V most appliances run  
on.

c) Power?

$$\boxed{P = IV = (0.1A)(20V) = 2 \text{ watt}}$$

↑  
Not much.

thy

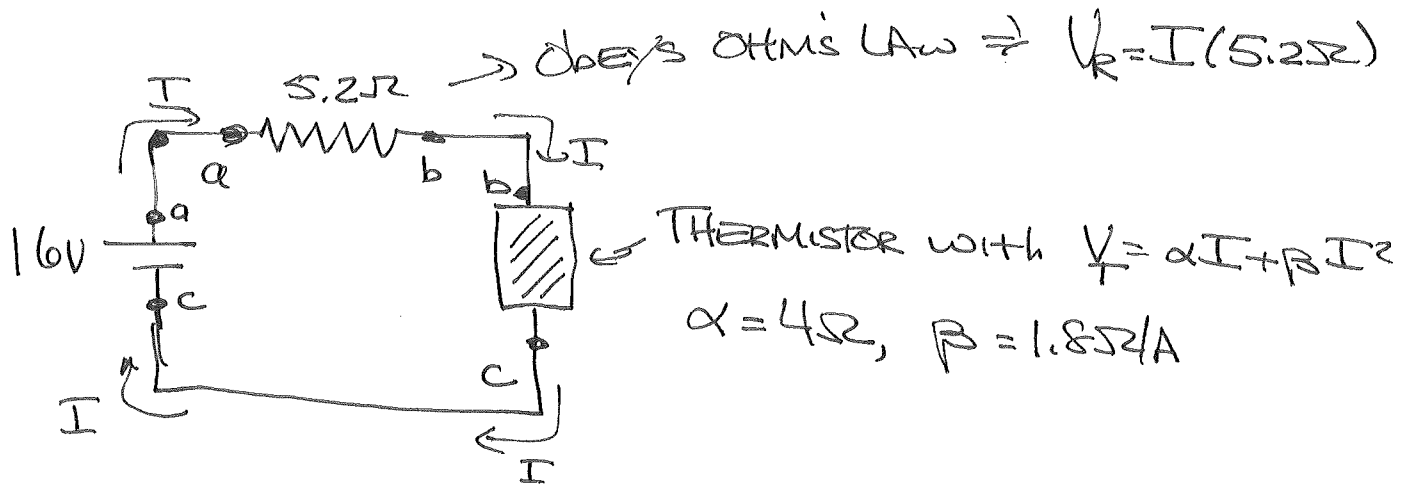

Label points (a), (b), (c) As Above

$$\Rightarrow V_{ac} = V_a - V_c = 16V$$

$$V_{ab} = V_a - V_b = V_R$$

$$V_{bc} = V_b - V_c = V_T$$

$$\Rightarrow V_{ab} + V_{bc} = V_{ac}$$

$$\Rightarrow V_R + V_T = 16V$$

$$\therefore I(5.2\Omega) + (4\Omega)I + (1.8\Omega/A)I^2 = 16V$$


$$\Rightarrow (1.8\Omega/A)I^2 + (9.2\Omega)I - 16V = 0 \leftarrow \text{QUADRATIC EQN.}$$

$$\Rightarrow I = \frac{-9.2\Omega \pm \sqrt{(9.2\Omega)^2 - 4(1.8\Omega/A)(-16V)}}{2(1.8\Omega/A)} = \frac{-9.2\Omega \pm \sqrt{199.84\Omega^2}}{3.6\Omega/A}$$

$$\Rightarrow I = 1.37A \text{ or } -6.48A \Rightarrow \boxed{I = 1.37A}$$

$\nearrow$   
No

#5

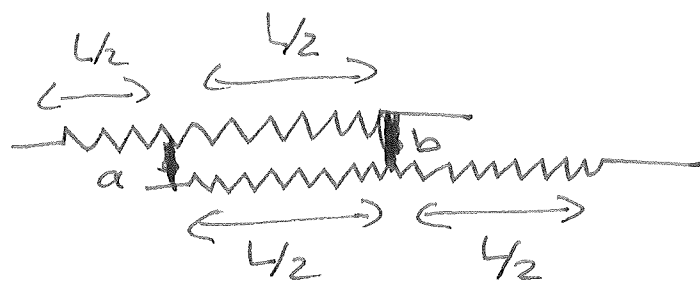


SOLDERED  $\Rightarrow$  Connected by  
Metal = EQUIPOTENTIAL  
SURFACE


Label a & b as shown  $\Rightarrow$  HALF of top Resistor AND HALF  
OF bottom Resistor have SAME  $V_{ab} \Rightarrow$  in Parallel with EACH  
OTHER

$$R = \frac{\rho L}{A} \Rightarrow \frac{1}{2}L \text{ of a } 5\Omega \text{ Resistor has } R = 2.5\Omega$$

So we basically have this:

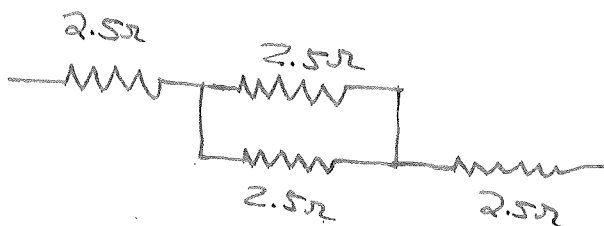


OR AS we'd more typically draw it:

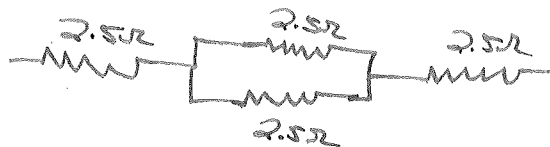

For Parallel Resistors  $R' = \frac{(2.5\Omega)(2.5\Omega)}{(2.5\Omega + 2.5\Omega)} = \frac{(2.5\Omega)(2.5\Omega)}{5\Omega} = \frac{1}{2}(2.5\Omega) = 1.25\Omega$

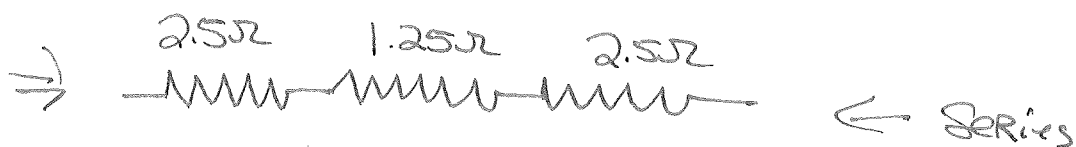two EQUAL Resistor in  
parallel have  $R' = R/2$




$$\text{So } R_{EQ} = 2.5\Omega + 1.25\Omega + 2.5\Omega = 6.25\Omega$$

126  
~~126~~

IF OHMMETER CONNECTED TO a+b,

WHAT WILL IT READ?


OHMMETER APPLIES VOLTAGE  $\Rightarrow$

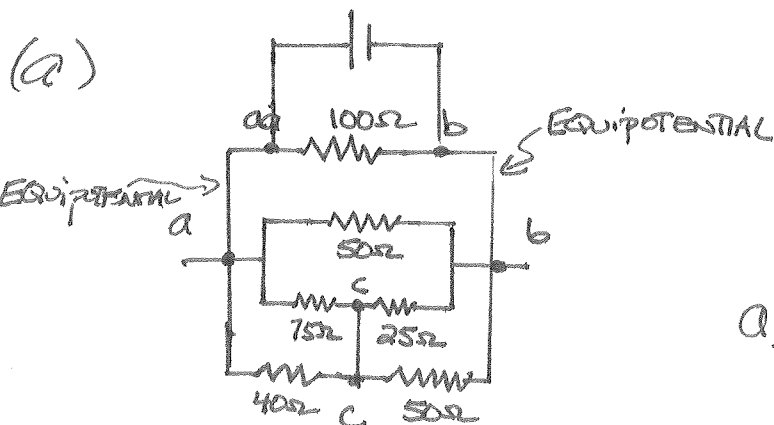


a, b  $\Rightarrow$  100Ω, UPPER 50Ω, AND  
REST IN PARALLEL.

a, c  $\Rightarrow$  75Ω, 40Ω IN PARALLEL

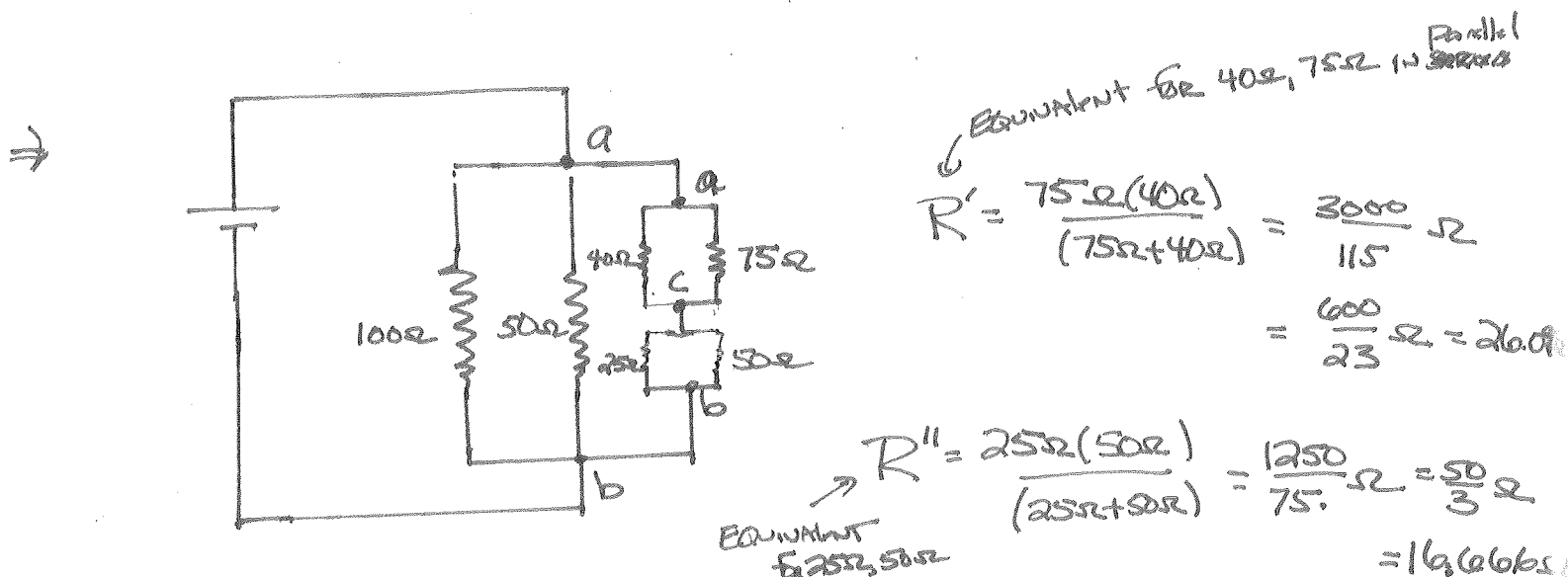b, c  $\Rightarrow$  25Ω, 50Ω IN PARALLEL



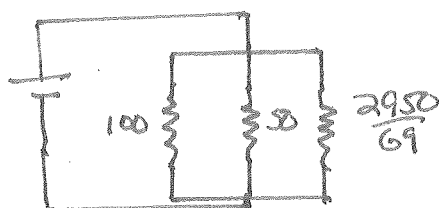
$$R' + R'' = \frac{2950}{69} = 22.753 \leftarrow R', R'' \text{ IN SERIES}$$



$$\frac{1}{R_{EQ}} = \frac{1}{100} + \frac{1}{50} + \frac{1}{2950/69} \Rightarrow R_{EQ} = 18.73\Omega$$


#7

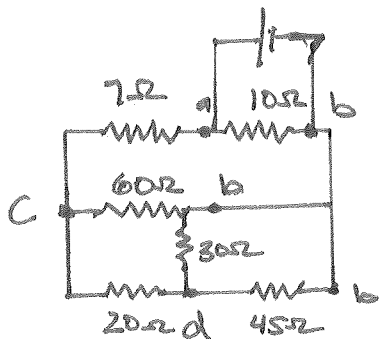

$ab \Rightarrow 10\Omega$  in parallel to everything else  
 $ac \Rightarrow 7\Omega$  in series with  $60, 20, 30, 45$  combo  
 $cd \Rightarrow 60\Omega$  in parallel to  $20, 30, 45\Omega$  combination


$db \Rightarrow 30, 45$  in parallel  
 $cd \Rightarrow 20$  in series with  $30, 45$

$\Rightarrow$

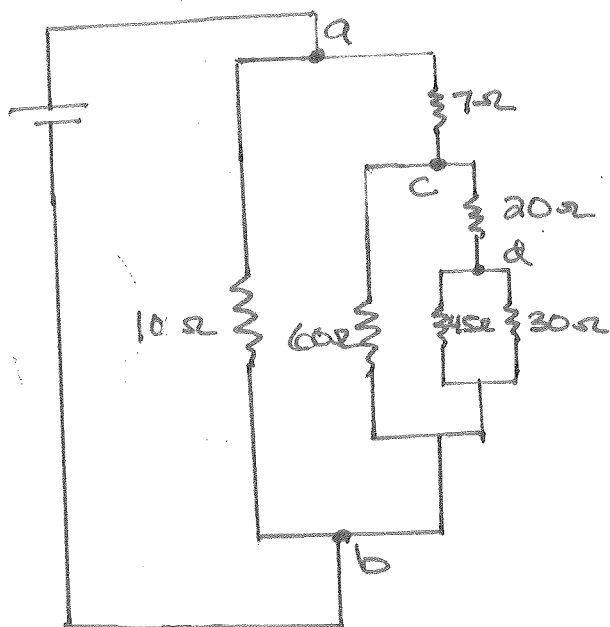

$$\begin{aligned}
 R' &= 30\Omega, 45\Omega \text{ in parallel} \\
 \Rightarrow R' &= \frac{30\Omega(45\Omega)}{30\Omega + 45\Omega} = 18\Omega \\
 20\Omega + 18\Omega &= 38\Omega
 \end{aligned}$$


$\Rightarrow$

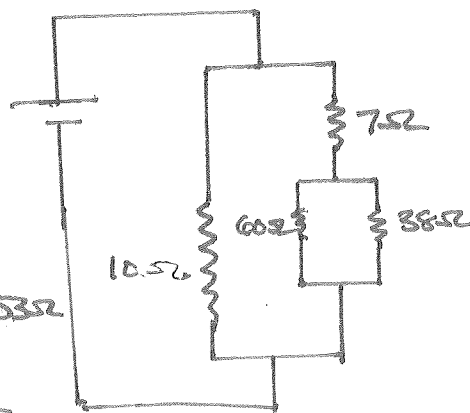

$$\begin{aligned}
 60, 38 \text{ in parallel} \Rightarrow R'' &= \frac{60\Omega(38\Omega)}{98\Omega} = \frac{1140}{98}\Omega \\
 &= 23.2653\Omega
 \end{aligned}$$
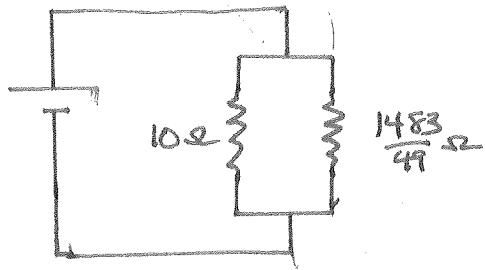
$$7 \text{ in series} \Rightarrow 7 + \frac{1140}{98} = \frac{1483}{49} = 30.2653\Omega$$







$$R_{EQ} = \frac{10\Omega \left( \frac{1483}{49}\Omega \right)}{\left[ 10\Omega + \frac{1483}{49}\Omega \right]}$$

$$\Rightarrow R_{EQ} = 7.5165 = 7.52\Omega$$

#8

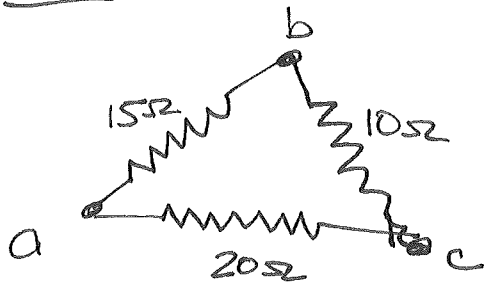


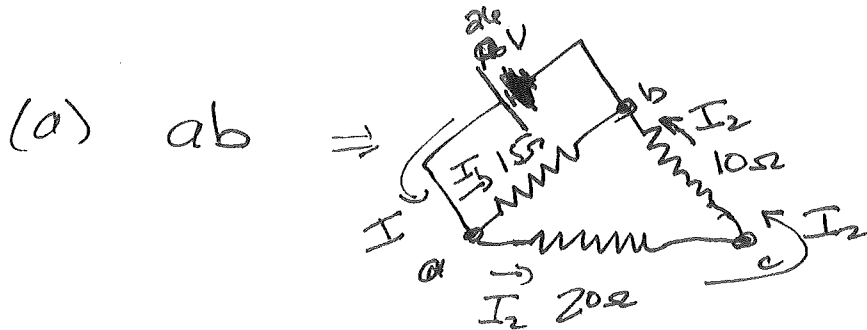
WHAT CURRENT FROM 26V battery IF  
Connected to:




Current splits at a  
 $I_1$  goes through  $15\Omega$   
then back to battery

$I_2$  goes through  $20\Omega$  then  $10\Omega$   
then back to battery

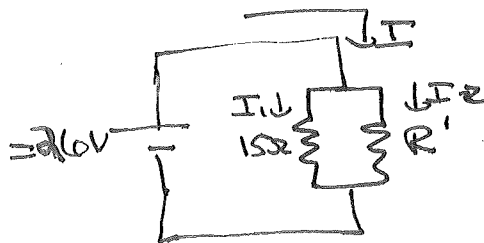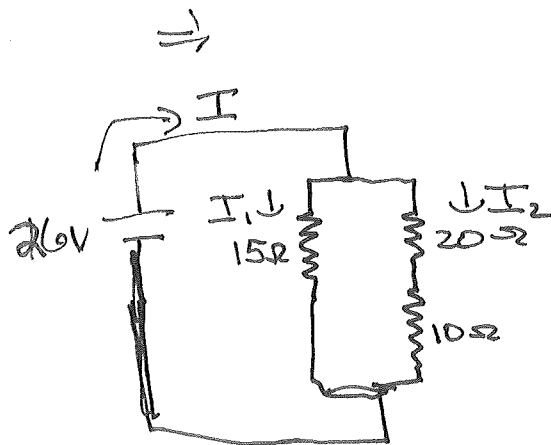$\Rightarrow 20\Omega + 10\Omega$  IN SERIES. By "Finger Test"  $15\Omega$  IN parallel  
to  $20\Omega/10\Omega$  COMBINATION




$$R' = 20\Omega + 10\Omega = 30\Omega$$

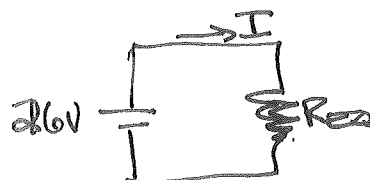

$$R_{eq} = \frac{15\Omega(30\Omega)}{15\Omega + 30\Omega} = 10\Omega$$


$$\Rightarrow I = \frac{26V}{10\Omega} = 2.6A$$

b) bc

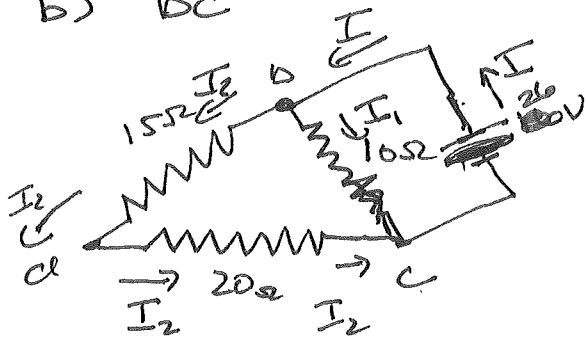

Now when Current splits,  $I_1$  goes Through  $10\Omega$  then back to battery.  $I_2$  goes through  $15\Omega$  then  $20\Omega$

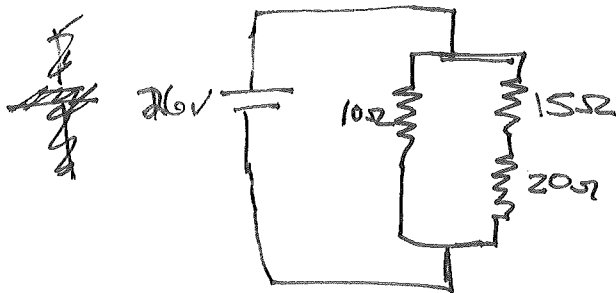
$\Rightarrow 15\Omega$  AND  $20\Omega$  IN Series,  $10\Omega$  IN parallel to Combination .




SAME Calculation For  $R_{eq}$  but

$$R' = 15\Omega + 20\Omega = 35\Omega$$

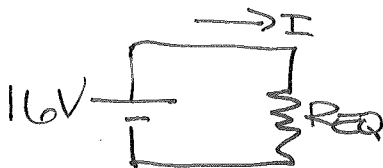
$$\Rightarrow R_{eq} = \frac{(10\Omega)(35\Omega)}{(10\Omega + 35\Omega)} = 7.77... \Omega$$



$$I = \frac{26V}{7.77\Omega} = 3.34A$$

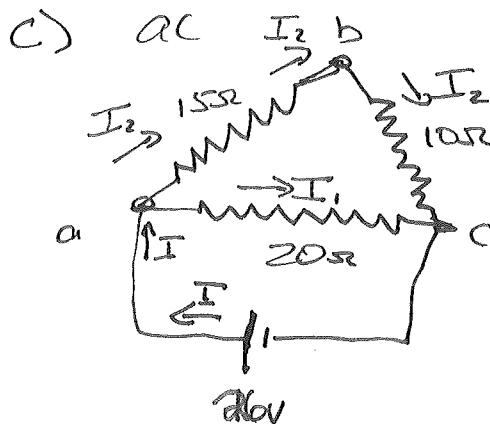

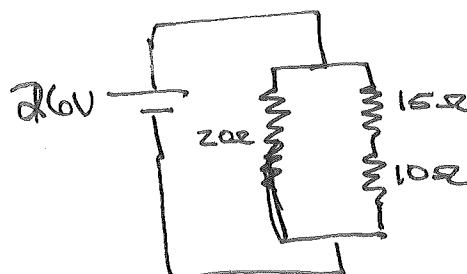~~20Ω~~  $15\Omega$  AND  $10\Omega$  IN Series,  $20\Omega$  IN parallel with Combination



$$R' = 15\Omega + 10\Omega = 25\Omega$$


$$R_{eq} = \frac{(20\Omega)(25\Omega)}{(20\Omega + 25\Omega)}$$

$$= 11.111... \Omega$$


$$\Rightarrow I = \frac{26V}{11.11\Omega} = 2.34A$$

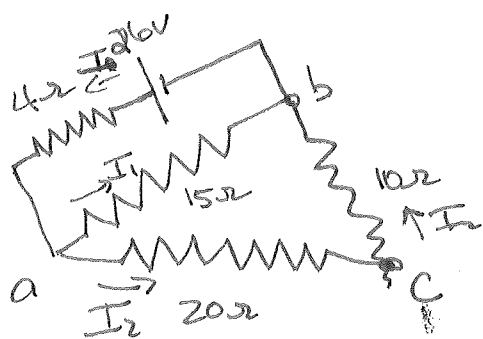d) IF Battery HAS  $4\Omega$  of internal Resistance, what Current if Connected across ab?


Simply ADD  $4\Omega$  is Series with battery.



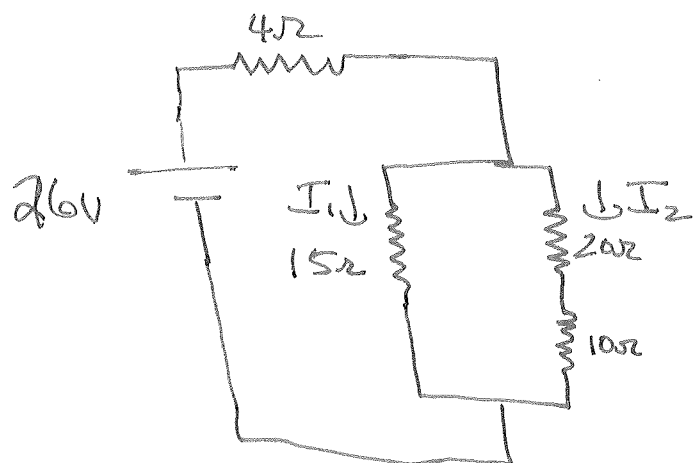Still HAVE  $20\Omega$  and  $10\Omega$  in Series,  
 $15\Omega$  in Parallel with combination.



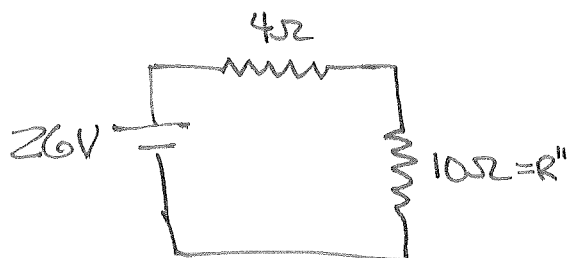Like Before the  $20\Omega$ ,  $10\Omega$  And  $15\Omega$   
 Behave like  $R'' = \frac{(15\Omega)(30\Omega)}{(15\Omega + 30\Omega)} = 10\Omega$



$4\Omega$  AND  $R''$  in Series  $\Rightarrow R_{eq} = 4\Omega + 10\Omega$   
 $\Rightarrow R_{eq} = 14\Omega$

$$I = \frac{26V}{14\Omega} = 1.857A = 1.86A$$

In Summary:

	ab	bc	ac	ab with Int. R
I	2.6A	3.34A	2.34A	1.86A