

Lecture 37

(L-C & L-R-C Circuits)

Physics 161-01 Spring 2012

Douglas Fields

LC Circuits


- Let's expand our usage of inductors by introducing a capacitor into the circuit.
- We start with a charged capacitor in series with a switch and an inductor.
- Let's apply Kirchhoff's loop rule:

$$\sum \Delta V = -\frac{q}{C} - L \frac{di}{dt} = 0 \Rightarrow$$

$$\frac{q}{C} + L \frac{di}{dt} = 0 \Rightarrow$$

$$L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0 \Rightarrow$$
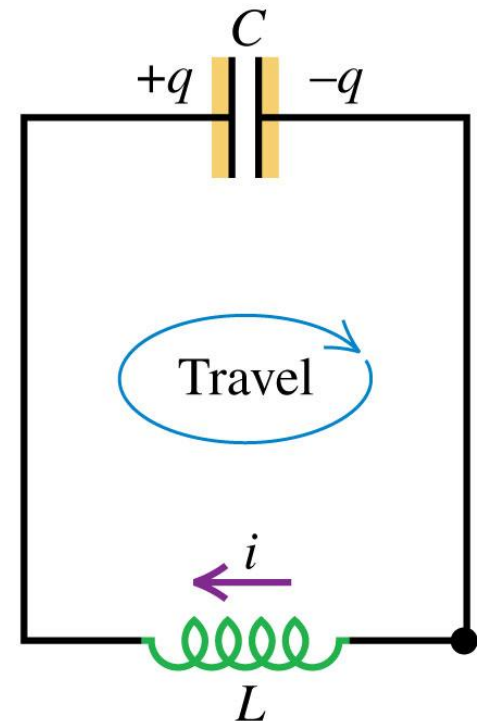
$$\frac{d^2 q}{dt^2} + \frac{1}{LC} q = 0$$



LC Circuits

- Do you recognize this equation?

$$\frac{d^2q}{dt^2} + \frac{1}{LC}q = 0$$

- What if I just changed q to x and renamed the constant?


$$\frac{d^2x}{dt^2} + \omega^2x = 0$$

- So the equation just describes oscillations with a frequency:

$$\frac{d^2q}{dt^2} + \frac{1}{LC}q = 0 \Rightarrow$$

$$q = Q_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

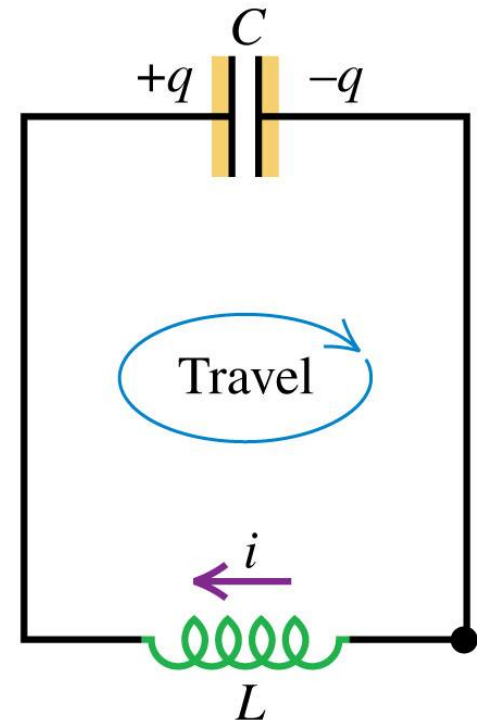

Analogy to Spring-Mass Oscillations

$$\frac{d^2x}{dt^2} + \frac{k}{m}x = 0 \Rightarrow$$

$$x = X_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$\frac{d^2q}{dt^2} + \frac{1}{LC}q = 0 \Rightarrow$$

$$q = Q_0 \cos(\omega t + \phi)$$

$$\omega = \sqrt{\frac{1}{LC}}$$

Table 30.1 Oscillation of a Mass-Spring System Compared with Electrical Oscillation in an *L-C* Circuit

Mass-Spring System

$$\text{Kinetic energy} = \frac{1}{2}mv_x^2$$

$$\text{Potential energy} = \frac{1}{2}kx^2$$

$$\frac{1}{2}mv_x^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2$$

$$v_x = \pm \sqrt{k/m} \sqrt{A^2 - x^2}$$

$$v_x = dx/dt$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$x = A \cos(\omega t + \phi)$$

Inductor-Capacitor Circuit

$$\text{Magnetic energy} = \frac{1}{2}Li^2$$

$$\text{Electric energy} = q^2/2C$$

$$\frac{1}{2}Li^2 + q^2/2C = Q^2/2C$$

$$i = \pm \sqrt{1/LC} \sqrt{Q^2 - q^2}$$

$$i = dq/dt$$




$$\omega = \sqrt{\frac{1}{LC}}$$

$$q = Q \cos(\omega t + \phi)$$

Energy/Current/Charge Oscillations


— $q = Q_0 \cos(\omega t + \phi)$

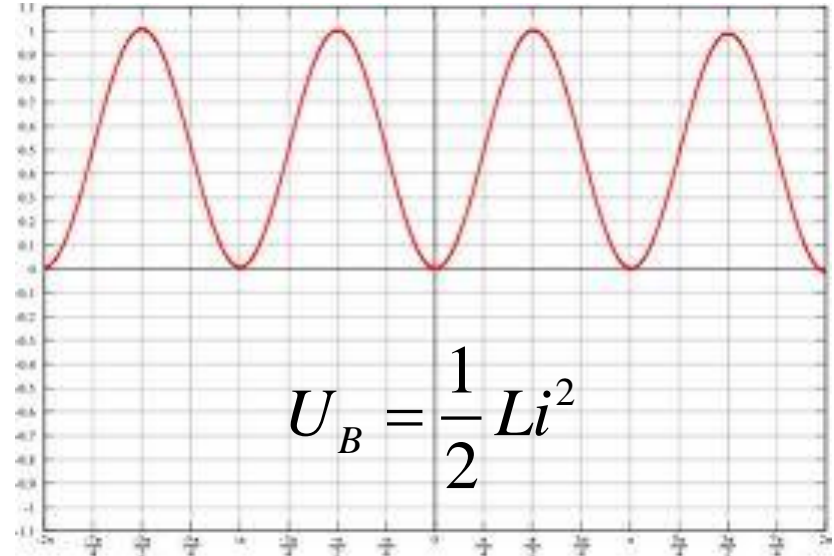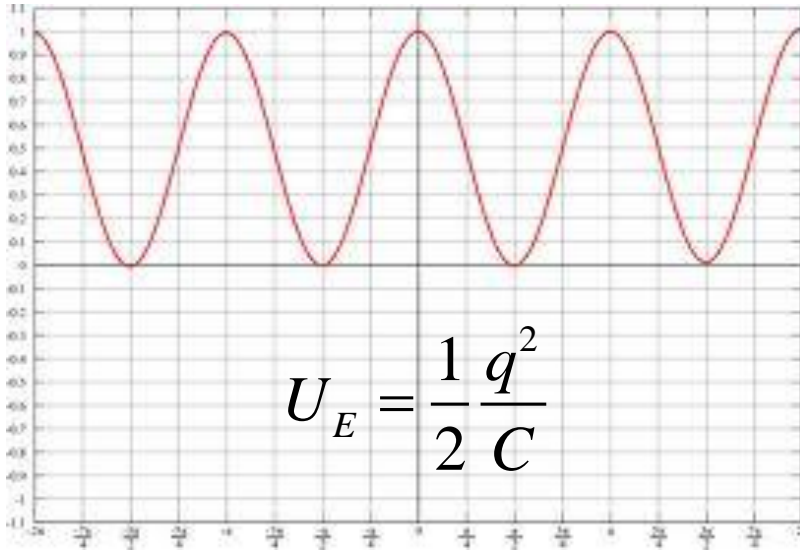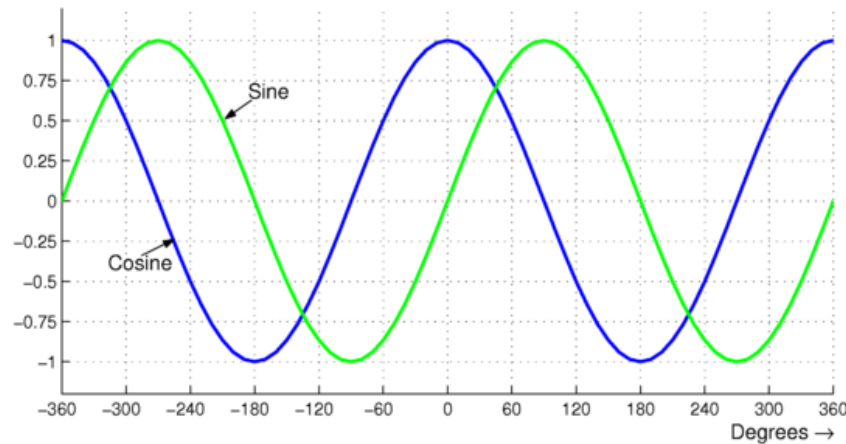— $i = -Q_0 \omega \sin(\omega t + \phi)$



Energy/Current/Charge Oscillations


$$E_{\text{Total}} = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} Li^2 = \text{Constant} = \frac{1}{2} \frac{Q_{\text{max}}^2}{C} = \frac{1}{2} LI_{\text{max}}^2$$

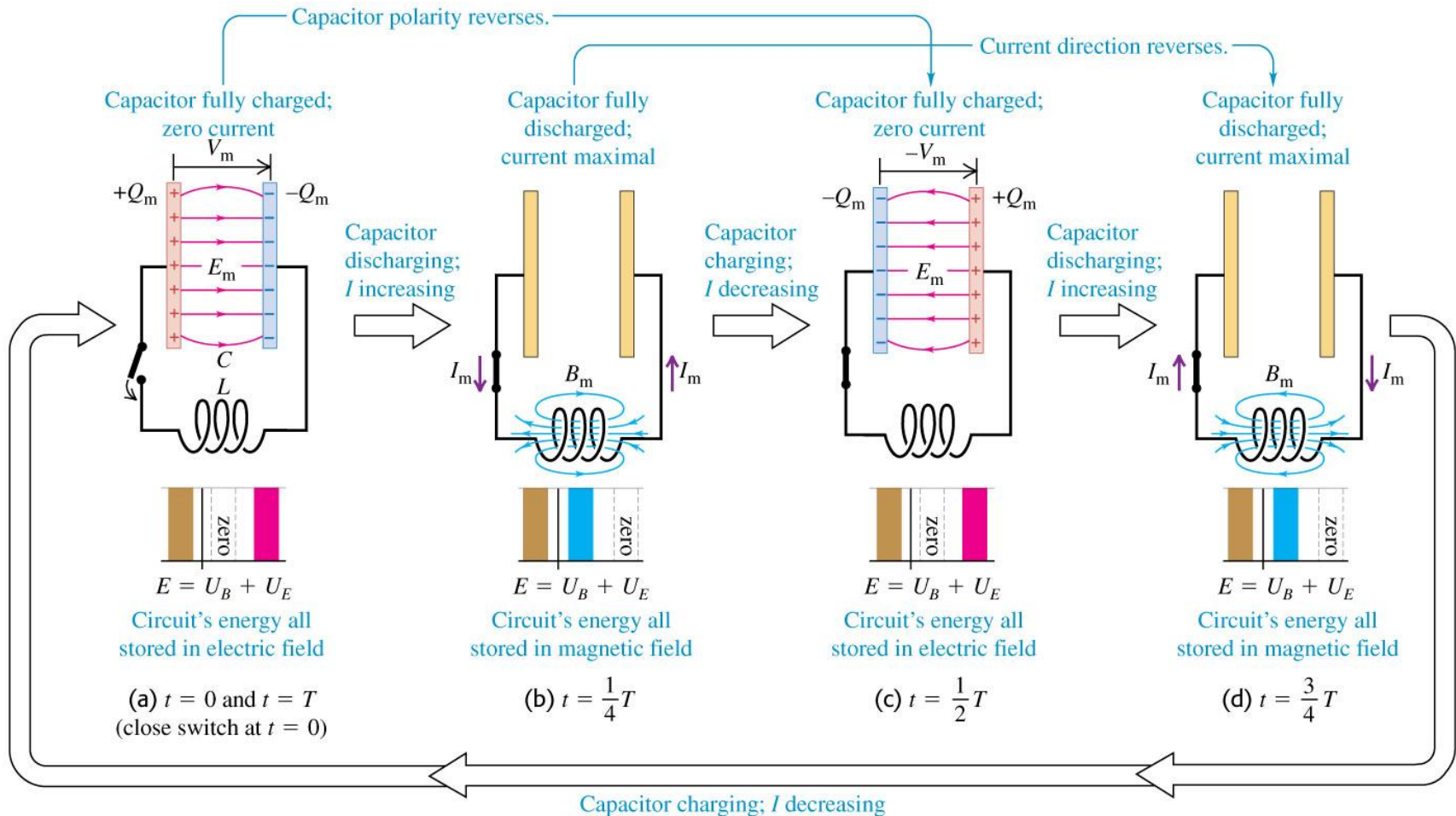

CPS 37-1

An inductor (inductance L) and a capacitor (capacitance C) are connected as shown.

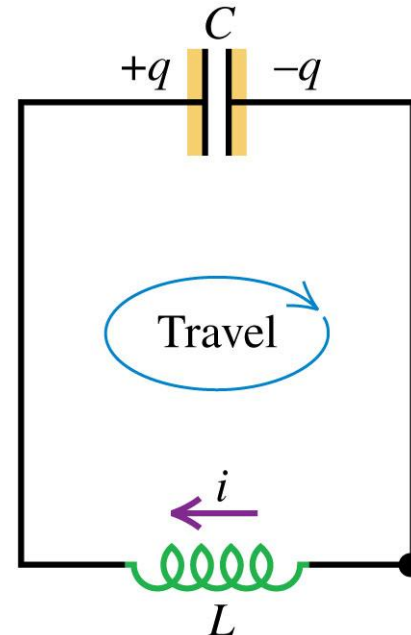If the values of both L and C are doubled, what happens to the *time* required for the capacitor charge to oscillate through a complete cycle?




© 2012 Pearson Education, Inc.

- A. It becomes 4 times longer.
- B. It becomes twice as long.
- C. It is unchanged.
- D. It becomes $1/2$ as long.
- E. It becomes $1/4$ as long.

CPS 37-1

An inductor (inductance L) and a capacitor (capacitance C) are connected as shown.

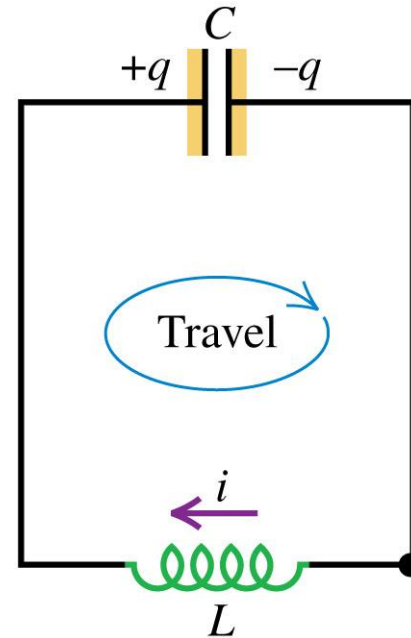If the values of both L and C are doubled, what happens to the *time* required for the capacitor charge to oscillate through a complete cycle?




© 2012 Pearson Education, Inc.

- ✓ A. It becomes 4 times longer.
- B. It becomes twice as long.
- C. It is unchanged.
- D. It becomes $1/2$ as long.
- E. It becomes $1/4$ as long.


Energy/Current/Charge Oscillations

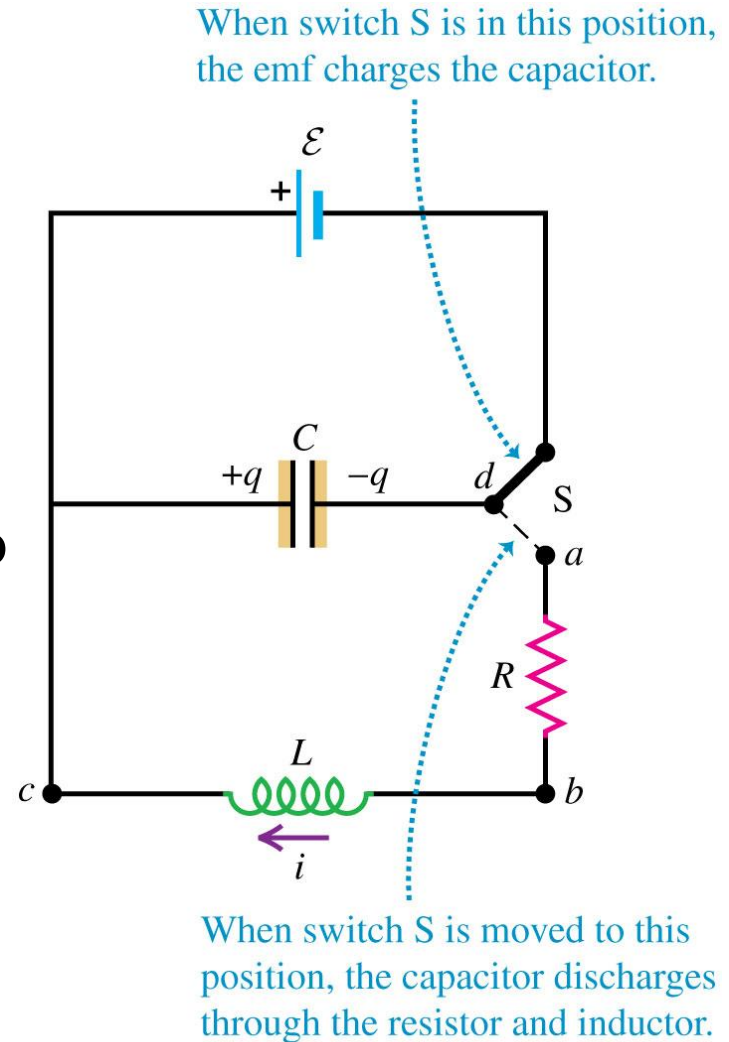- Now that you have the spring-mass system in your head as an analogy, what do you think happens if we put a resistor in series with the capacitor and inductor?
- Remember that with the resistor, the total energy will decrease due to the power dissipated in the resistor.




Energy/Current/Charge Oscillations

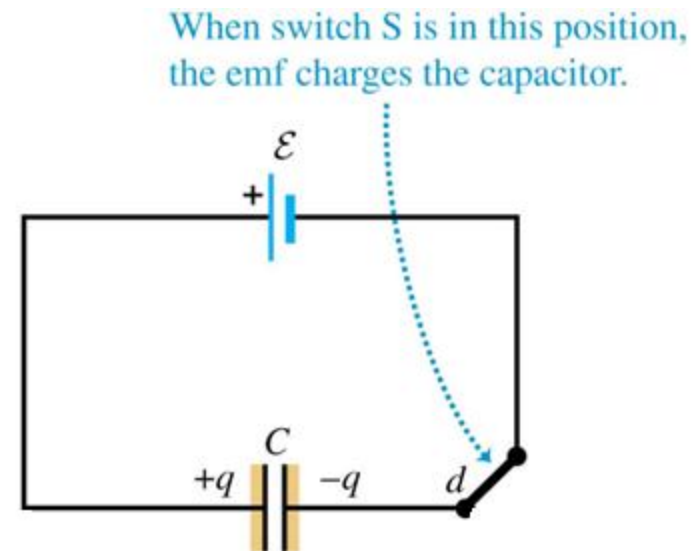- Let's first charge the capacitor with an EMF.



Energy/Current/Charge Oscillations

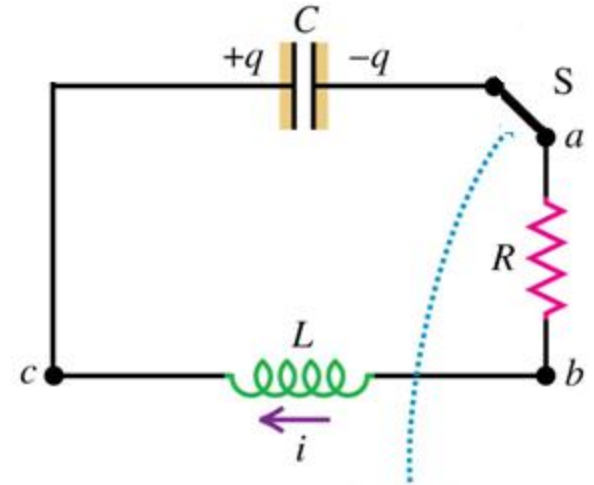- Then, remove the EMF and hook the capacitor in series to the resistor and inductor.



When switch S is moved to this position, the capacitor discharges through the resistor and inductor.

© 2012 Pearson Education, Inc.


$$\sum \Delta V = -iR - \frac{q}{C} - L \frac{di}{dt} = 0 \Rightarrow$$

$$\frac{q}{C} + L \frac{di}{dt} + iR = 0 \Rightarrow$$

$$\frac{d^2 q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0$$

Energy/Current/Charge Oscillations

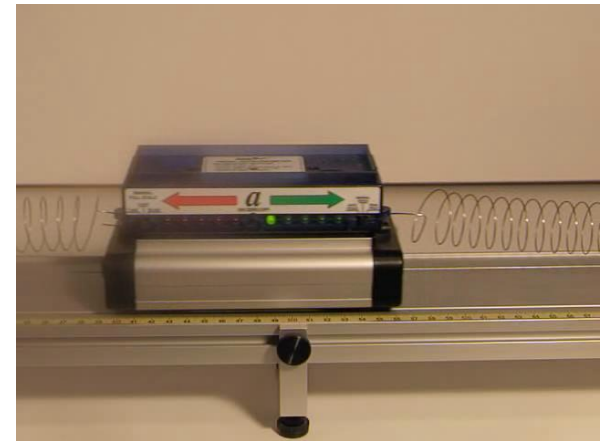- This should remind you of the equation for damped simple harmonic oscillations.



Energy/Current/Charge Oscillations

- With a relatively small resistor,


$$R^2 < \frac{4L}{C}$$

then there are oscillations whose amplitude decreases exponentially in time.

$$q = Ae^{-(R/2L)t} \cos\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t + \phi\right)$$

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

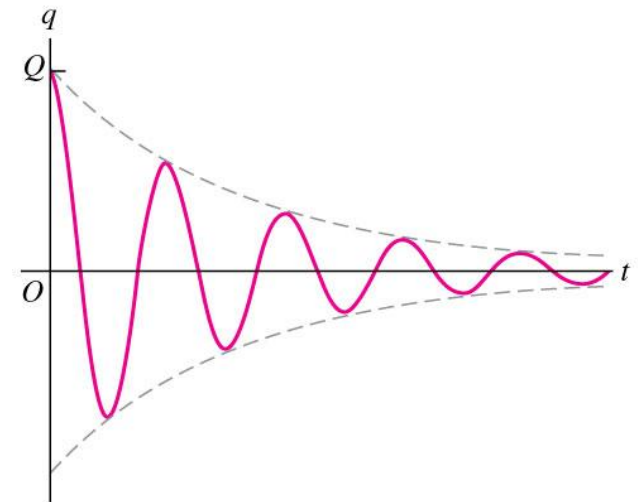(a) Underdamped circuit (small resistance R)



Energy/Current/Charge Oscillations

- When you increase the resistance to


$$R^2 = \frac{4L}{C}$$

then the system no longer oscillates, but instead damps down as quickly as is possible.

$$q = Ae^{-(R/2L)t} \cos\left(\sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}t + \phi\right)$$

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} = 0$$

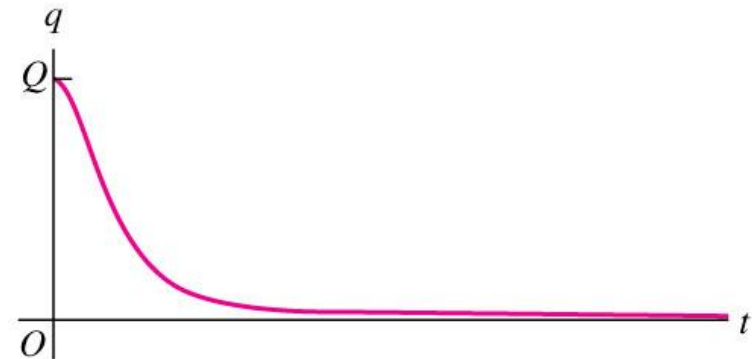(b) Critically damped circuit (larger resistance R)



Energy/Current/Charge Oscillations

- As you continue to increase the resistance,

$$R^2 > \frac{4L}{C}$$

again, you get no oscillations, but it takes a longer time for the charge on the capacitor to fully dissipate.

(c) Overdamped circuit (very large resistance R)

