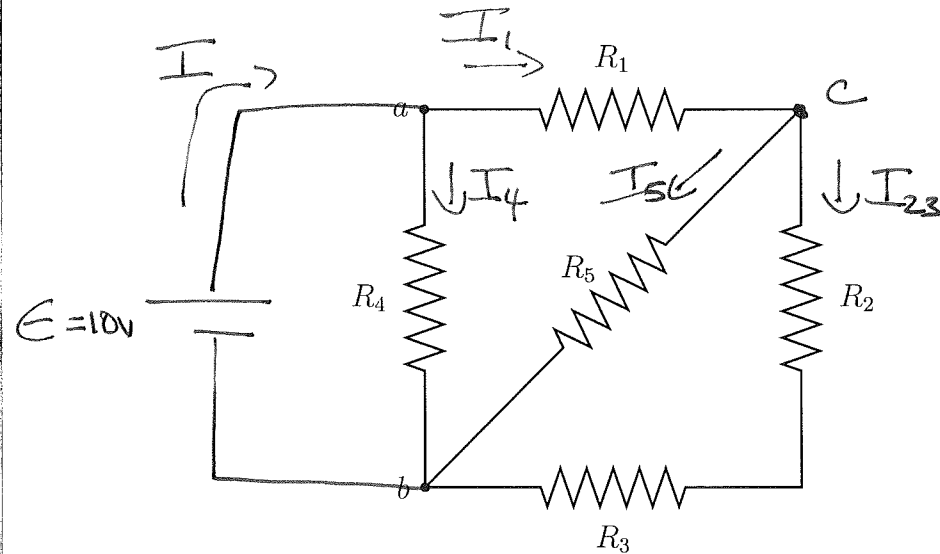


PHYSICS 161 TEST 4



$R_1 = 500 \Omega$
$R_2 = 200 \Omega$
$R_3 = 400 \Omega$
$R_4 = 100 \Omega$
$R_5 = 350 \Omega$

- (a) If a 10 V battery is connected to the points a and b, what is the equivalent resistance for this circuit? (8 pts)


Draw Battery AS SHOWN. At "a" Current From Battery splits INTO I_1 AND I_4 AS SHOWN. I_1 splits at "c" INTO I_5 AND I_{23} (SINCE ALL CURRENTS RECOMBINE at "b")

$\Rightarrow R_2$ AND R_3 IN SERIES. "Finger Test" shows R_5 IN Parallel WITH R_2/R_3 COMBINATION.

$I_1 = I_5 + I_{23} \Rightarrow R_1$ IN SERIES WITH $R_2/R_3/R_5$ COMBINATION

FINALLY, Finger Test $\Rightarrow R_4$ IN parallel WITH EVERYTHING ELSE


So our helpful DIAGRAM Looks Like:

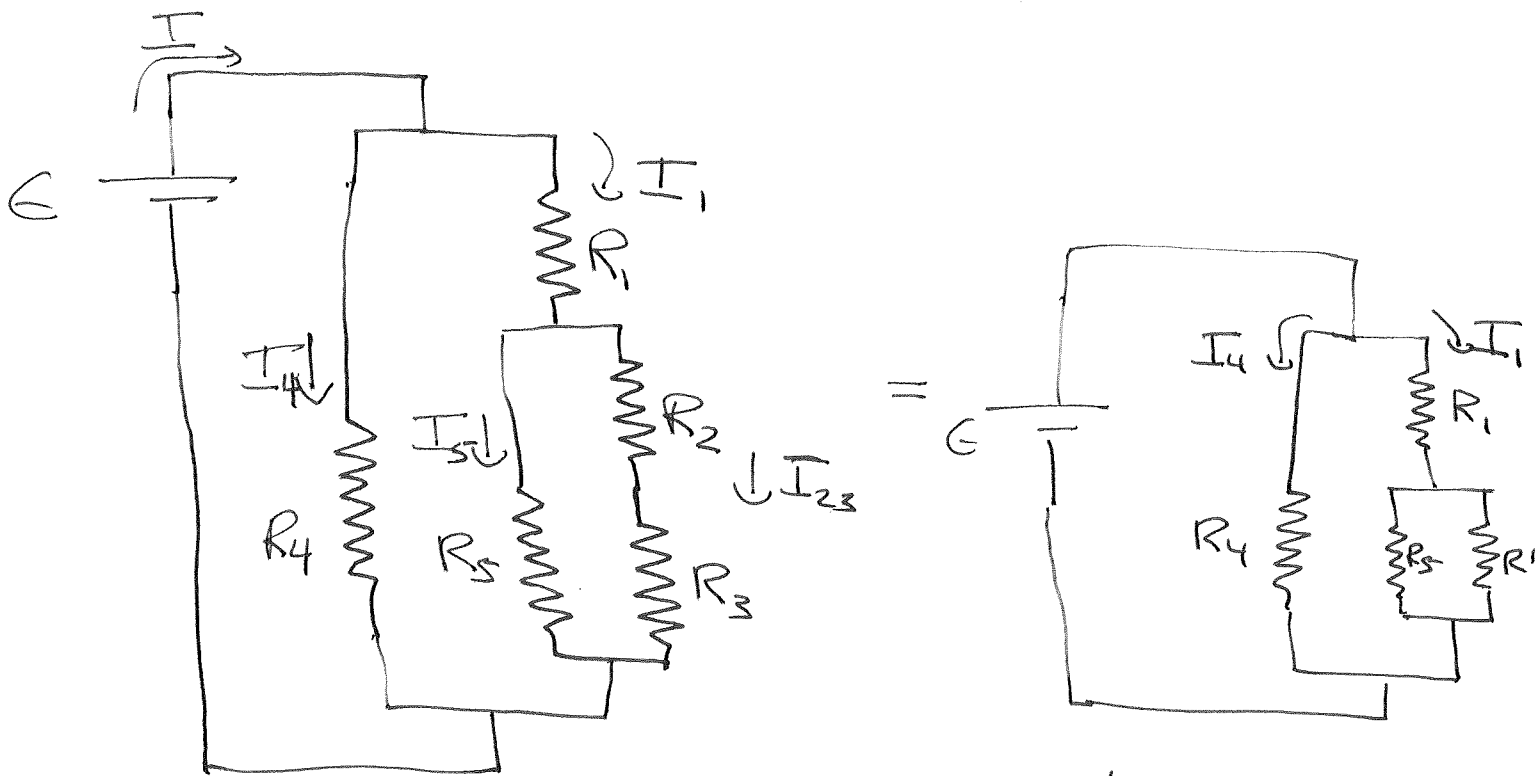

$$R' = R_2 + R_3 = 200\Omega + 400\Omega = 600\Omega$$

$$R_5 \text{ \& } R' \text{ in parallel} \Rightarrow R'' = \frac{R_5 R'}{R_5 + R'} = \frac{(350\Omega)(600\Omega)}{950\Omega} = 221\Omega$$
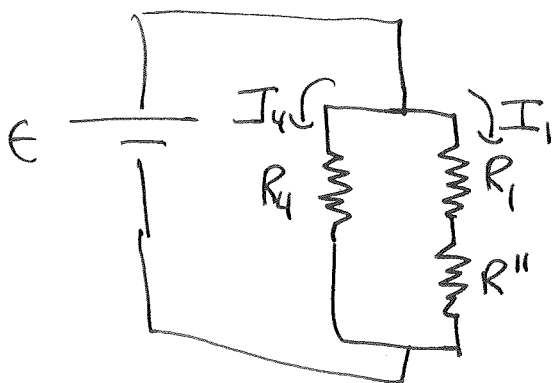
$$\hookrightarrow \frac{4200}{19} \Omega \text{ to be EXACT}$$




$$R_1 \text{ \& } R'' \text{ in series} \Rightarrow R''' = R_1 + R''$$

$$R''' = 500\Omega + 221\Omega$$

$$= 721\Omega \left(\frac{13700}{19} \Omega \right)$$

Finally:

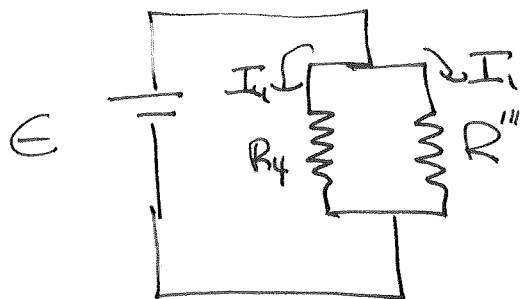

$$\text{Parallel} \Rightarrow R_{EQ} = \frac{R_4 R''}{R_4 + R''}$$

$$\Rightarrow R_{EQ} = \frac{(100\Omega)(781\Omega)}{(821\Omega)}$$

$$\Rightarrow R_{EQ} = 87.82\Omega$$

$$\text{EXACT : } \frac{1370000}{15600} = \frac{13700}{156} = \frac{6850}{78} = \frac{3425}{39} \Omega$$

b) WHICH RESISTOR uses Most Power? What Percentage of Power Supplied by battery?

Power Supplied by battery: $P = IE$.

$$I = \frac{E}{R_{eq}} = \frac{10V}{87.82\Omega} = 0.1139A \quad \therefore P = (0.1139A)(10V) = 1.139Watt$$

$P = IV \Rightarrow$ MOST Current AND Highest Voltage uses most Power.

Obvious CANDIDATE is R_4 SINCE "Finger Test" shows $V_4 = E = 10V$

$$P_4 = I_4 V_4 = \frac{V_4^2}{R_4} = \frac{(10V)^2}{100\Omega} = 1Watt$$

\Rightarrow OTHER RESISTORS USING $1.139Watt - 1Watt = 0.139Watt$ in total!

SO DEFINITELY R_4 .

$$\% = \frac{1Watt}{1.139Watt} = 87.8\%$$