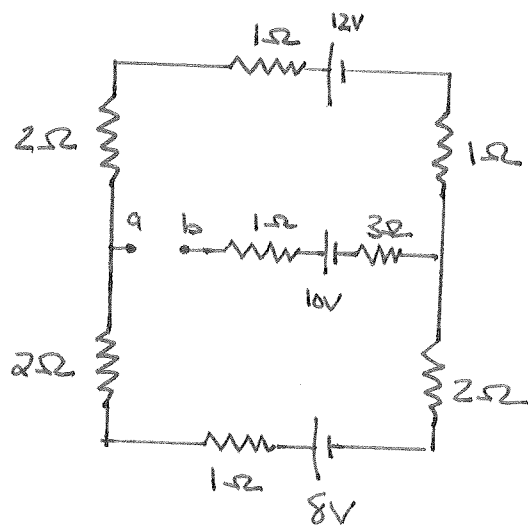



Physics 161, Hw #5

#1



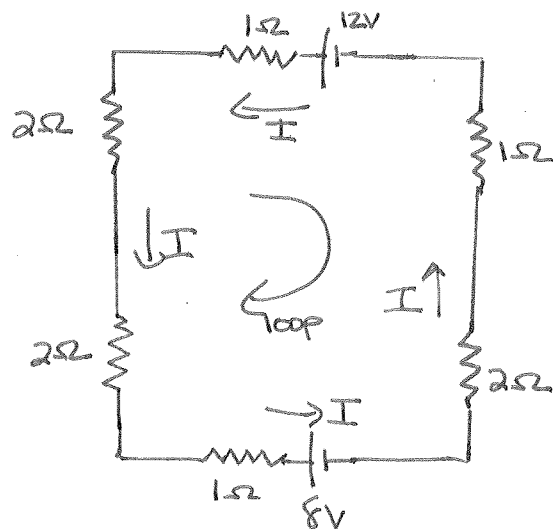a)  $V_{ab} = ?$  WITH GAP BETWEEN  $a$  &  $b$  NO CURRENT CAN FLOW FROM 10V battery

$\Rightarrow$  REMOVE THAT BRANCH WHEN CALCULATING CURRENT.




All elements in Series  $\Rightarrow$  ONE current  $I$   
AS SHOWN

$$\text{Loop: } +I(1\Omega) - 12V + I(1\Omega) + I(2\Omega) + 8V + I(1\Omega) + I(2\Omega) + I(2\Omega) = 0$$

$$\Rightarrow I(9\Omega) - 4V = 0$$

$$\Rightarrow I = \frac{4}{9} A = .444... A$$

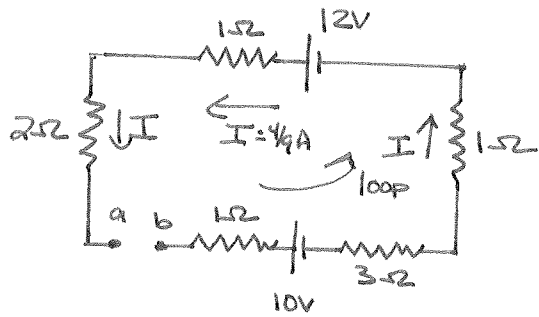To Find  $V_{ab}$  do an incomplete Loop From b to a




$$V_b - 0A(1\Omega) - 10V - 0A(3\Omega) - I(1\Omega) + 12V - I(1\Omega) - I(2\Omega) = V_a$$

$$\Rightarrow V_a - V_b = V_{ab} = 2V - I(4\Omega) = 2V - \frac{4}{9}A(4\Omega)$$

$$\Rightarrow \boxed{V_{ab} = .222...V = .222V}$$

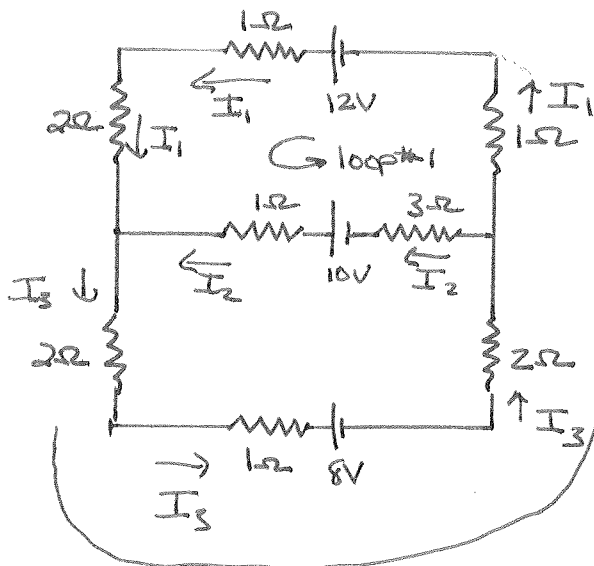b) IF a & b CONNECTED FIND Current IN 12V battery.



Now HAVE 3 currents,  $I_1, I_2, I_3$   
AS SHOWN

Junction Rule:  $I_1 + I_2 = I_3$

2 Loops: 'Upper' Loop AND Outer Loop

$$\text{From loop \#1: } -I_1(2\Omega) + I_2(1\Omega) - 10V + I_2(3\Omega) - I_1(1\Omega) + 12V - I_1(1\Omega) = 0$$

$$\Rightarrow -I_1(4\Omega) + I_2(4\Omega) + 2V = 0 \Rightarrow I_2 = \frac{I_1(4\Omega) - 2V}{4\Omega}$$

$$\Rightarrow I_2 = I_1 - .5A$$

$$\text{Loop \#2: } -I_1(2\Omega) - I_3(2\Omega) - I_3(1\Omega) - 8V - I_3(2\Omega) - I_1(1\Omega) + 12V - I_1(1\Omega) = 0$$

$$\Rightarrow -I_1(4\Omega) - I_3(5\Omega) + 4V = 0$$

$$\Rightarrow I_3 = \frac{4V - I_1(4\Omega)}{5\Omega} = .8A - .8I_1$$

$$I_1 + I_2 = I_3 \Rightarrow I_1 + (I_1 - .5A) = (.8A - .8I_1)$$


$$\Rightarrow 2I_1 - .5A = .8A - .8I_1 \Rightarrow 2.8I_1 = 1.3A$$

$$\Rightarrow \boxed{I_1 = .46428A = .464A \rightarrow \left(\frac{13}{28}A\right)}$$

For Completeness:  $I_2 = -.0357A \rightarrow \text{labeled wrong!}$

$$I_3 = .4286A$$

~~11.8~~

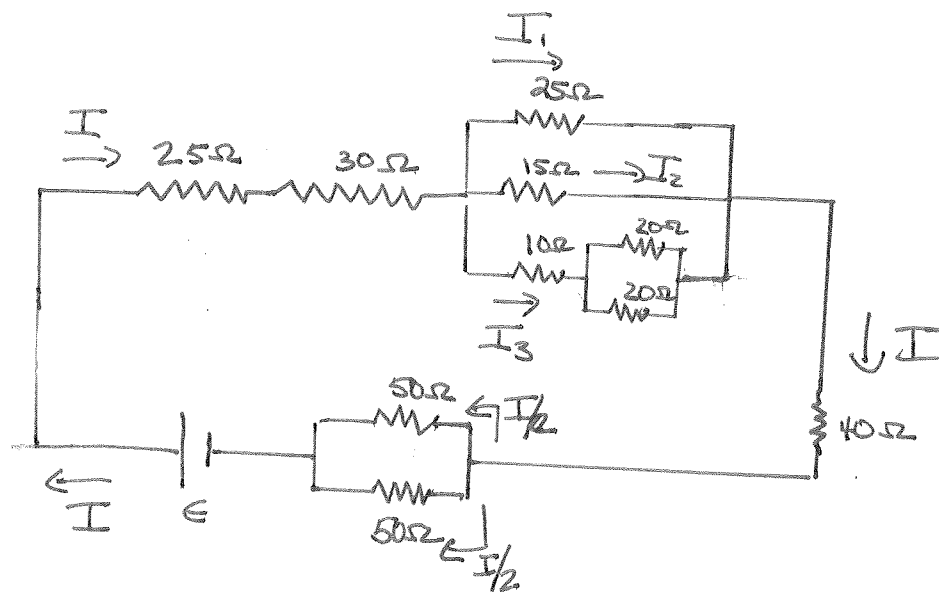

MAXIMUM POWER FOR ALL RESISTORS IS <sup>1.75</sup> 2 Watt. FIND MAX EMF

$P = I^2 R \Rightarrow$  RESISTOR WHICH GETS MAXIMUM CURRENT USES MOST POWER


Let  $I$  be current FROM BATTERY

AS LABELED ABOVE  $I_1 + I_2 + I_3 = I \Rightarrow$  EACH SMALLER THAN  $I$

OTHER PARALLEL EVEN EASIER, TWO EQUAL RESISTORS  $\Rightarrow$  EACH get  $I/2$  current

$\Rightarrow$  THE  $25\Omega, 30\Omega, 40\Omega$  ALL GET MAX CURRENT, SO  $40\Omega$  BEING LARGEST  $\Rightarrow$  <sup>1.75</sup> 1 Watt =  $I^2(40\Omega) \Rightarrow I = \text{~~0.209165 A~~ } 0.209165 A$

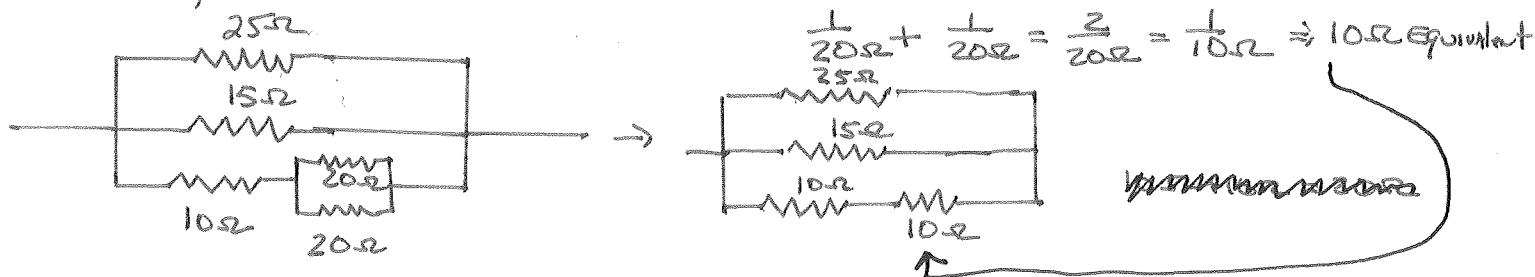TO FIND  $\epsilon$ , FIND EQUIVALENT RESISTANCE, LET'S LOOK AT CIRCUIT IN PIECES




$$10\Omega + 10\Omega = 20\Omega \Rightarrow \begin{array}{c} 25\Omega \\ \text{---} \\ 15\Omega \\ \text{---} \\ 20\Omega \end{array} = R''$$

$$\frac{1}{R''} = \frac{1}{25\Omega} + \frac{1}{15\Omega} + \frac{1}{20\Omega} = .1566... \Omega^{-1} \Rightarrow R'' = \frac{1}{.1566... \Omega^{-1}} = 6.383\Omega$$

Next Piece:
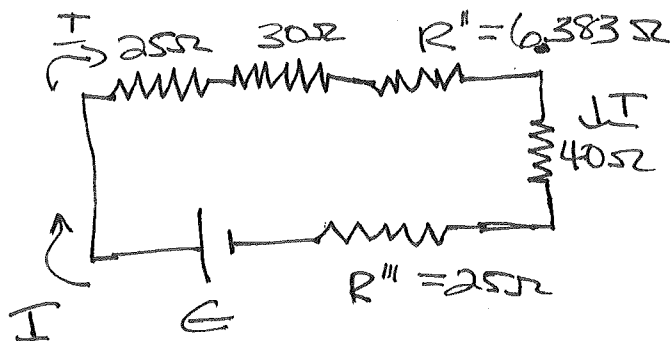
$$\begin{array}{c} 50\Omega \\ \text{---} \\ 50\Omega \end{array} \rightarrow R''' \quad R''' = \frac{(50\Omega)(50\Omega)}{(50\Omega + 50\Omega)} = 25\Omega$$



All in Series  $\Rightarrow$


$$R_{EQ} = 25\Omega + 30\Omega + 6.383\Omega + 25\Omega$$

$$\Rightarrow R_{EQ} = 126.383\Omega$$

$$E = I R_{EQ} \Rightarrow E = (0.209165A)(126.383\Omega) = 26.4549V$$

$$\Rightarrow \boxed{E = 26.4V}$$

Q3

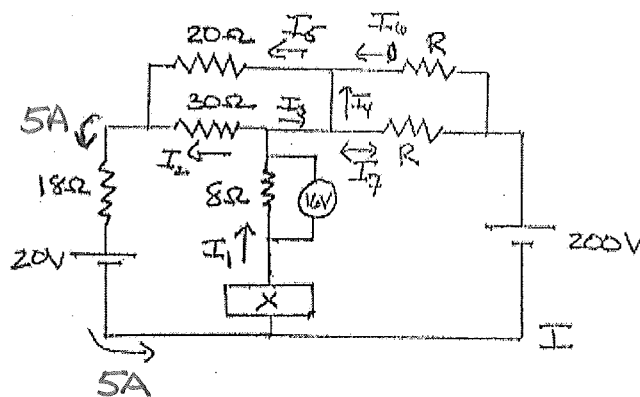

LOWER END OF  $8\Omega$  RESISTOR AT HIGHER POTENTIAL.


CURRENT FLOWS FROM HIGHER TO LOW POTENTIAL  $\Rightarrow$  CURRENT THROUGH  $8\Omega$  IS  $\uparrow$ . Let current through  $8\Omega$  be  $I_1$ .

a) Find EMF OF X.

$$\text{For } 8\Omega: V_{ab} = I_1 R \Rightarrow 16V = I_1 (8\Omega) \Rightarrow I_1 = 2A$$

Label remaining currents,  $I_2, I_3, I_4, I_5, I_6, I_7$  as shown

Look at this part first:

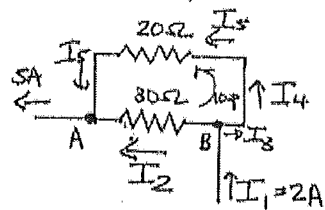

$$\text{From loop rule: } -I_5(20\Omega) + I_2(30\Omega) = 0$$

$$\Rightarrow I_5 = \frac{3}{2} I_2 = 1.5 I_2$$


$$\text{At A: Junction rule: } I_5 + I_2 = 5A$$

$$\Rightarrow \frac{3}{2} I_2 + I_2 = 5A \Rightarrow \frac{5}{2} I_2 = 5A$$

$$\Rightarrow I_2 = 2A \Rightarrow I_5 = 3A$$

$$\text{At B: Junction } \Rightarrow I_1 = I_2 + I_3 \Rightarrow 2A = 2A + I_3 \Rightarrow I_3 = 0$$

Now DO THE Following Loop:

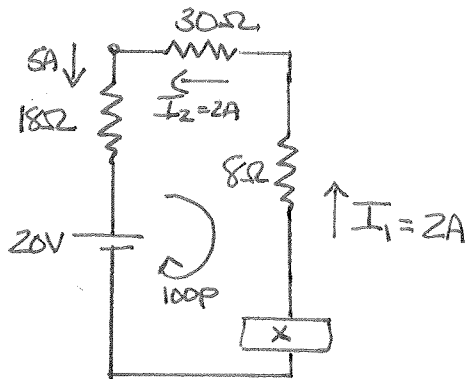

$$+2A(30\Omega) + 2A(8\Omega) + X + 20V + 5A(18\Omega) = 0$$


Assume  $\begin{array}{c} \text{+} \\ | \\ \text{+} \end{array}$  For Battery X

$$\Rightarrow 186V + X = 0 \Rightarrow X = -186V$$

$$\Rightarrow X = 186V \begin{array}{c} \text{+} \\ | \\ \text{+} \end{array}$$

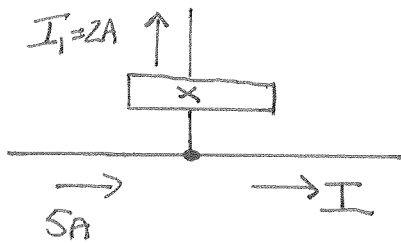b) Find  $I$  (WITH DIRECTION)

LOOK AT ~~LOWER~~ JUNCTION BELOW Battery X




JUNCTION RULE gives DIRECTION,  $I$  MUST BE AWAY FROM JUNCTION SO THAT


$$5A = 2A + I \Rightarrow I = 3A$$




c) Find R:

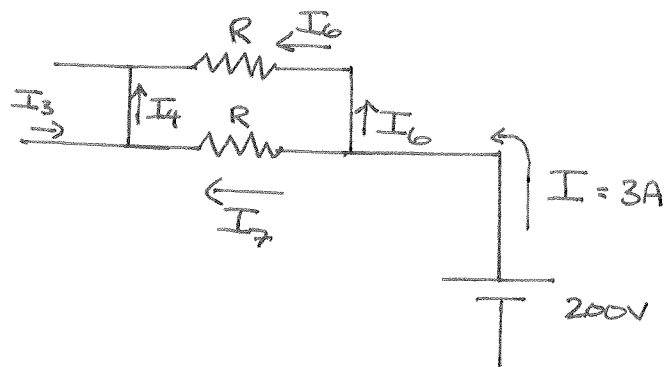

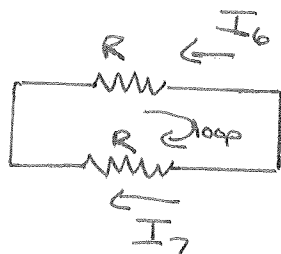Earlier found  $I_3 = 0 \Rightarrow I_3 + I_7 = I_4 \Rightarrow I_4 = I_7$  (ACTUALLY DON'T NEED)



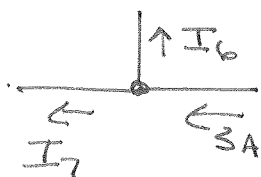
Loop Rule:  $+I_6R - I_7R = 0 \Rightarrow I_6 = I_7$



Junction:  $3A = I_7 + I_6 = I_7 + I_7$

$\Rightarrow 3A = 2I_7 \Rightarrow I_7 = 1.5A$

FINAL Loop:

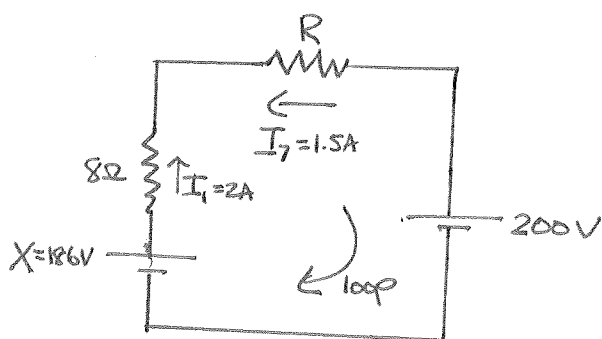


$+1.5A(R) - 200V + 186V - 2A(8\Omega) = 0$


$\Rightarrow 1.5A(R) - 30V = 0$

$\Rightarrow \boxed{R = 20\Omega}$


~~##~~

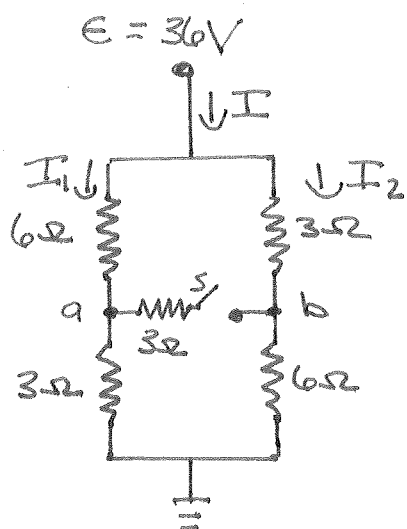

WITH SWITCH OPEN

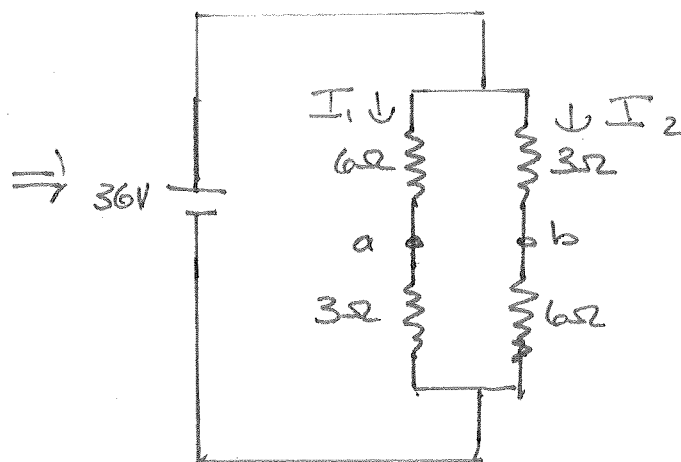

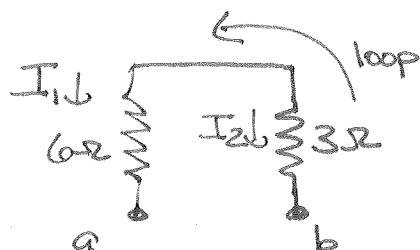a) WHAT IS  $V_{ab}$  WITH SWITCH OPEN: DO AN INCOMPLETE LOOP FROM b TO a:




$$V_b + I_2(3\Omega) - I_1(6\Omega) = V_a$$

$$\Rightarrow V_a - V_b = V_{ab} = I_2(3\Omega) - I_1(6\Omega)$$

TO FIND  $I_1$  AND  $I_2$ , WE CAN FIND  $R_{eq}$ .

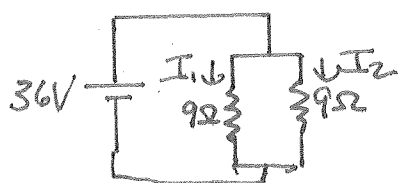BOTH PAIRS OF  $6\Omega$  AND  $3\Omega$  IN SERIES  $\Rightarrow 9\Omega$




BOTH  $9\Omega$  IN parallel to BATTERY  $\Rightarrow$

$$I_1 = I_2 = \frac{36V}{9\Omega} = 4A$$


$$\therefore V_{ab} = I_2(3\Omega) - I_1(6\Omega) = 4A(3\Omega) - 4A(6\Omega) = 4A(-3\Omega)$$

$$\Rightarrow \boxed{V_{ab} = -12V}$$

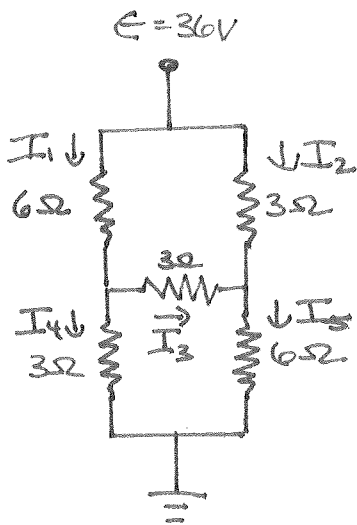b) When switch closed, what current through switch?



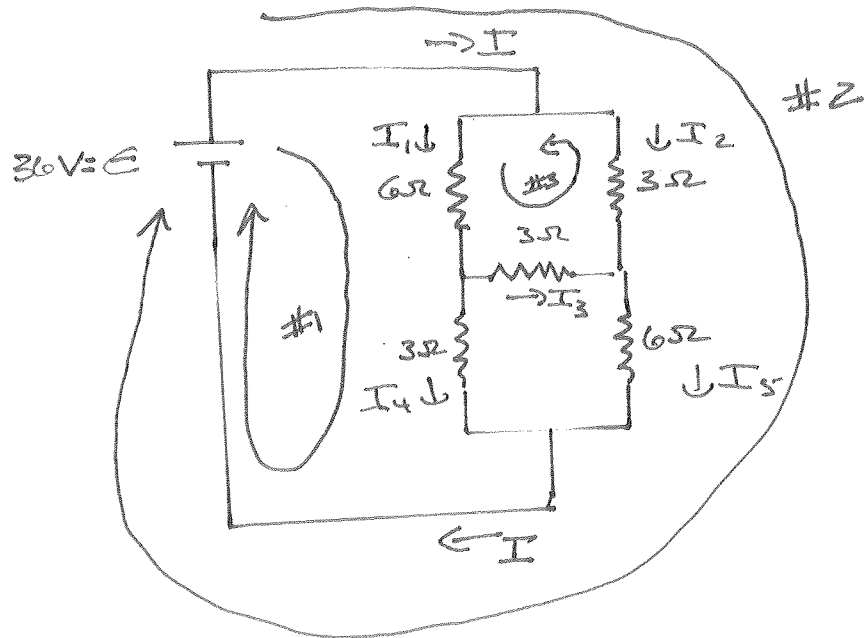$I_3 = ?$  No obvious parallel & series  
 $\Rightarrow$  KIRCHOFF'S



JUNCTION:  $I_1 + I_2 = I$

$$I_1 = I_3 + I_4 \Rightarrow \boxed{I_4 = I_1 - I_3}$$

$$I_2 + I_3 = I_5 \Rightarrow \boxed{I_5 = I_2 + I_3}$$

get rid of  $I_4$  AND  $I_5$

$$\text{Loop \#3: } -I_1(6\Omega) - I_3(3\Omega) + I_2(3\Omega) = 0$$

$$\Rightarrow \frac{-I_1(6\Omega) - I_3(3\Omega) + I_2(3\Omega)}{3\Omega} = 0$$

$$\Rightarrow -2I_1 - I_3 + I_2 = 0$$

$$I_1 = \frac{1}{3}I_3 + 4A, \quad I_2 = -\frac{2}{3}I_3 + 4A$$


$$\Rightarrow -2\left(\frac{1}{3}I_3 + 4A\right) - I_3 + \left(-\frac{2}{3}I_3 + 4A\right) = 0$$

$$\Rightarrow -\frac{2}{3}I_3 - 8A - I_3 - \frac{2}{3}I_3 + 4A = 0$$

$$\Rightarrow \left(-\frac{2}{3} - 1 - \frac{2}{3}\right)I_3 - 4A = 0 \Rightarrow -\frac{7}{3}I_3 = 4A$$

$$\Rightarrow \boxed{I_3 = -\frac{12}{7}A = -1.71A}$$

LABELED  $I_3$  IN  
WRONG DIRECTION

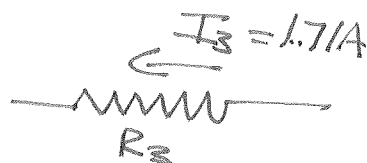

$$\text{Loop \#1: } -I_1(6\Omega) - I_4(3\Omega) + 36V = 0$$

$$\Rightarrow \frac{+I_1(6\Omega) + I_4(3\Omega)}{3\Omega} = \frac{36V}{3\Omega}$$

$$\Rightarrow 2I_1 + I_4 = 12A$$

$$I_4 = I_1 - I_3 \Rightarrow 2I_1 + (I_1 - I_3) = 12A$$

$$\Rightarrow 3I_1 - I_3 = 12A \Rightarrow \boxed{I_1 = \frac{1}{3}I_3 + 4A}$$

$$\text{Loop \#2: } -I_2(3\Omega) - I_5(6\Omega) + 36V = 0$$

$$\Rightarrow \frac{I_2(3\Omega) + I_5(6\Omega)}{3\Omega} = \frac{36V}{3\Omega}$$

$$\Rightarrow I_2 + 2I_5 = 12A$$


$$I_5 = I_2 + I_3 \Rightarrow I_2 + 2(I_2 + I_3) = 12A$$

$$\Rightarrow 3I_2 + 2I_3 = 12A \Rightarrow \boxed{I_2 = -\frac{2}{3}I_3 + 4A}$$

c). WHAT IS  $R_{EQ}$ ?

NOT BEING COMBINATIONS OF SERIES AND PARALLEL  
THIS CIRCUIT DOESN'T HAVE A "REAL"  $R_{EQ}$ .

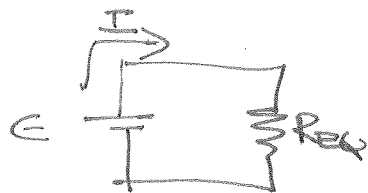BUT WE CAN DEFINE AN EFFECTIVE  $R_{EQ}$  FROM  
THE CONDITION THAT  $\mathcal{E} = I R_{EQ}$  WHERE  $I$  = CURRENT  
FROM BATTERY.



FROM JUNCTION RULE:  $I = I_1 + I_2$


$$I_1 = \frac{1}{3} I_3 + 4A = \frac{1}{3} \left( -\frac{12}{7} A \right) + 4A = -\frac{4}{7} A + 4A = \frac{24}{7} A = 3.4285A$$

$$I_2 = -\frac{2}{3} I_3 + 4A = -\frac{2}{3} \left( -\frac{12}{7} A \right) + 4A = +\frac{8}{7} A + 4A = \frac{36}{7} A = 5.143A$$

$$I = I_1 + I_2 = \frac{24}{7} A + \frac{36}{7} A = \frac{60}{7} A = 8.5711A$$

$$R_{EQ} = \frac{\mathcal{E}}{I} = \frac{36V}{\frac{60}{7}A} = \frac{252}{60} \Omega = 4.25\Omega$$

#5

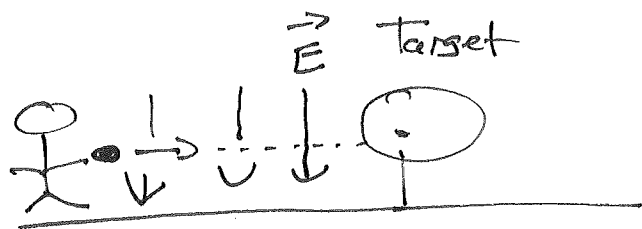

Coin:

$$M = 2.5g = 2.5 \times 10^{-3} \text{ kg}$$

$$Q = 4500 \mu\text{C} = 4500 \times 10^{-6} \text{ C} \\ = 4.5 \times 10^{-3} \text{ C}$$


$$V_0 = 15.2 \text{ m/s, Horizontal}$$

$$\vec{E} = 3.75 \text{ N/C, Down}$$

WHAT UNIFORM  $B$  to hit target?

Forces on Coin: Gravity, Electric Force,  $\vec{F}_E$ . Positive charge, DOWNWARD  $\vec{E} \Rightarrow$  DOWNWARD Force

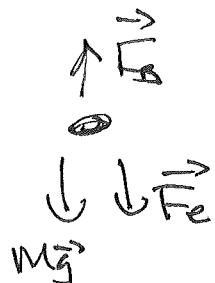Target Directly AHEAD of Coin  $\Rightarrow$  Coin needs to go Horizontally. Initial velocity is horizontal  $\Rightarrow$  ZERO Net Force




$$\sum \vec{F} = 0 \Rightarrow F_B - Mg - F_E = 0 \Rightarrow F_B = Mg + F_E \\ F_B = Mg + qE$$

$$F_B = (2.5 \times 10^{-3} \text{ kg})(9.8 \text{ m/s}^2) + (4.5 \times 10^{-3} \text{ C})(3.75 \text{ N/C}) \\ = .0245 \text{ N} + .016875 \text{ N} = .041375 \text{ N}$$

$$\Rightarrow \vec{F}_B = .041375 \text{ N, up}$$
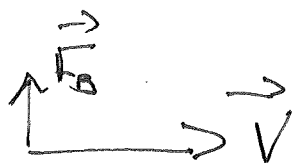
$$\vec{F}_B = q\vec{v} \times \vec{B}, \quad \vec{v} = \vec{v}_0 = 15.2 \text{ m/s, to right}$$



RHR  $\Rightarrow \vec{B}$  must be INTO PAGE  
to make  $\vec{F}_B$  up  $\Rightarrow \vec{B} = (\otimes)$


$$\Rightarrow F_B = qvB \sin 90^\circ = qvB \Rightarrow B = \frac{F_B}{qv} = \frac{.041375 \text{ N}}{(4.5 \times 10^{-8} \text{ C})(15.2 \text{ m/s})}$$

$$\Rightarrow \boxed{B = 0.605 \text{ T}} \leftarrow \text{Very LARGE, but not impossible so.}$$

OF COURSE THIS IS THE SMALLEST MAGNETIC FIELD NEEDED.

$\vec{B}$  doesn't have to be straight INTO THE PAGE to make  $\vec{F}_B$  point upwards. As long as  $\vec{B}$  has A COMPONENT INTO THE PAGE  $\vec{F}_B$  will be upward. THE OTHER COMPONENT OF  $\vec{B}$ , parallel to  $\vec{v}$ , causes NO FORCE.

Looking From "Above":

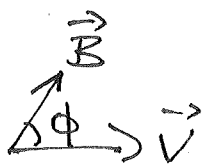


(Now  $\vec{F}_B = (\otimes)$ ,  $\phi = 90^\circ$   
gives previous result)

$$F_B = qvB \sin \phi \Rightarrow B = \frac{F_B}{qv \sin \phi} = \frac{0.605 \text{ T}}{\sin \phi} \quad 0 < \phi \leq 90^\circ$$

$$\Rightarrow B \geq 0.605 \text{ T}$$



#6

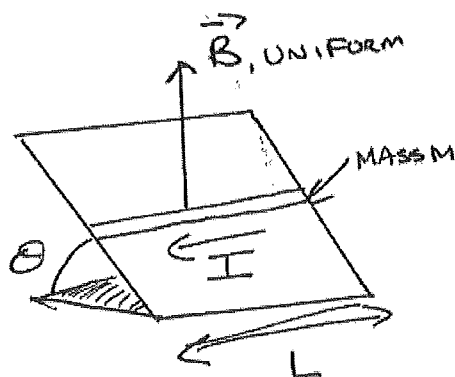


WHAT CURRENT KEEPS WIRE FROM SLIDING DOWN

Forces on wire: gravity which on an incline splits itself into parallel and perpendicular components,  $W_{\parallel} = Mg \sin \theta$ ,  $W_{\perp} = Mg \cos \theta$

A normal force,  $\vec{n}$  which is perpendicular  
and magnetic force,  $\vec{F}_M$

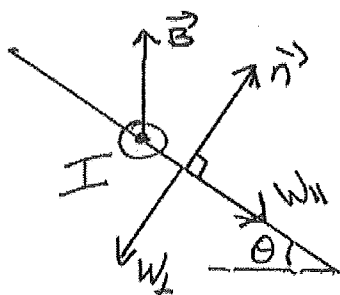IF WE DRAW THE INCLINE FROM THE SIDE, SUCH THAT  $\vec{B}$  is straight up, the incline is at angle  $\theta$ , the current will be into or out of page.



WE SEE THAT  $F_M$  MUST  
CANCEL  $W_{\parallel}$ .


FROM RIGHT HAND RULE, CURRENT  
MUST BE FLOWING OUT OF PAGE

$$I = \odot$$

SO ON ORIGINAL DRAWING CURRENT  
FLOWING RIGHT TO LEFT (AS SHOWN).


$$I = \odot, \vec{B} = \uparrow \Rightarrow F_M = ILB \sin 90^\circ = ILB$$

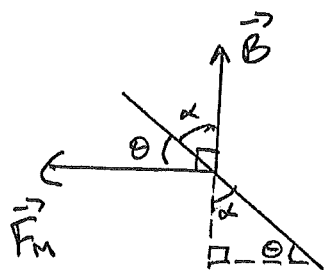but  $\vec{F}_M$  is NOT opposite to  $W_{\parallel}$ . IT IS  $90^\circ$  TO  $\vec{B}$ .




$$\alpha = 90^\circ - \theta$$

SO THE FREE BODY DIAGRAM LOOKS LIKE:

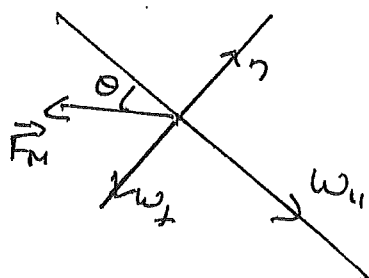

WHICH IS EASIER TO DRAW AS:

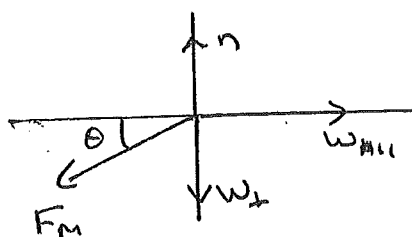

$$\sum F_{\parallel} = W_{\parallel} - F_m \cos \theta. \text{ NOT MOVING } \Rightarrow \sum F_{\parallel} = 0$$

$$\Rightarrow W_{\parallel} = F_m \cos \theta \Rightarrow Mg \sin \theta = I L B \cos \theta \Rightarrow I = \frac{Mg \sin \theta}{L B \cos \theta} = \frac{Mg}{L B} \left( \frac{\sin \theta}{\cos \theta} \right)$$

$$\Rightarrow \boxed{I = \frac{Mg \tan \theta}{L B}}$$

For Completeness:  $\sum F_n = n - W_{\perp} - F_m \sin \theta = 0$  (NOT MOVING)

$$\Rightarrow n = W_{\perp} + F_m \sin \theta = Mg \cos \theta + I L B \sin \theta = Mg \cos \theta + \frac{Mg}{L B} \left( \frac{\sin \theta}{\cos \theta} \right) L B \sin \theta$$

$$\Rightarrow n = Mg \cos \theta + Mg \frac{\sin^2 \theta}{\cos \theta} = \frac{Mg \cos^2 \theta}{\cos \theta} + \frac{Mg \sin^2 \theta}{\cos \theta} = \frac{Mg}{\cos \theta} (\cos^2 \theta + \sin^2 \theta)$$

$$\Rightarrow n = \frac{Mg}{\cos \theta} = Mg \sec \theta$$