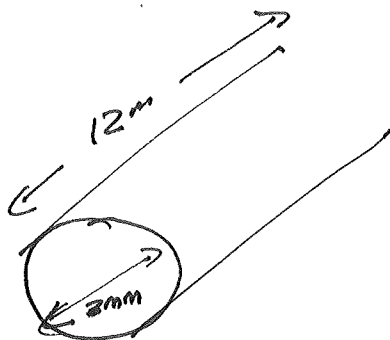


Physics 161, Hw #4

#1



$$R = .25 \Omega$$

Circular AREA OF DIAMETER 3mm

$$\Rightarrow r = 1.5 \text{ mm} = 1.5 \times 10^{-3} \text{ m}$$

$$A = \pi r^2 = \pi (1.5 \times 10^{-3} \text{ m})^2 = 7.069 \times 10^{-6} \text{ m}^2$$

a) WHAT IS RESISTIVITY?

$$R = \frac{\rho L}{A} \Rightarrow \rho = \frac{R \cdot A}{L} = \frac{.25 \Omega (7.069 \times 10^{-6} \text{ m}^2)}{12 \text{ m}} \Rightarrow \boxed{\rho = 1.47 \times 10^{-7} \Omega \cdot \text{m}}$$

b) IF  $E = 1.75 \text{ V/m}$ , WHAT IS TOTAL CURRENT?

$$E = \rho J \Rightarrow J = \frac{E}{\rho} = \frac{1.75 \text{ V/m}}{1.47 \times 10^{-7} \Omega \cdot \text{m}} = 1.19 \times 10^7 \text{ A/m}^2$$

$$J = \frac{I}{A} \Rightarrow I = JA = (1.19 \times 10^7 \text{ A/m}^2) (7.069 \times 10^{-6} \text{ m}^2) \Rightarrow \boxed{I = 84.2 \text{ A}}$$

c) IF THE MATERIAL HAS  $n = 8.5 \times 10^{28}$  free electrons/ $\text{m}^3$  FIND DRIFT VELOCITY.


$$J = nev_d \Rightarrow v_d = \frac{J}{ne} = \frac{1.19 \times 10^7 \text{ A/m}^2}{(8.5 \times 10^{28} \text{ m}^{-3})(1.6 \times 10^{-19} \text{ C})}$$

$$\Rightarrow v_d = 8.75 \times 10^{-4} \text{ m/s} = 0.875 \text{ mm/s}$$

$$\text{UNIT: } \frac{\text{A}}{\text{m}^2} \frac{\text{m}^3}{\text{C}} = \frac{\text{C} \cdot \text{m}}{\text{s} \cdot \text{C}} = \frac{\text{m}}{\text{s}} = \text{m/s}$$

↑  
EVEN FOR VERY LARGE CURRENT, THE DRIFT VELOCITY IS SMALL

#2

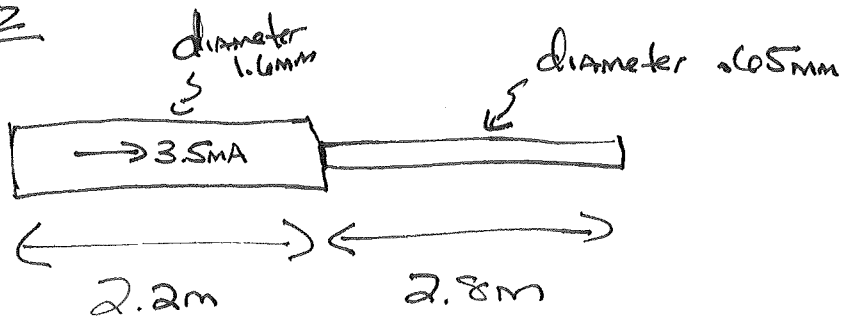

Let Larger Section be #1:

$$I_1 = 3.5 \text{ mA}$$

$$d_1 = 1.6 \text{ mm}, L_1 = 2.2 \text{ m}$$

Smaller Section is #2:

$$I_2 = ?, d_2 = .65 \text{ mm}, L_2 = 2.8 \text{ m}$$

a) WHAT IS  $I_2$ ? EVERY CHARGE THAT LEAVES ~~#2~~ <sup>#1</sup> MUST GO INTO #2 (OR VICE-VERSA)  $\Rightarrow$  #1 AND #2 ARE CONNECTED IN SERIES  $\Rightarrow I_2 = I_1 = 3.5 \text{ mA}$

b) WHAT IS  $E_1$ ?  $E = \rho J$ . Copper at  $20^\circ\text{C}$  has  $\rho = 1.72 \times 10^{-8} \Omega \cdot \text{m}$

$$\Rightarrow E_1 = \rho J_1 = (1.72 \times 10^{-8} \Omega \cdot \text{m}) J_1 = (1.72 \times 10^{-8} \Omega \cdot \text{m}) \frac{I_1}{A_1} \quad A_1 = \pi r_1^2$$
$$r_1 = \frac{1.6 \text{ mm}}{2} = .8 \text{ mm}$$

$$\Rightarrow E_1 = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(3.5 \times 10^{-3} \text{ A})}{\pi (.8 \times 10^{-3} \text{ m})^2}$$

$$\text{Unit: } \frac{\Omega \cdot \text{A}}{\text{m}} = \frac{\text{V/A} \cdot \text{A}}{\text{m}} = \text{V/m}$$


$$\Rightarrow E_1 = 2.99 \times 10^{-5} \text{ V/m}$$

c) WHAT IS  $E_2$ ?  $E_2 = \rho J_2 = \rho \frac{I_2}{A_2}$

$$A_2 = \pi r_2^2 \quad r_2 = \frac{.65 \text{ mm}}{2} = .325 \text{ mm}$$

$$\Rightarrow E_2 = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(3.5 \times 10^{-3} \text{ A})}{\pi (.325 \times 10^{-3} \text{ m})^2} \Rightarrow E_2 = 1.81 \times 10^{-4} \text{ V/m}$$

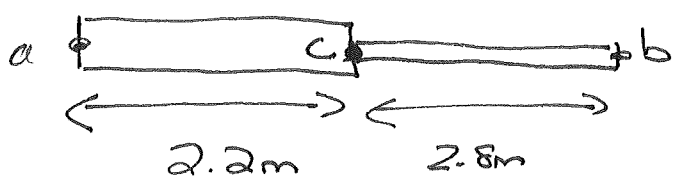d) WHAT IS THE POTENTIAL DIFFERENCE BETWEEN THE ENDS?



$$V_{ab} = ?$$

Let CONNECTION POINT be C

$$V_{ac} = V_a - V_c, \quad V_{cb} = V_c - V_b$$

$$\Rightarrow V_{ac} + V_{cb} = V_a - V_c + V_c - V_b = V_a - V_b = V_{ab}$$



Assuming UNIFORM  $E_1$  AND  $E_2 \Rightarrow V_{ac} = E_1 L_1, \quad V_{cb} = E_2 L_2$

$$\Rightarrow V_{ac} = (2.99 \times 10^{-5} \text{ V/m})(2.2\text{m}) = 6.578 \times 10^{-5} \text{ V}$$

$$V_{cb} = (1.81 \times 10^{-4} \text{ V/m})(2.8\text{m}) = 5.068 \times 10^{-4} \text{ V}$$

$$\Rightarrow V_{ab} = 5.7258 \times 10^{-4} \text{ V} = .57258 \text{ mV} = .573 \text{ mV}$$

#3

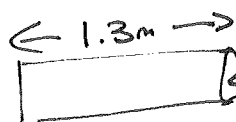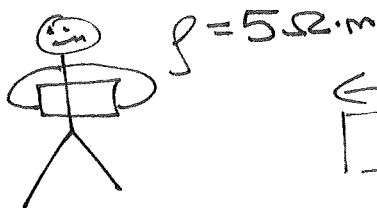

diameter 0.16m  $\Rightarrow$   
radius,  $r = .08m$

a) WHAT IS RESISTANCE?  $R = \rho \frac{L}{A} = \frac{\rho L}{\pi r^2} = \frac{5.52 \cdot 10^{-8} (1.3m)}{\pi (.08m)^2}$

$\Rightarrow \boxed{R = 323 \Omega}$


b)  $V = ?$  to produce  $I = 100mA = .1A$

$V = IR \Rightarrow \boxed{V = (.1A)(323\Omega) = 32.3V}$

$\hookrightarrow$  Much less  
than the  
120V most appliances  
run on

c)  $P = IV = (.1A)(32.3V) \Rightarrow \boxed{P = 3.23 \text{ watt}}$

thy

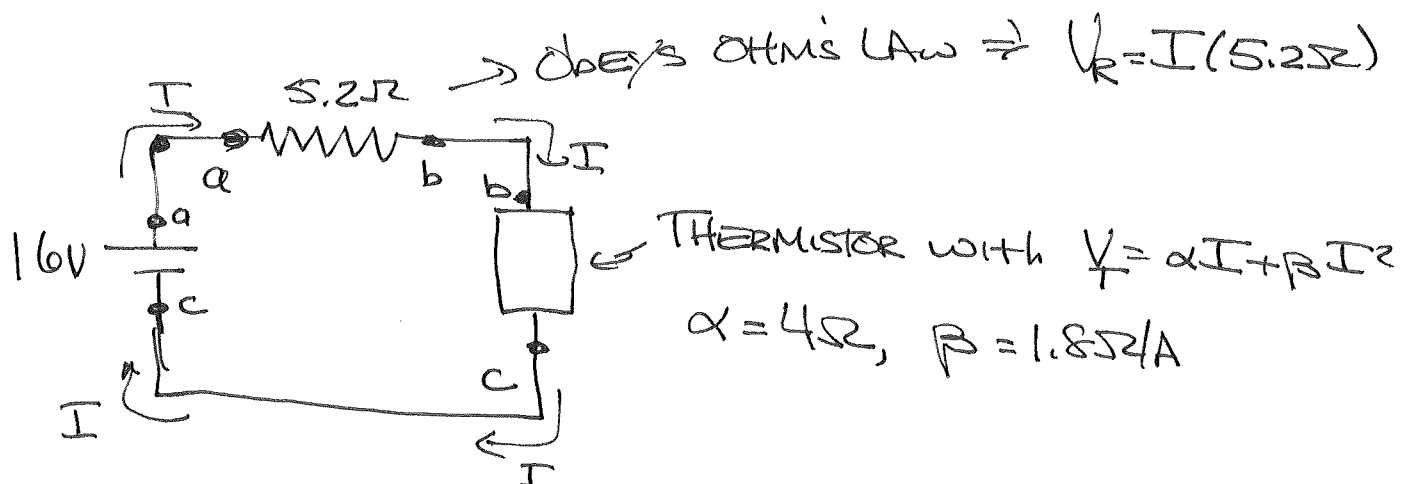

Label points (a), (b), (c) As Above

$$\Rightarrow V_{ac} = V_a - V_c = 16V$$

$$V_{ab} = V_a - V_b = V_R$$

$$V_{bc} = V_b - V_c = V_T$$

$$\Rightarrow V_{ab} + V_{bc} = V_{ac}$$

$$\Rightarrow V_R + V_T = 16V$$

$$\therefore I(5.2\Omega) + (4\Omega)I + (1.8\Omega/A)I^2 = 16V$$


$$\Rightarrow (1.8\Omega/A)I^2 + (9.2\Omega)I - 16V = 0 \leftarrow \text{QUADRATIC EQN.}$$

$$\Rightarrow I = \frac{-9.2\Omega \pm \sqrt{(9.2\Omega)^2 - 4(1.8\Omega/A)(-16V)}}{2(1.8\Omega/A)} = \frac{-9.2\Omega \pm \sqrt{199.84\Omega^2}}{3.6\Omega/A}$$

$$\Rightarrow I = 1.37A \text{ or } -6.48A \Rightarrow \boxed{I = 1.37A}$$

$\nearrow$   
No


#5

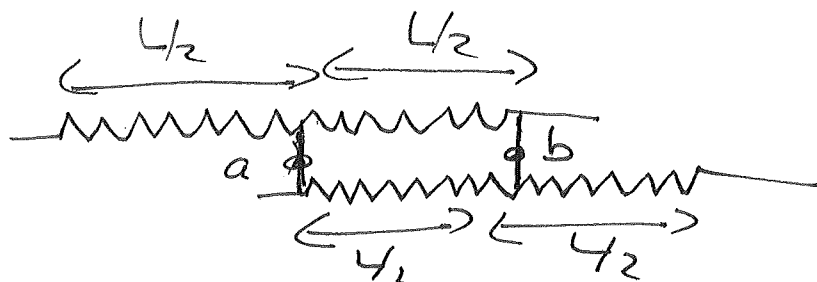

Soldered  $\Rightarrow$  Connected  
by Metal = Equipotential  
SURFACE

Label a, b  $\Rightarrow$  HALF OF TOP Resistor AND HALF OF bottom  
Resistor at  $V_{ab} \Rightarrow$  IN parallel WITH EACH OTHER
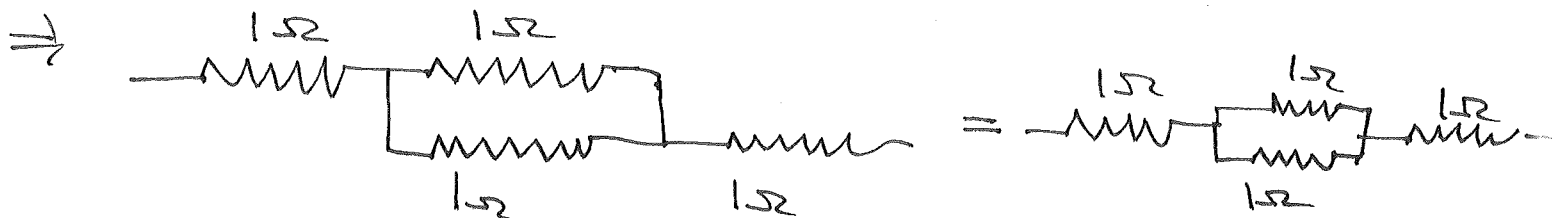
$$R = \frac{\rho L}{A} \Rightarrow \frac{1}{2} \text{ OF A } 2\Omega \text{ Resistor HAS } R = 1\Omega$$



FIND EQUIVALENT RESISTANCE. For parallel combination

$$R' = \frac{(1\Omega)(1\Omega)}{(1\Omega + 1\Omega)} = \frac{1}{2}\Omega \Rightarrow \text{1}\Omega \text{ --- } \frac{1}{2}\Omega \text{ --- } 1\Omega$$

3 RESISTORS IN SERIES  $\Rightarrow R_{EQ} = 1\Omega + \frac{1}{2}\Omega + 1\Omega$

$$\Rightarrow R_{EQ} = 2\frac{1}{2}\Omega = 2.5\Omega$$


126  
~~126~~

IF OHMMETER CONNECTED TO a+b,

WHAT WILL IT READ?

OHMMETER APPLIES VOLTAGE  $\Rightarrow$

(a)

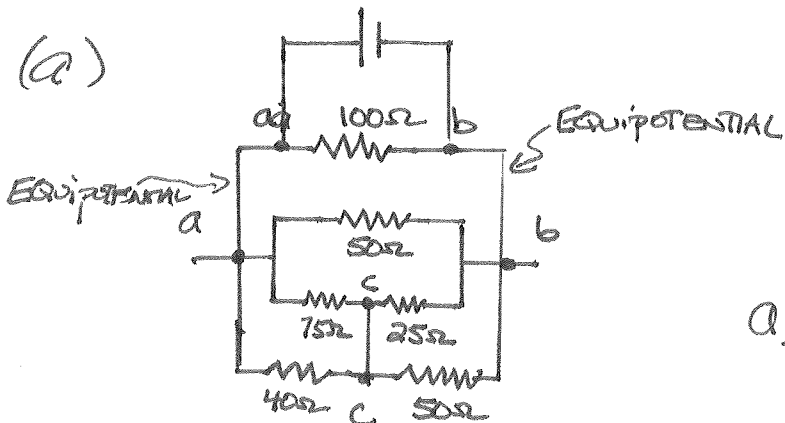


a, b  $\Rightarrow$  100Ω, UPPER 50Ω, AND  
REST IN Parallel.

a, c  $\Rightarrow$  75Ω, 40Ω in parallel

b, c  $\Rightarrow$  25Ω, 50Ω in parallel

$\Rightarrow$

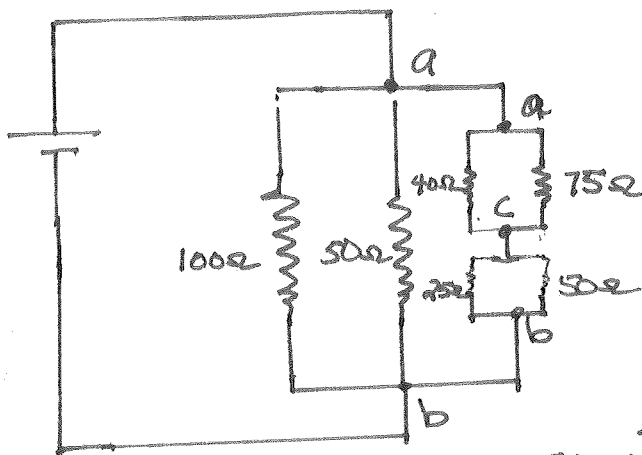


Equivalent for 40Ω, 75Ω in Parallel

$$R' = \frac{75\Omega(40\Omega)}{(75\Omega+40\Omega)} = \frac{3000}{115}\Omega = \frac{600}{23}\Omega = 26.09\Omega$$

Equivalent for 25Ω, 50Ω

$$R'' = \frac{25\Omega(50\Omega)}{(25\Omega+50\Omega)} = \frac{1250}{75}\Omega = \frac{50}{3}\Omega = 16.666\Omega$$

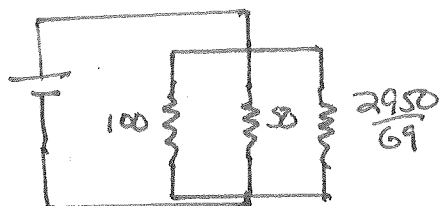
$$R' + R'' = \frac{2950}{69} = 22.753 \leftarrow R', R'' \text{ IN SERIES}$$



$$\frac{1}{R_{EQ}} = \frac{1}{100} + \frac{1}{50} + \frac{1}{2950/69} \Rightarrow R_{EQ} = 18.73\Omega$$



#7

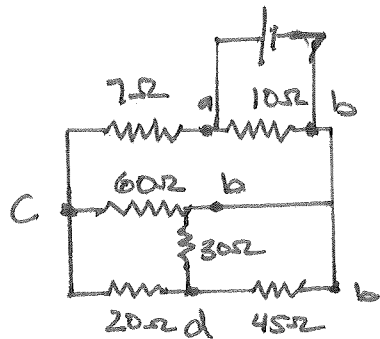

$ab \Rightarrow 10\Omega$  in parallel to everything else


$ac \Rightarrow 7\Omega$  in series with 60, 20, 30, 45 combo

$cb \Rightarrow 60\Omega$  in parallel to 20, 30, 45Ω  
COMBINATION

$db \Rightarrow 30, 45$  in parallel

$cd \Rightarrow 20$  in series with 30, 45

$\Rightarrow$

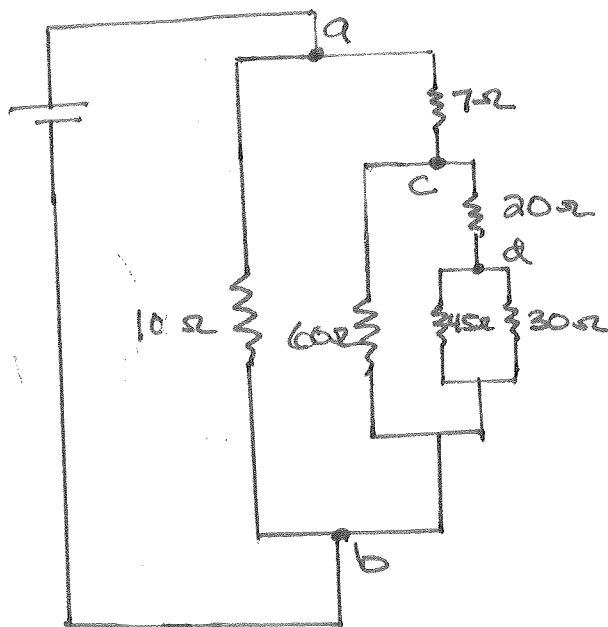

$R' = 30\Omega, 45\Omega$  in parallel


$$\Rightarrow R' = \frac{30\Omega(45\Omega)}{(30\Omega + 45\Omega)} = 18\Omega$$


$$20\Omega + 18\Omega = 38\Omega$$

$$60, 38 \text{ in parallel} \Rightarrow R'' = \frac{60\Omega(38\Omega)}{98\Omega} = \frac{1140}{49}\Omega$$

$$= 23.2653\Omega$$
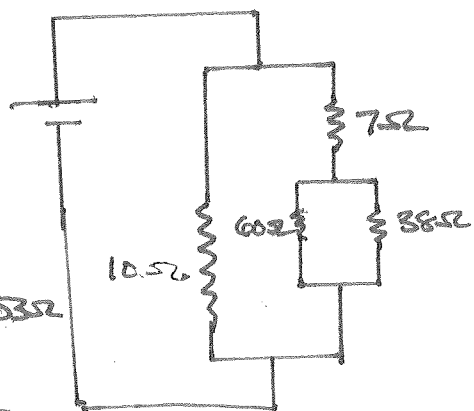
$$7\Omega \text{ in series} \Rightarrow 7 + \frac{1140}{49} = \frac{1483}{49} = 30.2653\Omega$$




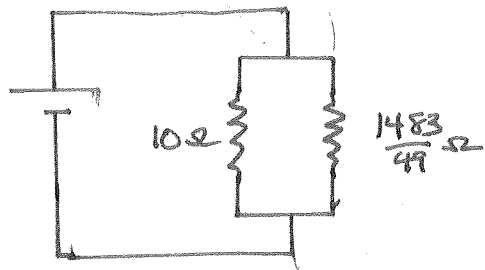


$$R_{EQ} = \frac{10\Omega \left( \frac{1483}{49}\Omega \right)}{\left[ 10\Omega + \frac{1483}{49}\Omega \right]}$$

$$\Rightarrow R_{EQ} = 7.5165 = 7.52\Omega$$

#8

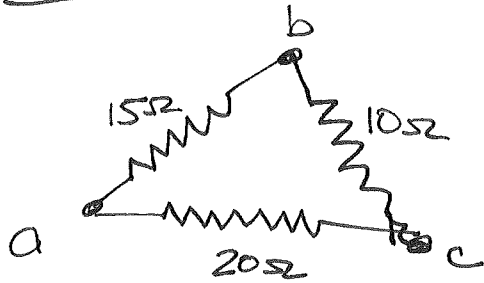


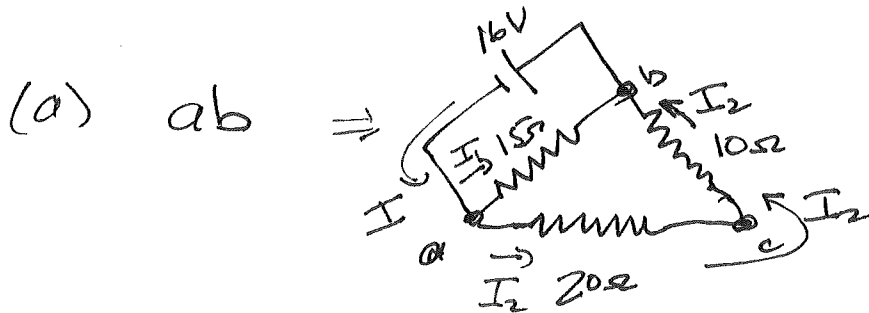
WHAT CURRENT FROM 16V battery IF  
Connected to:




Current splits at a  
 $I_1$  goes through  $15\Omega$   
then back to battery

$I_2$  goes through  $20\Omega$  then  $10\Omega$   
then back to battery

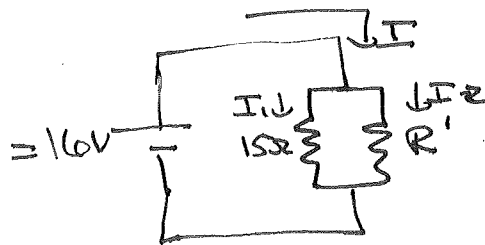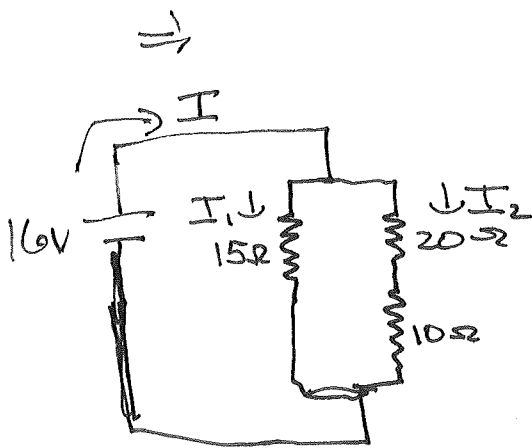$\Rightarrow 20\Omega + 10\Omega$  IN SERIES. By "Finger Test"  $15\Omega$  IN parallel  
to  $20\Omega/10\Omega$  COMBINATION




$$R' = 20\Omega + 10\Omega = 30\Omega$$

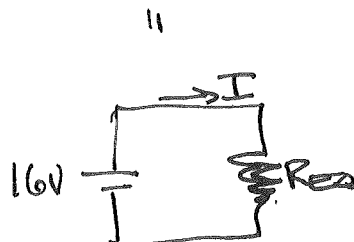

$$R_{eq} = \frac{15\Omega(30\Omega)}{15\Omega + 30\Omega} = 10\Omega$$


$$\Rightarrow I = \frac{16V}{10\Omega} = 1.6A$$

b) bc

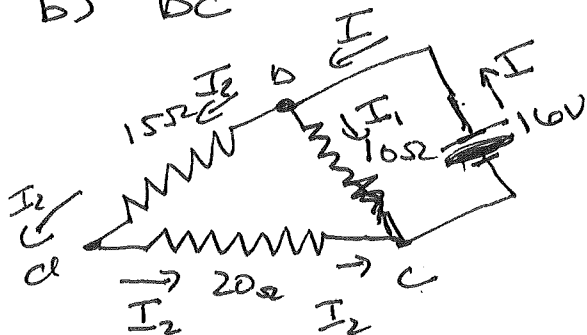

Now when Current splits,  $I_1$  goes through  $10\Omega$  then back to battery.  $I_2$  goes through  $15\Omega$  then  $20\Omega$

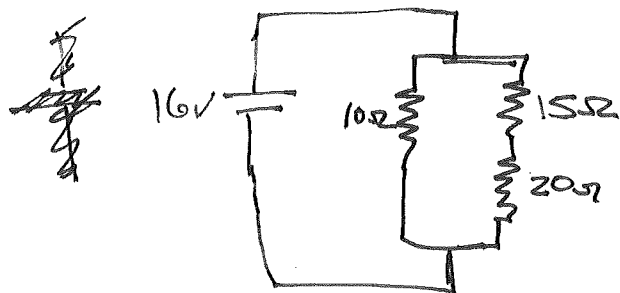
$\Rightarrow 15\Omega$  AND  $20\Omega$  IN SERIES,  $10\Omega$  IN parallel to Combination.




SAME Calculation for  $R_{eq}$  but

$$R' = 15\Omega + 20\Omega = 35\Omega$$

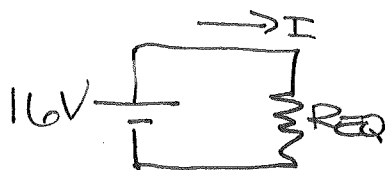
$$\Rightarrow R_{eq} = \frac{(10\Omega)(35\Omega)}{(10\Omega + 35\Omega)} = 7.77... \Omega$$



$$I = \frac{16V}{7.77\Omega} = 2.057A$$

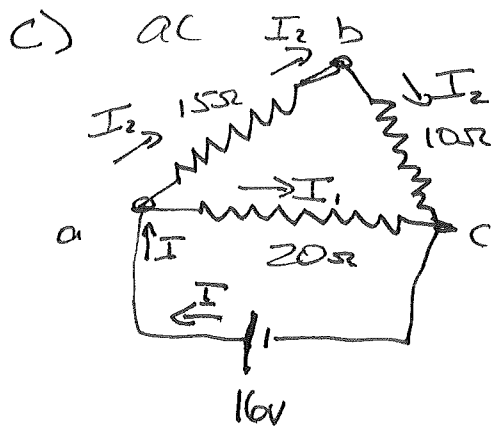

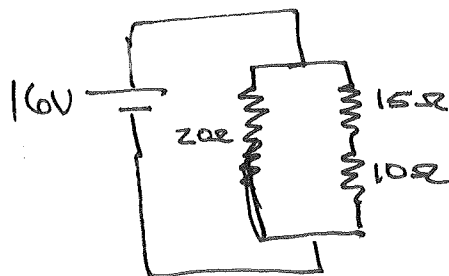~~20Ω~~  $15\Omega$  AND  $10\Omega$  IN SERIES,  $20\Omega$  IN parallel with Combination




$$R' = 15\Omega + 10\Omega = 25\Omega$$

$$R_{eq} = \frac{(20\Omega)(25\Omega)}{(20\Omega + 25\Omega)} = 11.111... \Omega$$


$$\Rightarrow I = \frac{16V}{11.111\Omega} = 1.44A$$

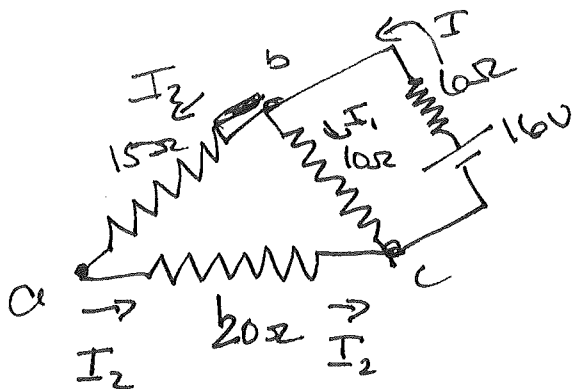d) IF battery has  $6\Omega$  OF INTERNAL Resistance  
 $\Rightarrow$  What current, if connected across bc?

Simply ADD  $6\Omega$  in series with battery.




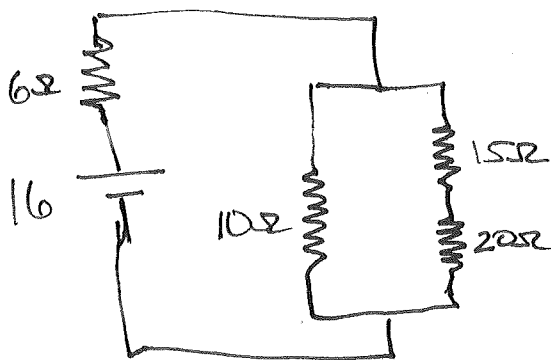Still HAVE  $15\Omega$ ,  $20\Omega$  IN Series  
 $10\Omega$  IN parallel with combination



Like before, the  $10\Omega$ ,  $15\Omega$   
 And  $20\Omega$  behave like
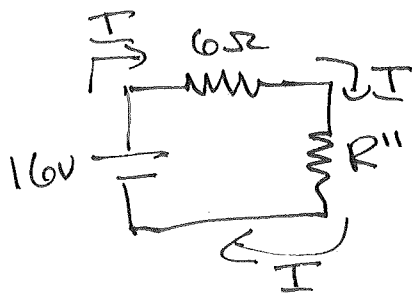
$$R'' = \frac{(10\Omega)(35\Omega)}{45\Omega} = 7.77... \Omega$$



$6\Omega$  AND  $R''$  IN series  $\Rightarrow R_{EQ} = 6\Omega + 7.77\Omega$

$$\Rightarrow R_{EQ} = 13.77\Omega$$

$$\therefore I = \frac{16V}{13.77\Omega} = 1.16129A = 1.16A$$

In Summary:

	ab	bc	ac	bc with INTERNAL R
I	1.16A	2.057A	1.44A	1.16A