

Addition & Subtraction

Addition and Subtraction



- Motivation: need to add and/or subtract values represented as binary numbers
 - Note need for identification of coding method: unsigned binary, two's complement, fixed point, floating point, excess code, ...
 - Scheme should be extensible; that is, once method identified, should be able to apply method with varying numbers of bits

Adding Two 8-bit Numbers

$$\begin{array}{r} 1\ 1\ 1\ 0\ 1\ 1\ 1\ 0 \\ 0\ 0\ 1\ 0\ 0\ 0\ 1\ 0 \\ \hline 0\ 0\ 0\ 1\ 0\ 0\ 0\ 0 \end{array}$$

Adding Two 8-bit Numbers
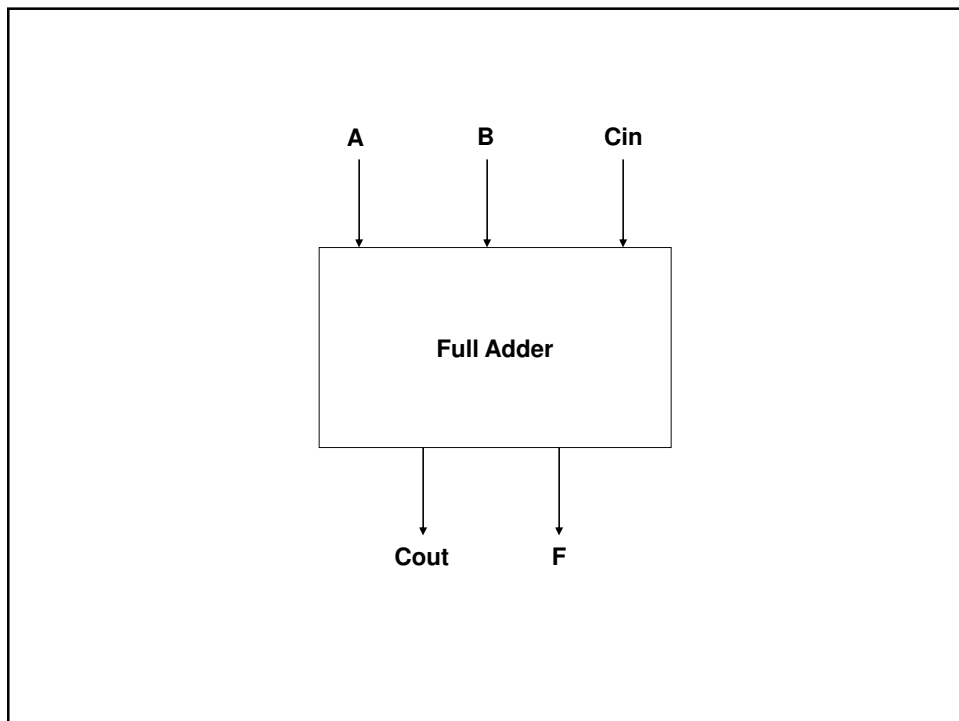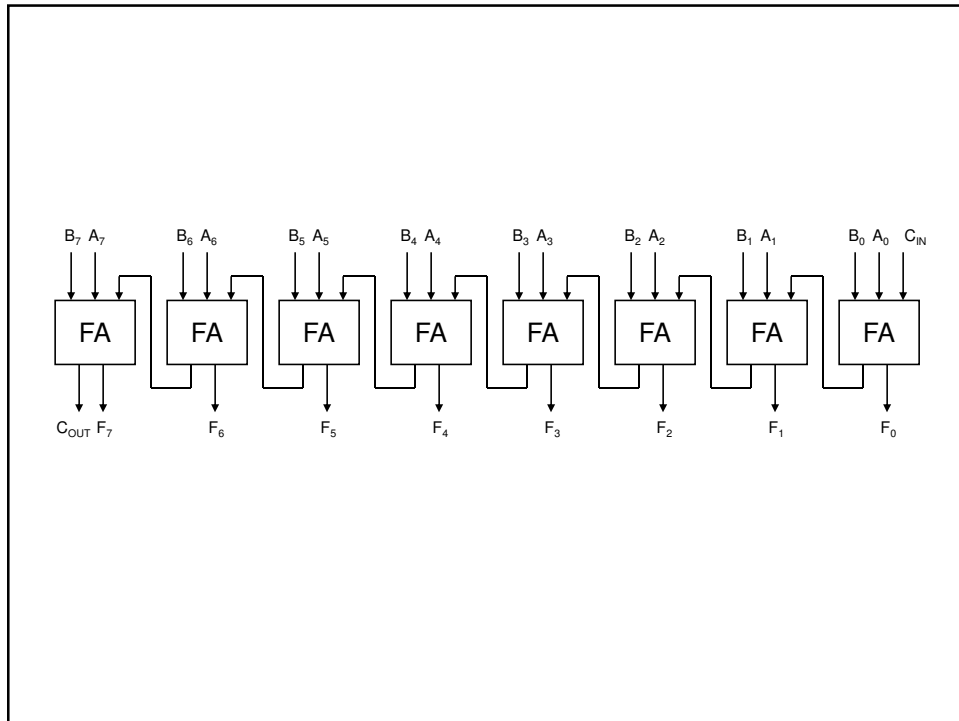
$$\begin{array}{r} \overset{1}{1}\ \overset{1}{1}\ \overset{1}{1}\ \overset{0}{1}\ \overset{0}{0}\ \overset{1}{1}\ \overset{1}{1}\ \overset{1}{1}\ \overset{0}{1}\ \overset{0}{0} \\ 0\ 0\ 1\ 0\ 0\ 0\ 1\ 0 \\ \hline 0\ 0\ 0\ 1\ 0\ 0\ 0\ 0 \end{array}$$



Full Adder Truth Table

A	B	Cin	Cout	F
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

K-Map for Three Variables

			A	
	x	x	x	x
Cin	x	x	x	x
	B			


K-Map Construction

not A		A	
not B	B		not B
not Cin			
Cin			


Full Adder – K-Map for F

		A	
		0	1
Cin	0	0	1
	1	1	0
		B	

Full Adder – Kmap for F

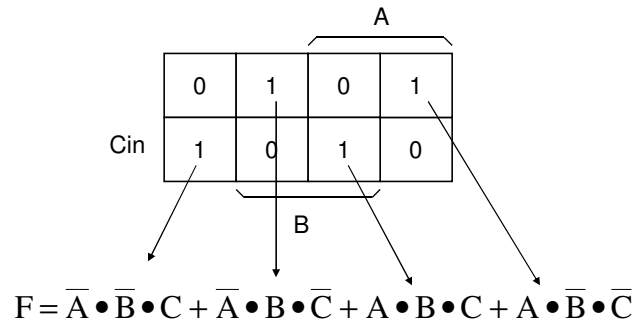

Full Adder – K-Map for Cout

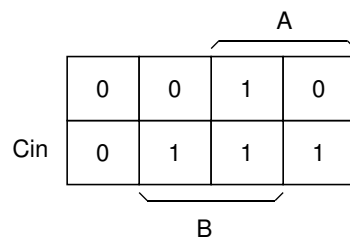


Full Adder – K-Map for Cout

	A			
	0	0	1	0
Cin	0	1	1	1
	B			

Full Adder – K-Map for Cout

	A			
	0	0	1	0
Cin	0	1	1	1
	B			
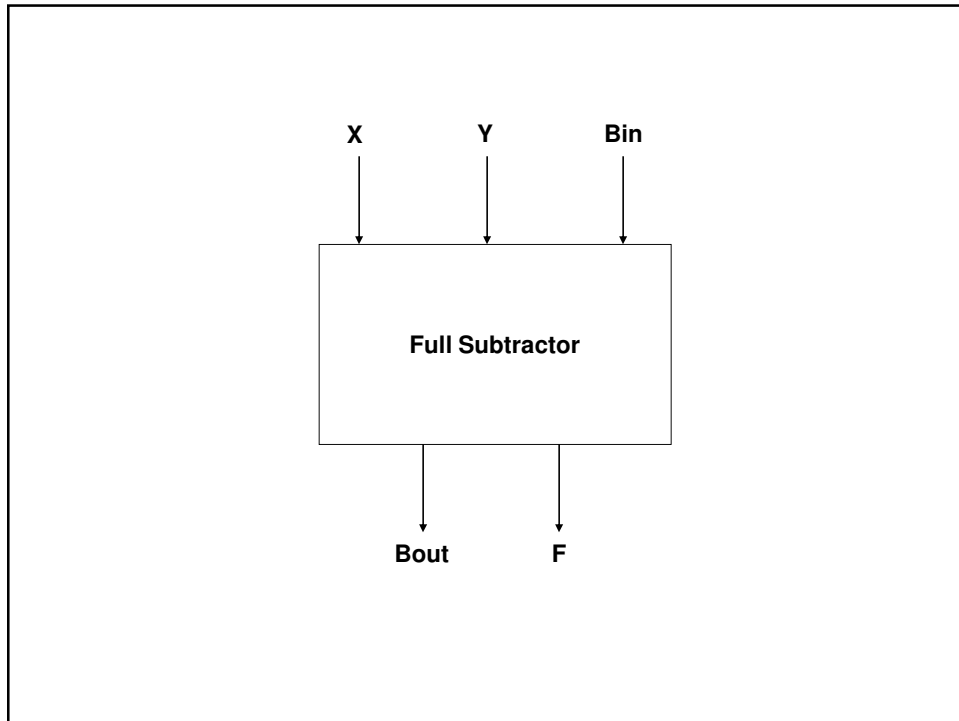
$$\text{Cout} = B \bullet C + A \bullet B + A \bullet C$$



Full Subtractor Truth Table				
X	Y	Bin	Bout	F
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Full Subtractor Truth Table

X	Y	Bin	Bout	F
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Full Subtractor – K-Map for F

	X			
	0	1	0	1
Bin	1	0	1	0
	Y			

$$F = \bar{X} \cdot \bar{Y} \cdot B + \bar{X} \cdot Y \cdot \bar{B} + X \cdot Y \cdot B + X \cdot \bar{Y} \cdot \bar{B}$$


Full Subtractor – K-Map for Bout

		X	
		0	0
Bin	0	0	1
	1	1	0
		Y	

Full Subtractor – K-Map for Bout


		X	
		0	0
Bin	0	1	0
	1	1	0
		Y	
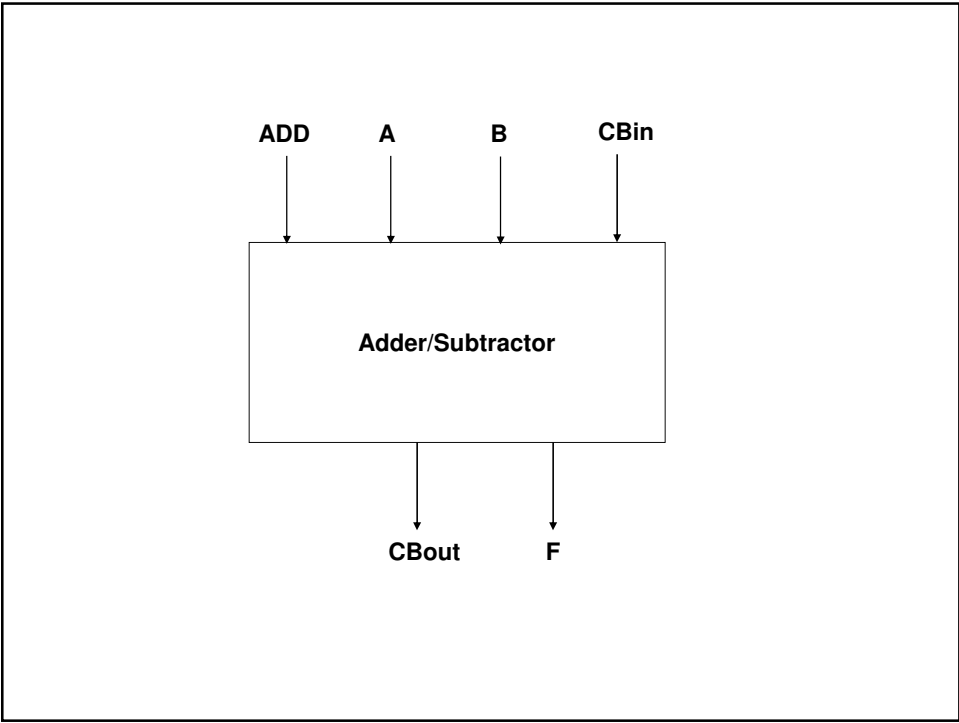
$$\text{Bout} = \overline{X} \bullet B + \overline{X} \bullet Y + Y \bullet B$$




ADD	A	B	CBin	Cbout	F
0	0	0	0	0	0
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	1	0
0	1	0	0	0	1
0	1	0	1	0	0
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	0	0
1	0	0	1	0	1
1	0	1	0	0	1
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	1	1

K-Map For Four Variables

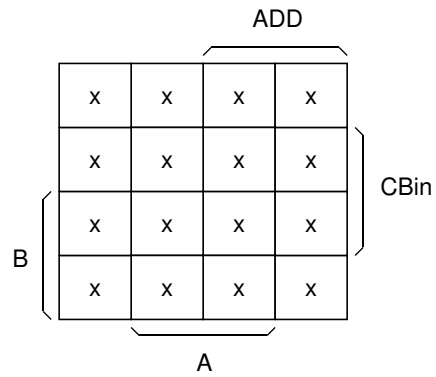

K-Map Construction (4 bits)

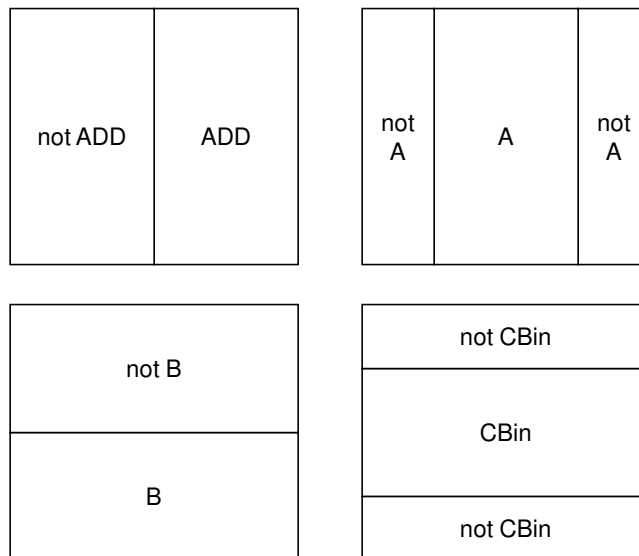

K-Map For F


ADD			
0	1	1	0
1	0	0	1
0	1	1	0
1	0	0	1

A

B

CBin

K-Map For F

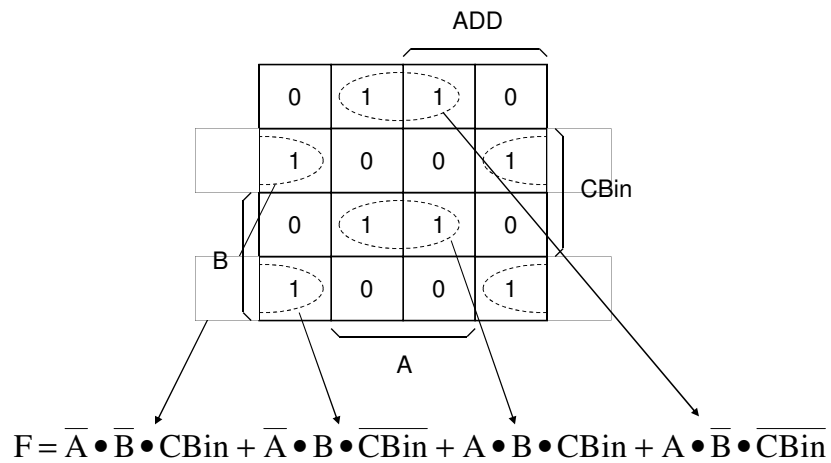

K-Map For CBout

ADD			
0	0	0	0
1	0	1	0
1	1	1	1
1	0	1	0
A			

B

CBin

K-Map For CBout



ADD			
0	0	0	0
1	0	1	0
1	1	1	1
1	0	1	0
A			



B



CBin



$$CBout = \overline{ADD} \cdot \overline{A} \cdot CBin + \overline{ADD} \cdot \overline{A} \cdot B + ADD \cdot A \cdot CBin + ADD \cdot A \cdot B + B \cdot CBin$$


Timing for Ripple Carry Adder

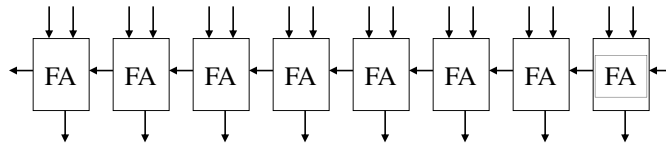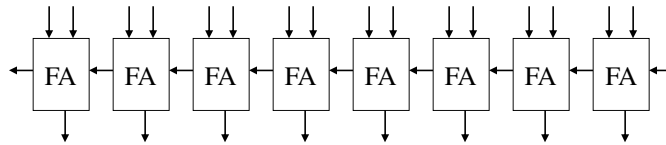

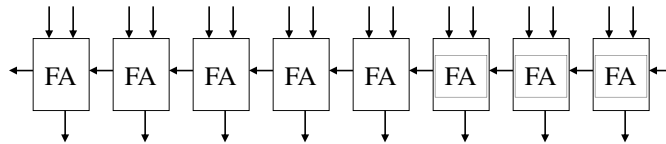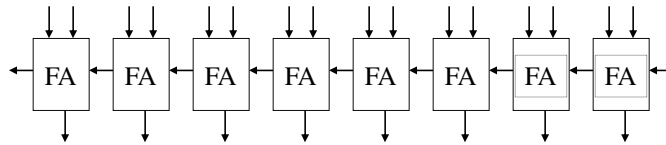


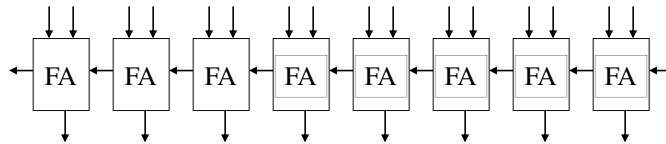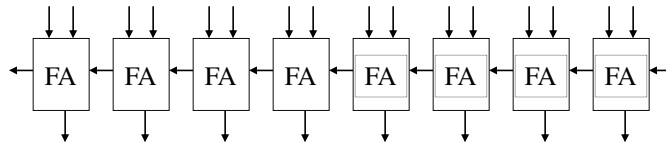

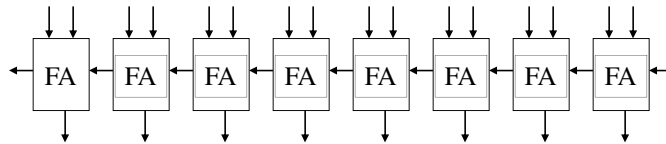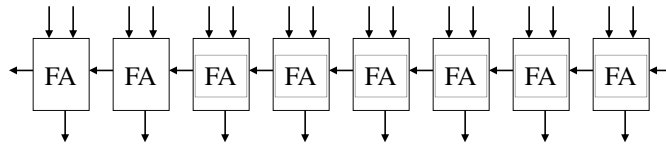

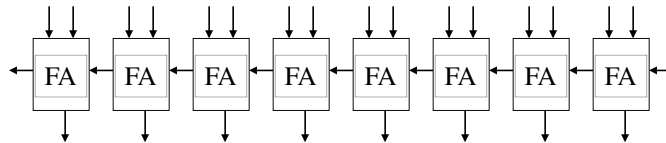

Look Ahead System (2 Bits)

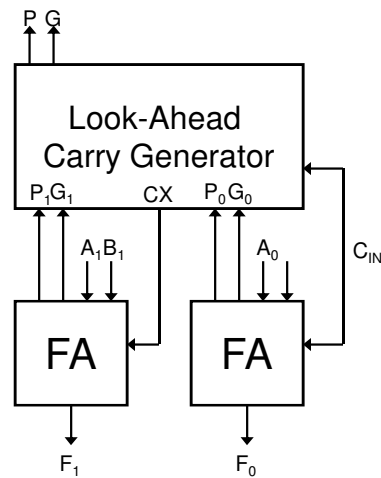

Look Ahead System (2 Bit)


$$CX = G_0 + P_0 C_{IN}$$



$$\begin{aligned} CY &= G_1 + P_1 CX \\ &= G_1 + P_1 G_0 + P_1 P_0 C_{IN} \end{aligned}$$



$$\text{Generate} = G_1 + P_1 G_0$$



$$\text{Propagate} = P_1 P_0$$


Look Ahead Method

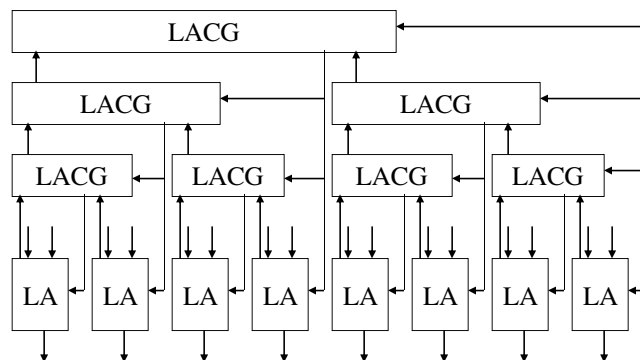

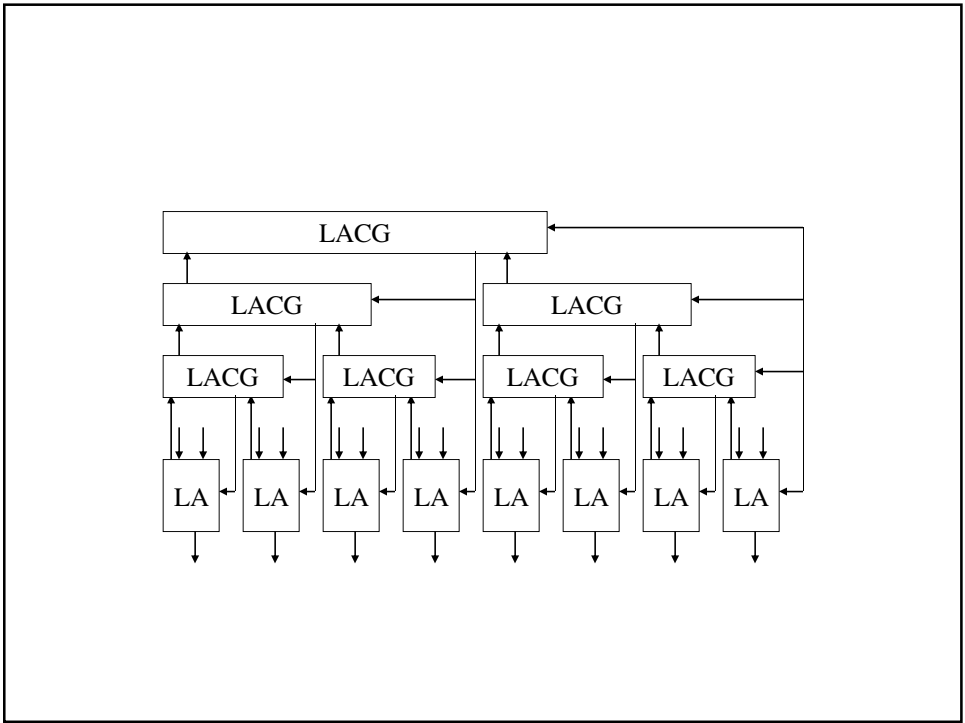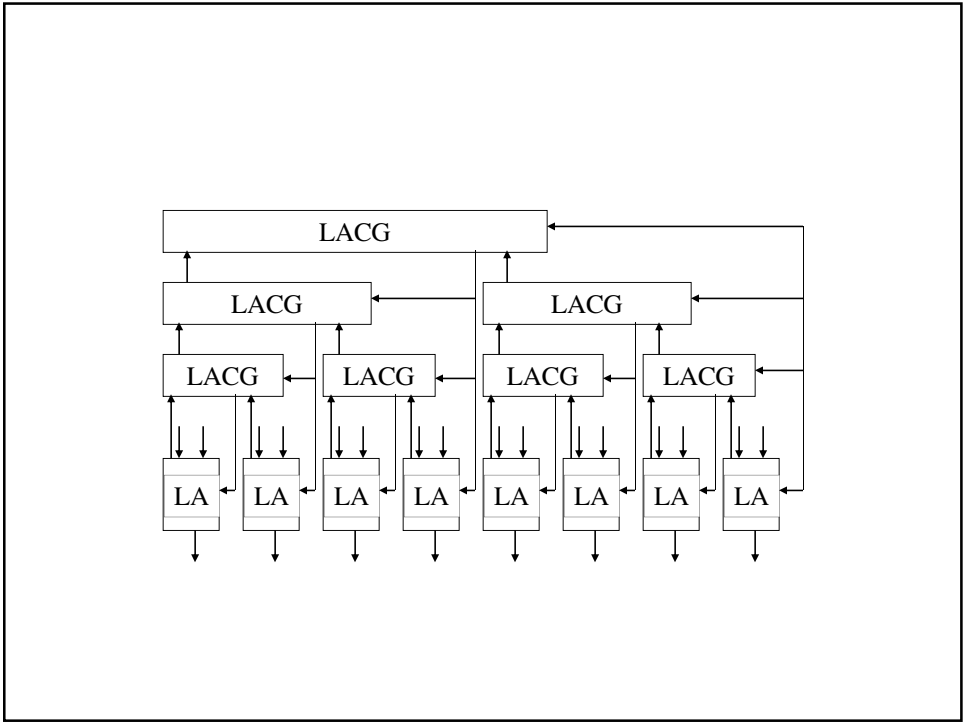


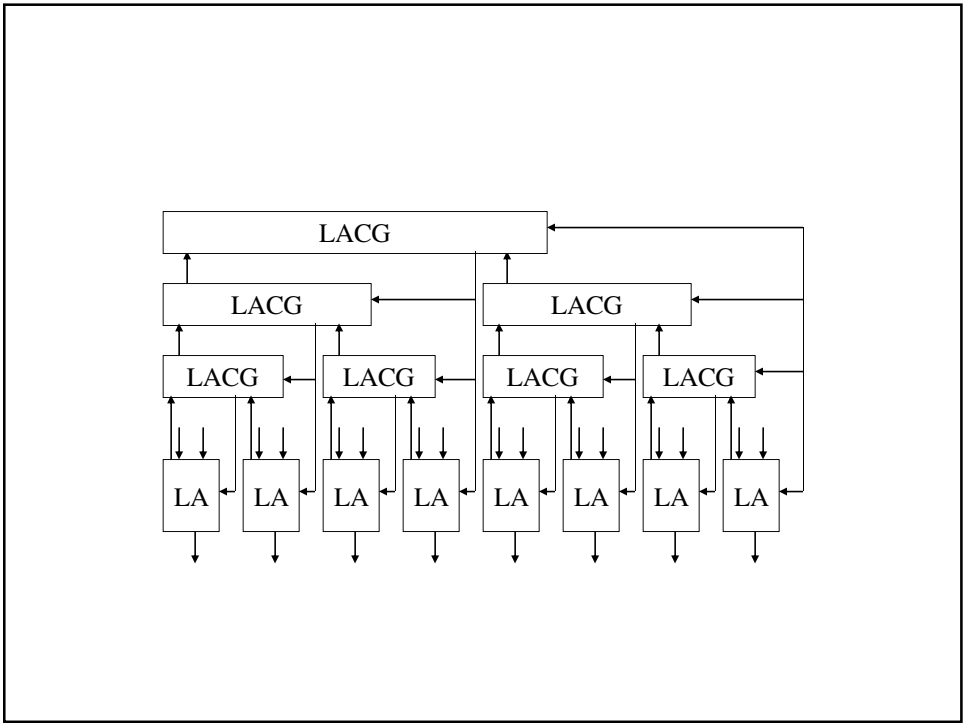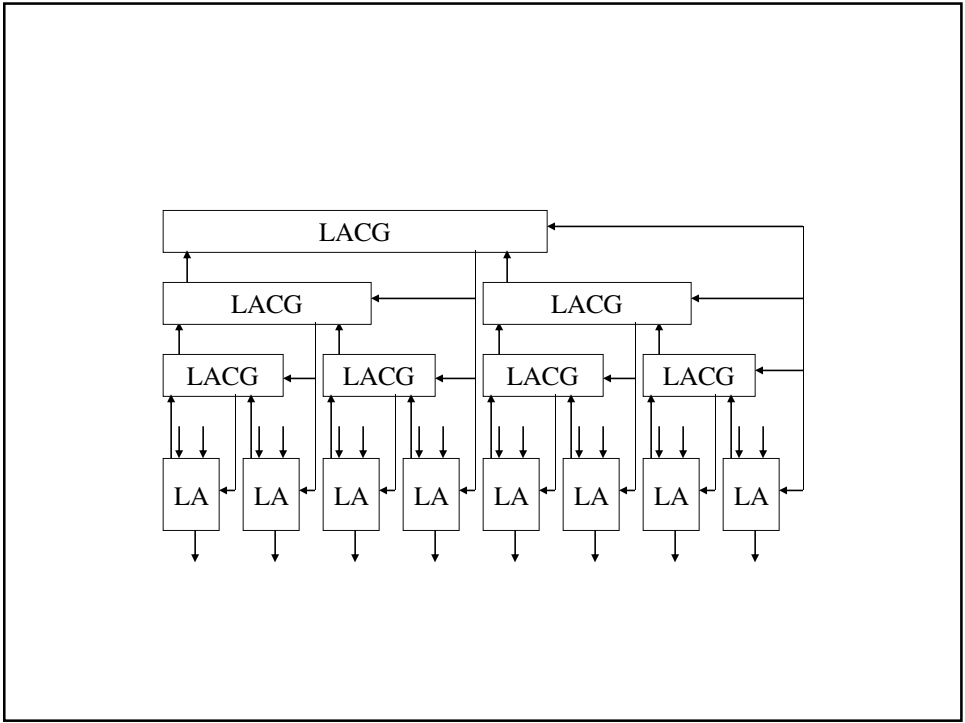

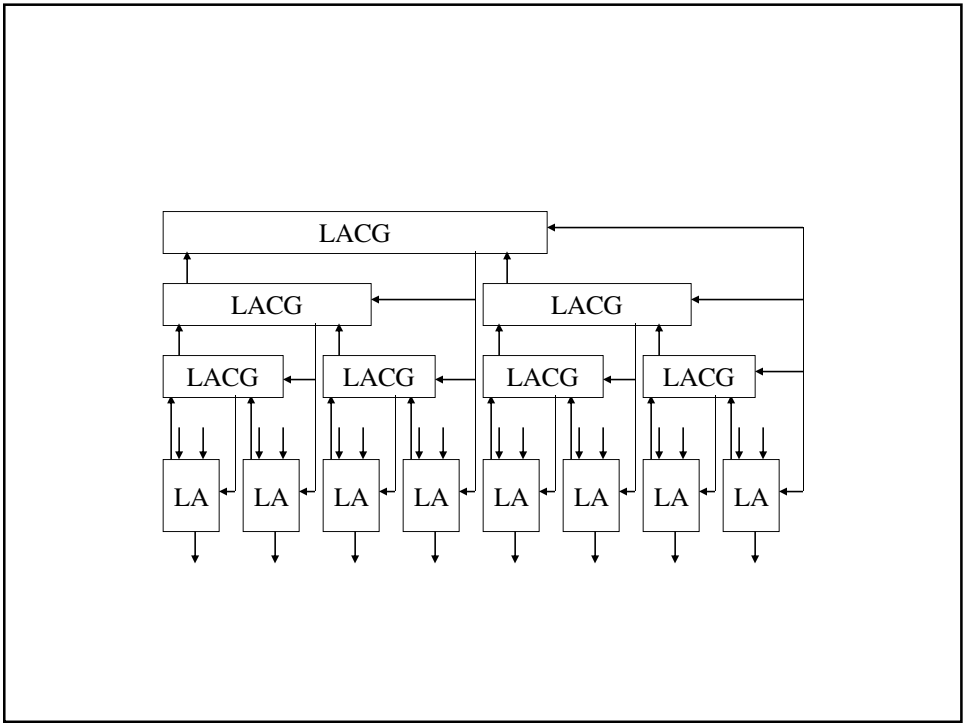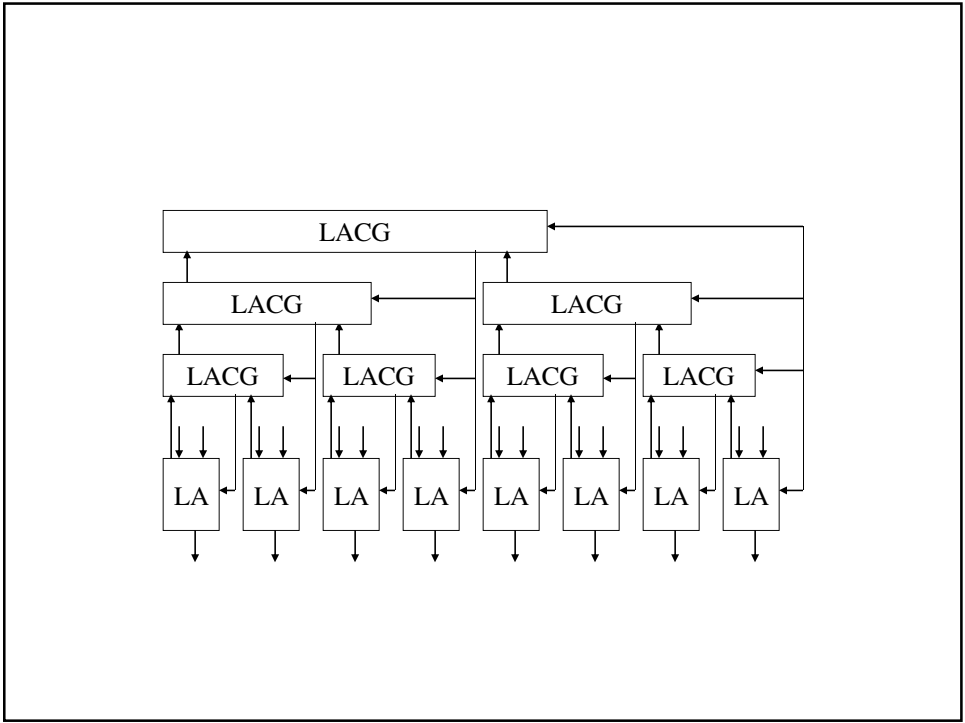

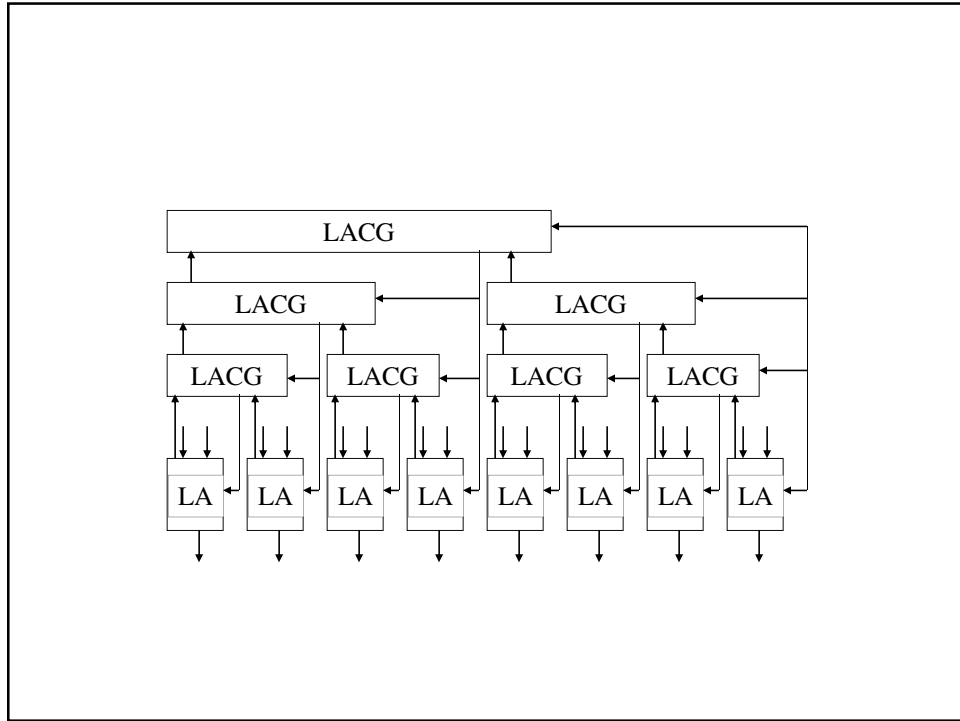

Look Ahead System

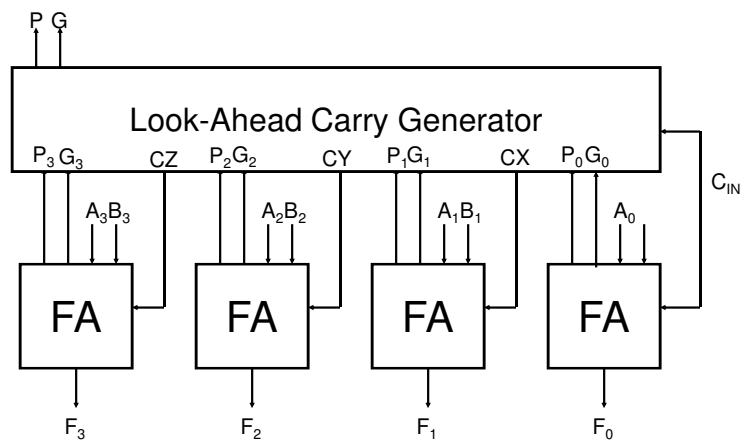

Look Ahead System

$$CX = G_0 + P_0 C_{IN}$$

$$\begin{aligned} CY &= G_1 + P_1 CX \\ &= G_1 + P_1 G_0 + P_1 P_0 C_{IN} \end{aligned}$$

$$\begin{aligned} CZ &= G_2 + P_2 CY \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{IN} \end{aligned}$$

Look Ahead System

$$\begin{aligned} C_{NEXT} &= G_3 + P_3 CZ \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + \\ &\quad P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_{IN} \end{aligned}$$

$$\begin{aligned} G_{OUT} &= G_3 + P_3 G_2 + P_3 P_2 G_1 + \\ &\quad P_3 P_2 P_1 G_0 \end{aligned}$$

$$P_{OUT} = P_3 P_2 P_1 P_0$$

Look-Ahead, 4 bits wide...

