

Lecture 38


(Phasors & Alternating Current)

Physics 161-01 Spring 2012

Douglas Fields



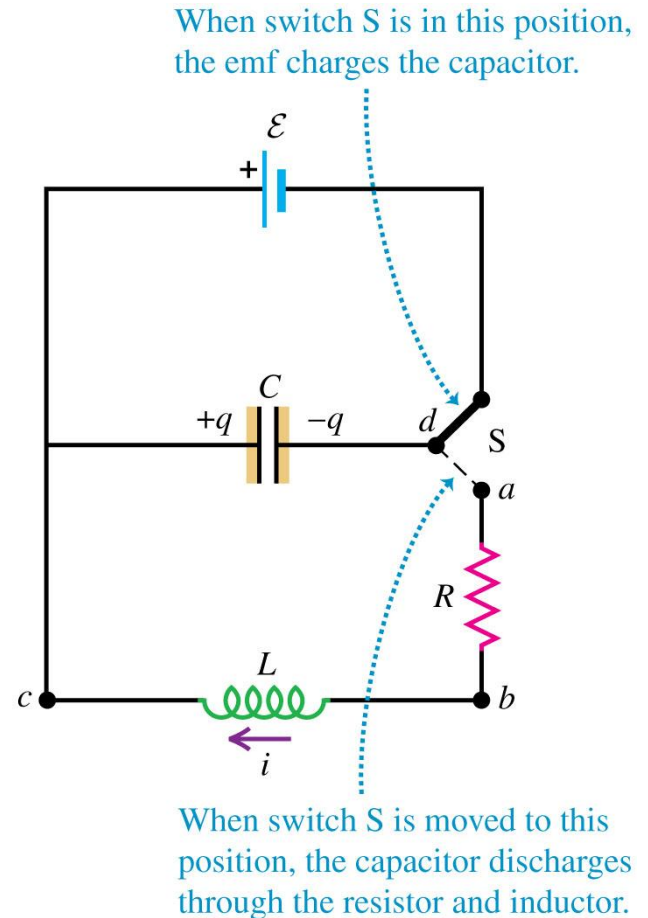- Until now, we have dealt with circuits where the source of EMF (e.g., the battery) has a constant value.
- This is known as a direct current (DC) source.
- For many reasons however, much of the world's power is not delivered as a uni-directional EMF.





Alternating EMF

- So, now we want to examine how the circuit elements we have behave when they are driven with an alternating current (AC) source.
- An AC source supplies an EMF which follows a cosine dependency:

$$v(t) = V_{max} \cos(\omega t)$$

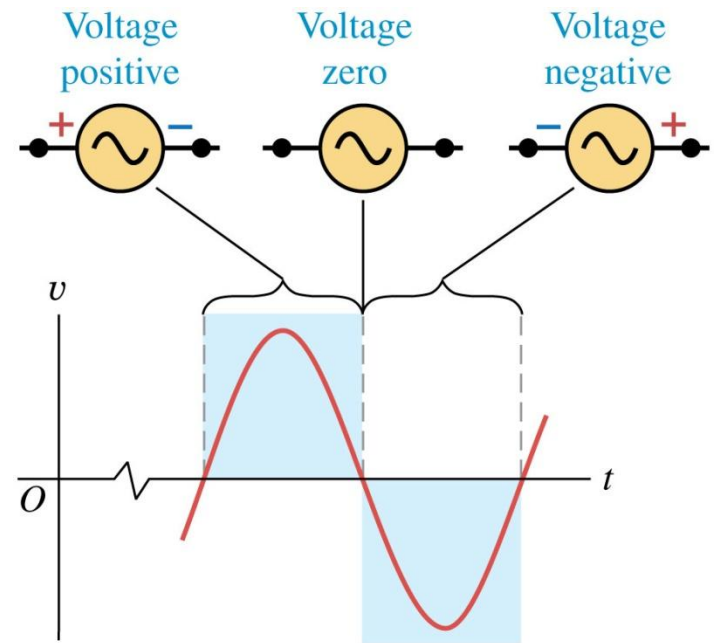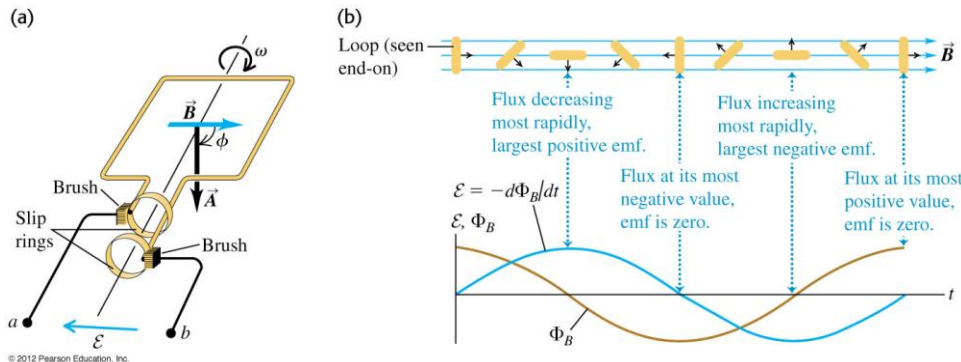- Is this a random choice?
- No, remember what you get naturally from a generator?



Phasors




Phasors

- If we have some quantity that depends sinusoidally on time,

$$\begin{aligned} i(t) &= I_{max} \cos(\omega t) \\ &= I \cos(\omega t) \end{aligned}$$


we can represent that as a vector of length I , which rotates around the origin with an angular velocity ω .

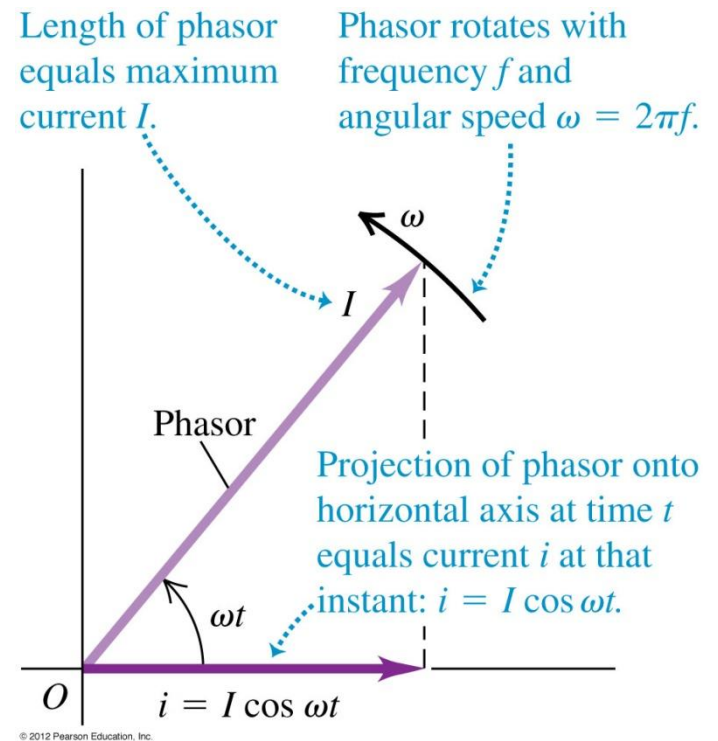- $i(t)$ is now represented by the projection of the phasor onto the horizontal axis.




Phasors

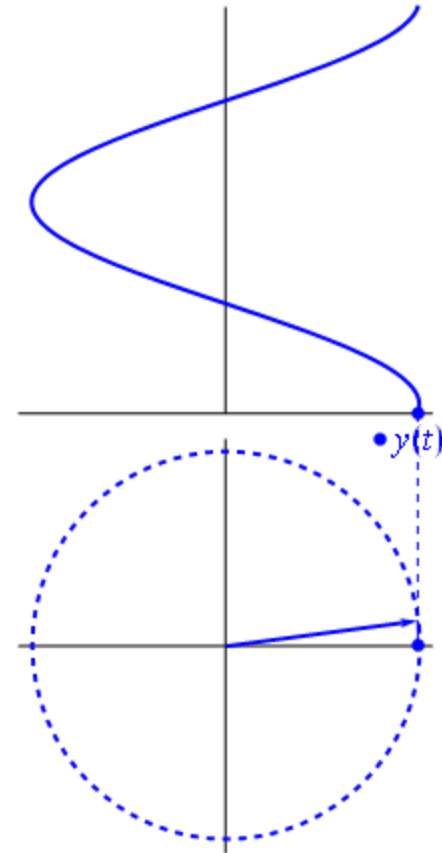- Here is a nice representation of a moving phasor.
- You can find this at:
<http://en.wikipedia.org/wiki/Phasor>
- You may be wondering:
“How is this useful?”
- Hopefully, by the end of today’s lecture, you will see.




AC Circuits With a Resistor

(a) Circuit with ac source and resistor

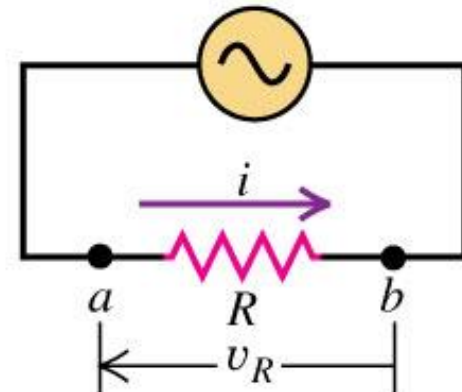

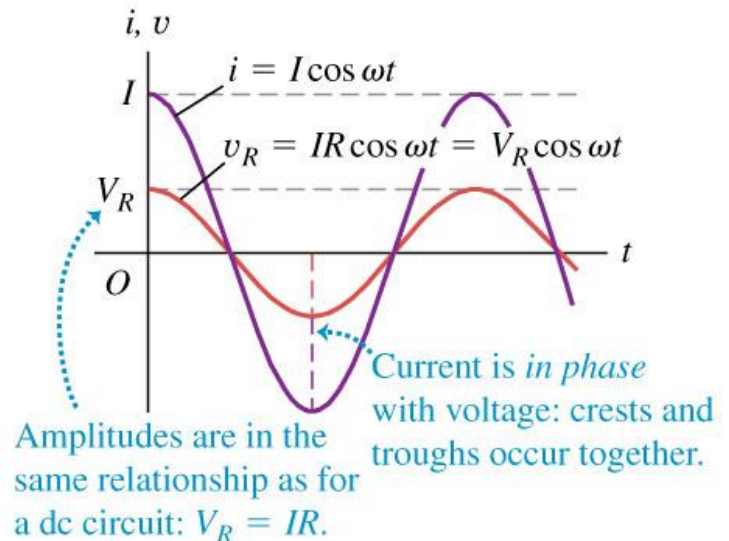(b) Graphs of current and voltage versus time




- Now, let's re-look at all of our circuit elements, now with an AC source.
- If we put a resistor in series with an AC source, the current through the resistor will just be given by Ohm's Law:

$$v_R = iR \Rightarrow$$


$$v_R = IR \cos(\omega t)$$

AC Circuits With a Resistor

(a) Circuit with ac source and resistor

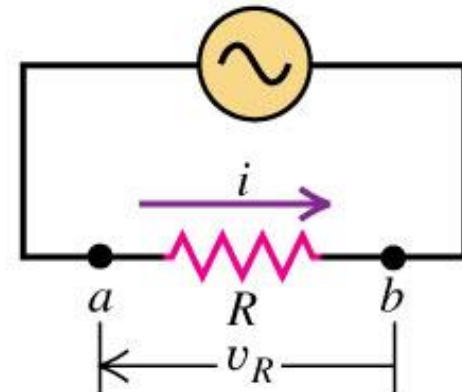

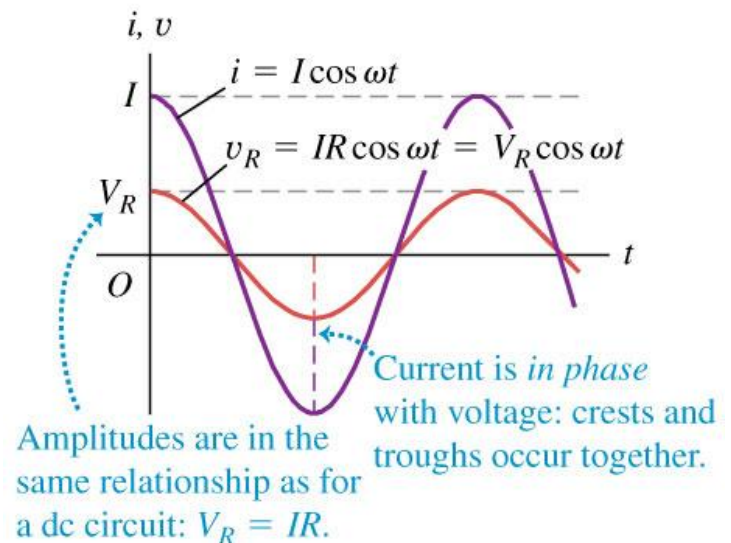(b) Graphs of current and voltage versus time



- So we can represent the voltage across the resistor as a phasor, which *is in phase with* current phasor.

$$v_R = IR \cos(\omega t)$$


AC Circuits With a Resistor

(b) Graphs of current and voltage versus time


- Notice that the magnitude of the phasor gives its maximum value, and we can write that maximum value as:

$$v_R = IR \cos(\omega t) = V_R \cos(\omega t)$$

$$V_R = IR$$

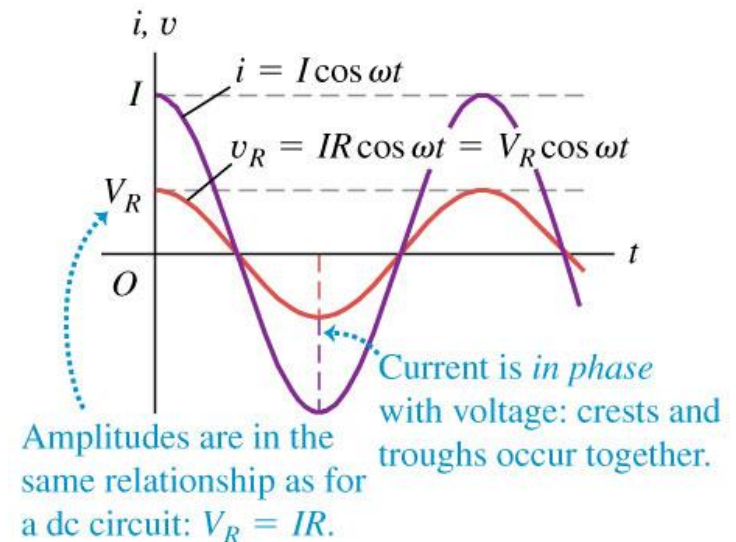


« (c) Phasor diagram

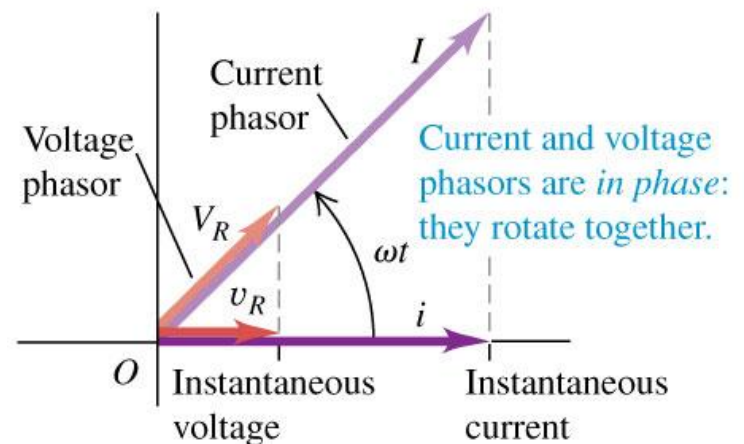

CPS 38-1

A resistor is connected across an ac source as shown. For this circuit, what is the relationship between the instantaneous current i through the resistor and the instantaneous voltage v_{ab} across the resistor?

(a) Circuit with ac source and resistor

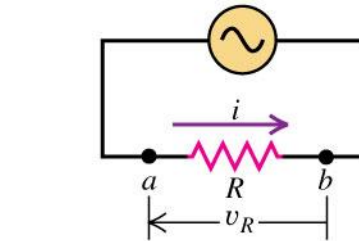


© 2012 Pearson Education, Inc.

- A. i is maximum at the same time as v_{ab} .
- B. i is maximum one-quarter cycle before v_{ab} .
- C. i is maximum one-quarter cycle after v_{ab} .
- D. not enough information given to decide

CPS 38-1

A resistor is connected across an ac source as shown. For this circuit, what is the relationship between the instantaneous current i through the resistor and the instantaneous voltage v_{ab} across the resistor?

(a) Circuit with ac source and resistor

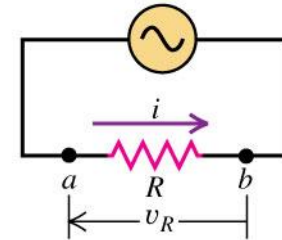

© 2012 Pearson Education, Inc.



- A. i is maximum at the same time as v_{ab} .
- B. i is maximum one-quarter cycle before v_{ab} .
- C. i is maximum one-quarter cycle after v_{ab} .
- D. not enough information given to decide


AC Circuits With an Inductor

- Now, let's look at what an inductor looks like when connected to an AC source.

$$v_L = L \frac{di}{dt} = L \frac{d}{dt} (I \cos(\omega t)) = -I \omega L \sin(\omega t) \\ = I \omega L \cos(\omega t + 90^\circ)$$


- So, the voltage across the inductor is out of phase with the current source...

(a) Circuit with ac source and inductor

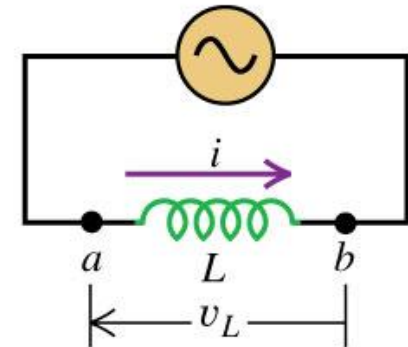

© 2012 Pearson Education, Inc.

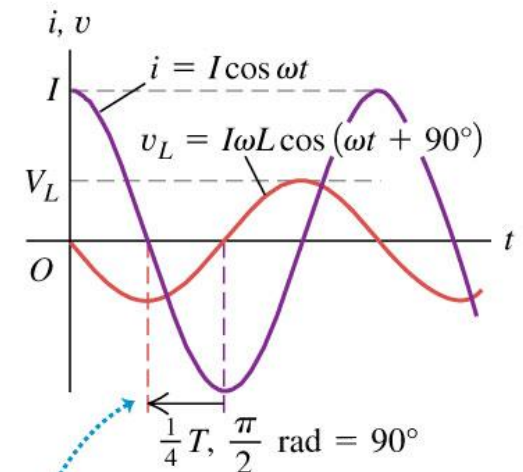(b) Graphs of current and voltage versus time



Voltage curve *leads* current curve by a quarter-cycle (corresponding to $\phi = \pi/2$ rad = 90°).


© 2012 Pearson Education, Inc.

AC Circuits With an Inductor

- So we can represent the voltage across the inductor also as a phasor, which **leads** the current phasor by 90 degrees.

$$v_L = I\omega L \cos(\omega t + 90^\circ)$$

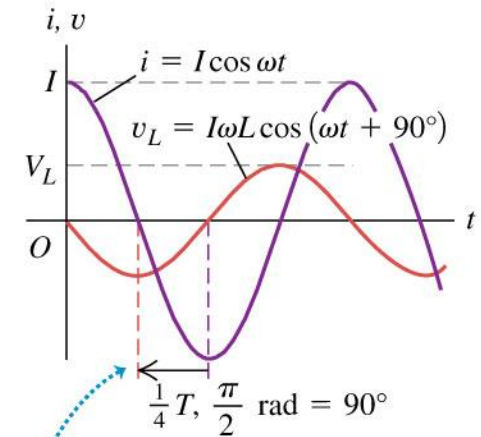
(b) Graphs of current and voltage versus time



Voltage curve *leads* current curve by a quarter-cycle (corresponding to $\phi = \pi/2 \text{ rad} = 90^\circ$).

© 2012 Pearson Education, Inc.

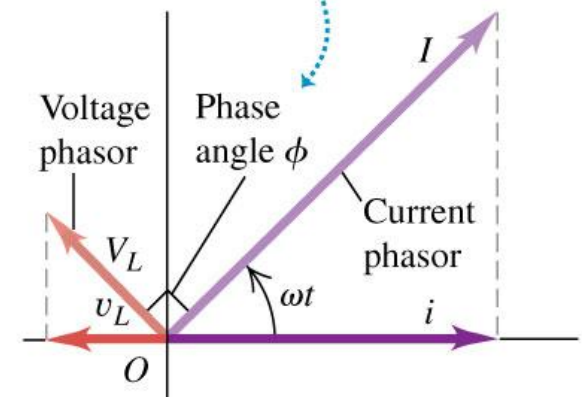Voltage phasor *leads* current phasor by $\phi = \pi/2 \text{ rad} = 90^\circ$.



© 2012 Pearson Education, Inc.

AC Circuits With an Inductor

- Notice that the magnitude of the phasor gives its maximum value, and we can write that maximum value as:


$$v_L = I \omega L \cos(\omega t + 90^\circ) = V_L \cos(\omega t + 90^\circ)$$

$$V_L = I X_L,$$

$$X_L = \omega L$$

- X_L is called the inductive reactance.

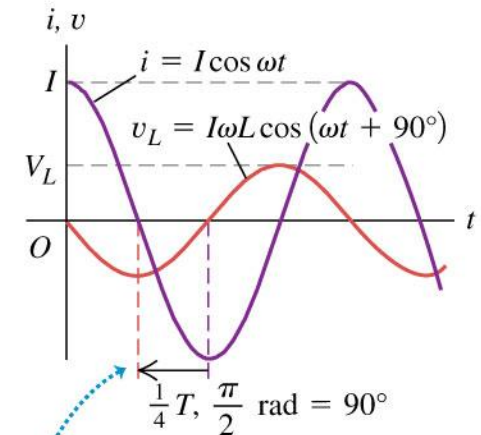
(b) Graphs of current and voltage versus time



Voltage curve *leads* current curve by a quarter-cycle (corresponding to $\phi = \pi/2$ rad = 90°).

© 2012 Pearson Education, Inc.

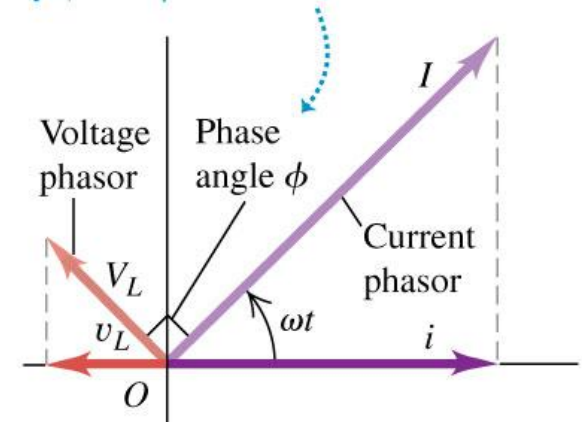Voltage phasor *leads* current phasor by $\phi = \pi/2$ rad = 90° .



© 2012 Pearson Education, Inc.

AC Circuits With a Capacitor

- Now, let's see what a capacitor looks like when connected to an AC source.


$$v_C = \frac{q}{C}$$

$$q = \int_0^q i dt = \int_0^q I \cos(\omega t) dt = \frac{I}{\omega} \sin(\omega t) \Rightarrow$$


$$v_C = \frac{I}{\omega C} \sin(\omega t) = \frac{I}{\omega C} \cos(\omega t - 90^\circ)$$

- So, the voltage across the capacitor is out of phase with the current source...

(a) Circuit with ac source and capacitor

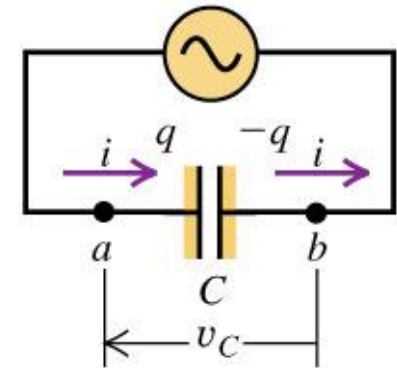

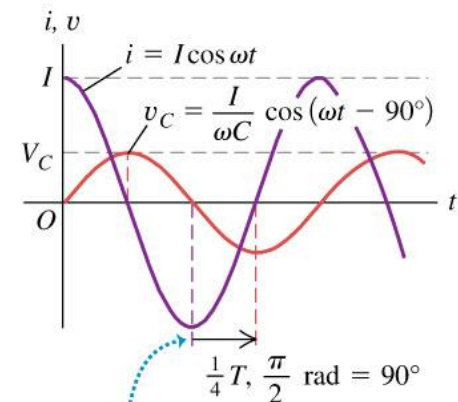
(b) Graphs of current and voltage versus time



Voltage curve lags current curve by a quarter-cycle (corresponding to $\phi = -\pi/2$ rad = -90°).


AC Circuits With a Capacitor

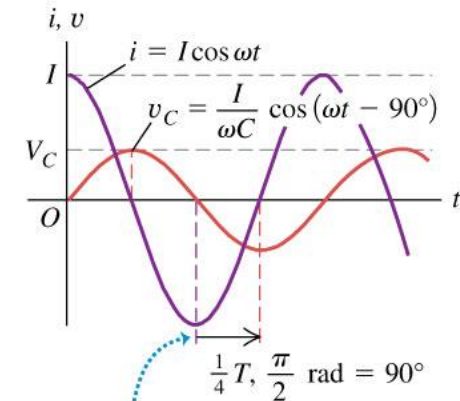(b) Graphs of current and voltage versus time



Voltage curve *lags* current curve by a quarter-cycle (corresponding to $\phi = -\pi/2$ rad = -90°).

(c) Phasor diagram

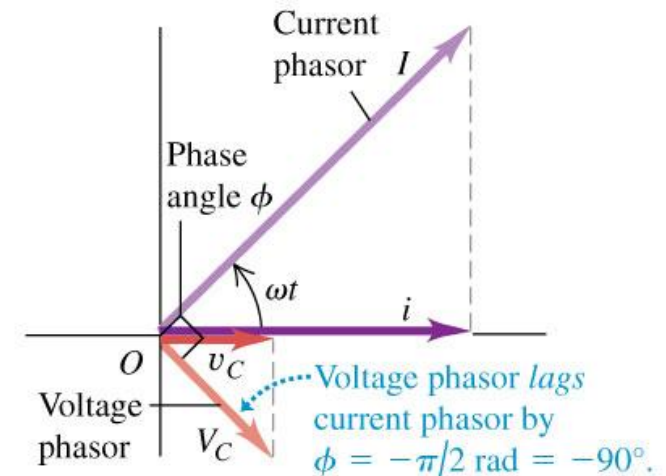

- So we can represent the voltage across the inductor also as a phasor, which ***lags*** the current phasor by 90 degrees.

$$v_C = \frac{I}{\omega C} \cos(\omega t - 90^\circ)$$

AC Circuits With a Capacitor

- Notice that the magnitude of the phasor gives its maximum value, and we can write that maximum value as:


$$v_C = \frac{I}{\omega C} \cos(\omega t - 90^\circ) = V_C \cos(\omega t - 90^\circ)$$

$$V_C = IX_C,$$

$$X_C = \frac{1}{\omega C}$$


- X_C is called the capacitive reactance.

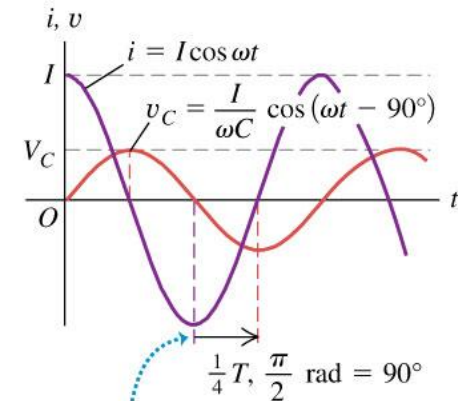(b) Graphs of current and voltage versus time



Voltage curve *lags* current curve by a quarter-cycle (corresponding to $\phi = -\pi/2$ rad = -90°).

(c) Phasor diagram

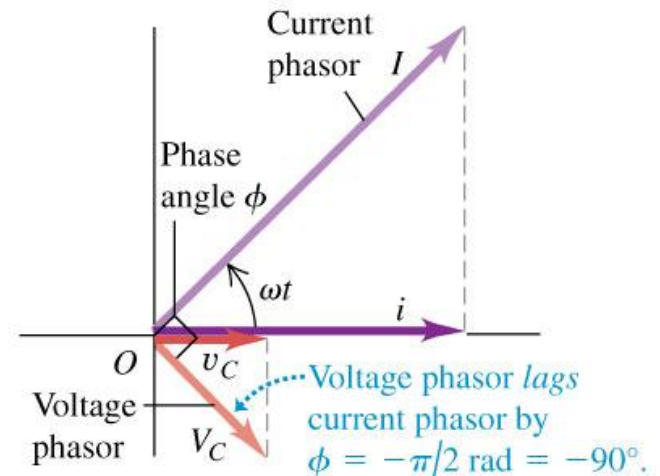


Usefulness of Reactances

Table 31.1 Circuit Elements with Alternating Current

Circuit Element	Amplitude Relationship	Circuit Quantity	Phase of v
Resistor	$V_R = IR$	R	In phase with i
Inductor	$V_L = IX_L$	$X_L = \omega L$	Leads i by 90°
Capacitor	$V_C = IX_C$	$X_C = 1/\omega C$	Lags i by 90°

© 2012 Pearson Education, Inc.

- Notice that the reactances are dependent on the angular frequency, (the resistance is not).
- As $\omega \rightarrow 0$ (DC), there is no inductive effect – X_L goes to zero and current is passed through the inductor, while no current is passed through the capacitor – X_C diverges.
- As ω gets large, X_C goes to zero and current is passed through the capacitor, while no current is passed through the inductor – X_L gets large because of the quickly changing current.

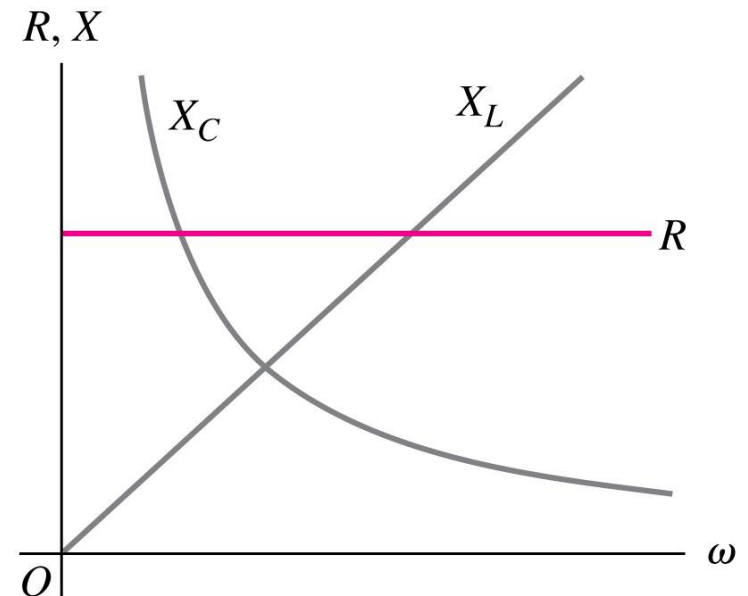


© 2012 Pearson Education, Inc.

Usefulness of Reactances

- We can use these properties to create frequency filters.
- Inductors are used as “low-pass” filters.
- Capacitors are used as “high-pass” filters.
- In combination, you can create a “cross-over” circuit.

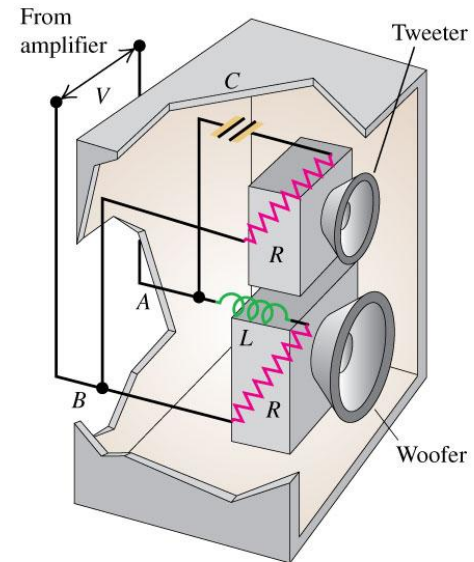(a) A crossover network in a loudspeaker system



(b) Graphs of rms current as functions of frequency for a given amplifier voltage

