
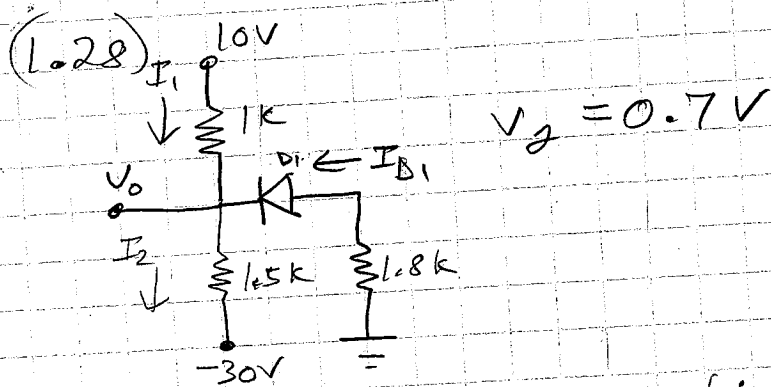


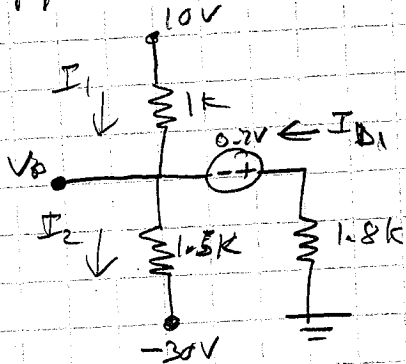Anthony Marcuso  
ECE 321  
HW-2  
30 Aug 2012



Suppose  $D_1$  is Forward biased:



$$KCL: -\left(\frac{10 - V_o}{1k}\right) + \frac{V_o - (-30)}{1.5k} - \left(\frac{0 - (V_o + 0.7)}{1.8k}\right) = 0$$

$$9V_o - 90 + 6V_o + 180 + 5V_o + 3.5 = 0$$

$$20V_o = 93.5$$


$$V_o = \boxed{-4.675V}$$

$$I_{D1} = \frac{0 - (-4.675 + 0.7)}{1.8k} = \boxed{2.21mA} = I_{1.8k}$$


$\therefore D_1$  is Forward-biased.

$$I_{1.5k} = \frac{-4.675 - (-30)}{1.5k} = \boxed{16.883mA} = I_{1.5k}$$
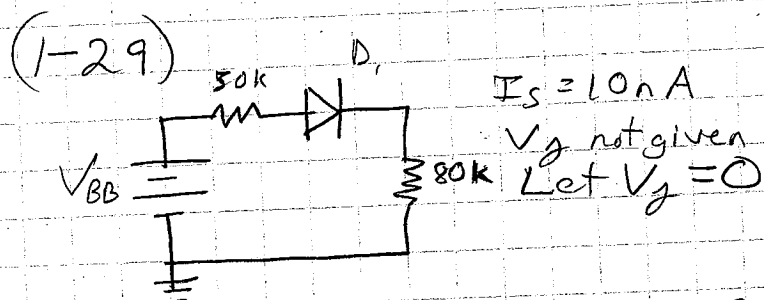
$$I_{1k} = \frac{10 - (-4.675)}{1k} = \boxed{14.675mA} = I_{1k}$$



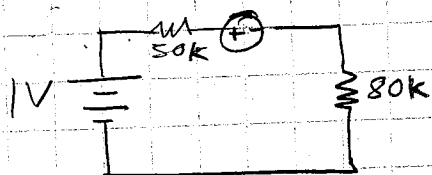(a)  $V_{BB} = 1\text{V}$ , Suppose  $D_1$  is forward-biased:



KVL:  $-1\text{V} + (50\text{k})I_D + 80\text{k}(I_D) = 0$

$(130\text{k})I_D = 1\text{V}$


$I_D = \boxed{7.69\mu\text{A}}$

$I_D = 7.69\mu\text{A} = I_S(e^{\frac{V_D}{V_{TH}}} - 1)$

$V_D = 26\text{mV} \ln\left(\frac{7.69\mu\text{A}}{10\text{nA}} + 1\right) = \boxed{172\text{mV}}$

$I_D$  and  $V_D$  positive  $\therefore D_1$  is forward-biased.

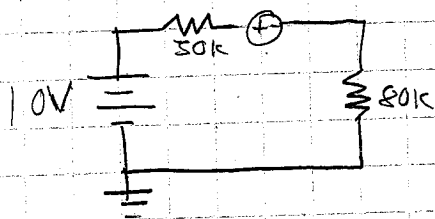(b)  $V_{BB} = 10\text{V}$ , Suppose  $D_1$  is forward-biased:




KVL:  $-10\text{V} + (50\text{k})I_D + (80\text{k})I_D = 0$

$(130\text{k})I_D = 10\text{V}$

$I_D = \boxed{76.9\mu\text{A}}$

$V_D = 26\text{mV} \ln\left(\frac{76.9\mu\text{A}}{10\text{nA}} + 1\right) = \boxed{232\text{mV}}$

$\therefore D_1$  is forward-biased

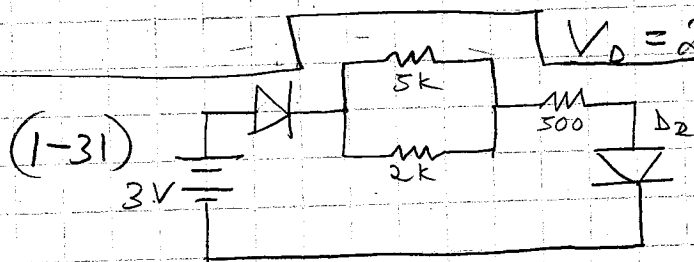


$I_{SD1} = 1\text{nA}$

$I_{SD2} = 4\text{nA}$

$V_g$  not given  $\Rightarrow$  Let  $V_g = 0$

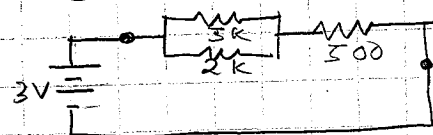
Assume  $D_1$  and  $D_2$  are forward biased:




KVL:  $-3\text{V} + 1.928\text{k}I_D + 500I_D = 0$

$1.928\text{k}I_D = 3 \Rightarrow I_D = \boxed{1.55\text{mA}}$

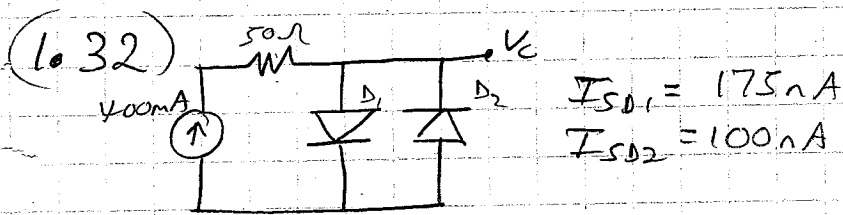$V_D = 26\text{mV} \ln\left(\frac{1.55\text{mA}}{4\text{nA}} + 1\right) = \boxed{335\text{mV}} = V_o$   $\therefore D_1$  and  $D_2$  are forward-biased



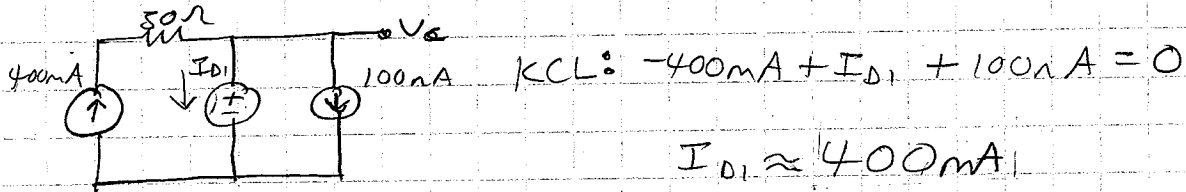
Assume  $D_1$  is forward-biased and  $D_2$  is reverse-biased.




$$I_{D1} \approx 400\text{mA}$$

$$V_{D1} = 26\text{mV} \ln\left(\frac{400\text{mA}}{175\text{nA}} + 1\right) = 381\text{mV} = V_c$$

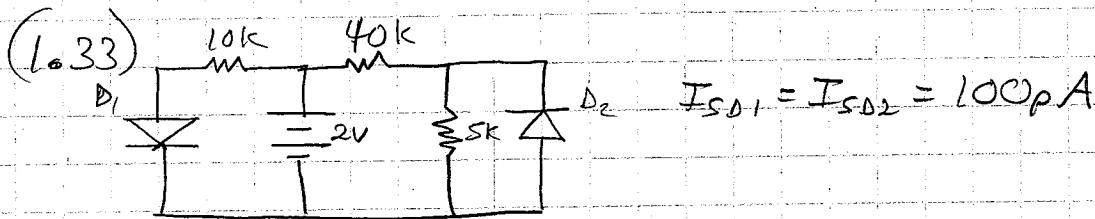$\therefore D_1$  is forward-biased and  $D_2$  is reverse-biased



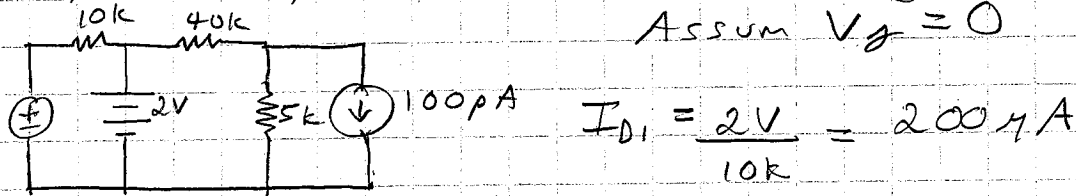Assume  $D_1$  is forward biased and  $D_2$  is reverse-biased  
Assume  $V_g = 0$



$$V_{D1} = 26\text{mV} \ln\left(\frac{200\mu\text{A}}{100\text{pA}} + 1\right) = \boxed{377.2\text{mV}}$$

$$\text{KCL: } -\left(\frac{2 - V_x}{40\text{k}}\right) + \frac{V_x}{5\text{k}} + 100\text{pA} = 0$$

$$-2 + V_x + 8V_x + (40\text{k})(100\text{pA}) = 0$$

$$9V_x = 1.99$$


$$V_x = 222\text{mV}$$

$$I_{5\text{k}} = \frac{V_x}{5\text{k}} = \boxed{44.44\mu\text{A}}$$


$$I_{D1} = \frac{2 - 377.2\text{mV}}{10\text{k}} = \boxed{162.28\mu\text{A}}$$

$\therefore D_1$  is forward-biased  
and  $D_2$  is reverse-biased

(1.34)

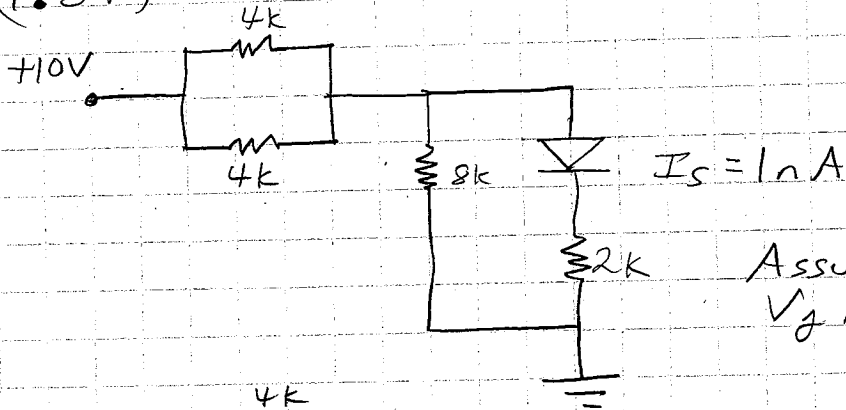

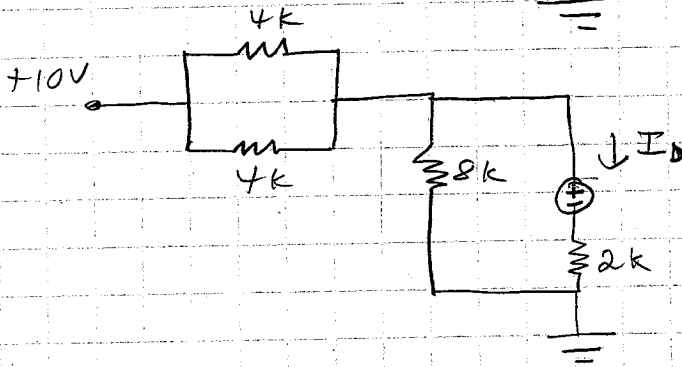Assume forward-biased  
 $V_f$  not given, assume  $V_f = 0$



$$I_D = \frac{8k}{8k + 2k} \frac{10V}{4k // 4k + 8k // 2k}$$


$$I_D = \boxed{2.22 \text{ mA}}$$

$$V_D = 26 \text{ mV} \ln \left( \frac{2.22 \text{ mA}}{1 \text{ nA}} + 1 \right)$$

$$V_D = \boxed{380 \text{ mV}}$$

$\therefore D_1$  is forward-biased

(1.35)

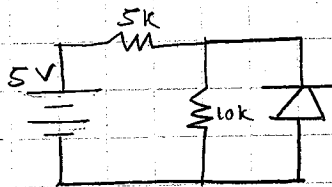

$$C_{j0} = 100 \text{ fF}$$

$$V_{bi} = 0.72 \text{ V}$$

$I_s$  not given


$\Rightarrow$  Assume  $I_s = 0$

$$V_R = \frac{10k}{15k} 5V = 3.33 \text{ V} \quad (\text{reverse diode voltage})$$


$$C_j = \frac{C_{j0}}{\left(1 + \frac{V_R}{V_{bi}}\right)^{1/2}} = \frac{100 \text{ fF}}{\left(1 + \frac{3.33 \text{ V}}{0.72 \text{ V}}\right)^{1/2}} = \boxed{17.76 \text{ fF}}$$

Anthony Mancuso  
ECE 321  
H.W-2  
30 Aug 2012

(1-36)

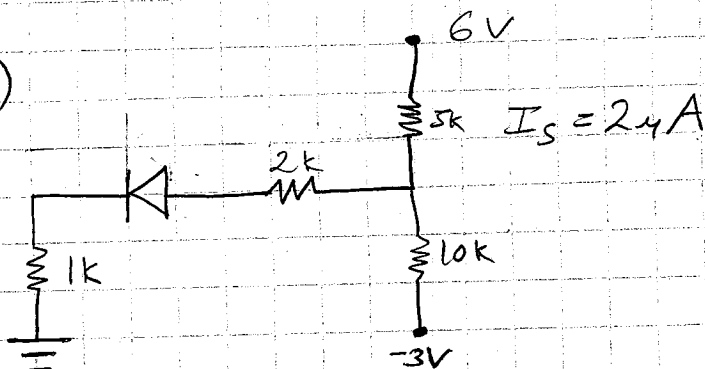

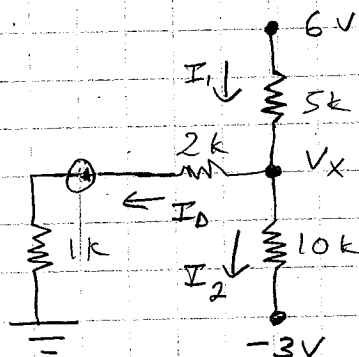Assume D is forward biased.  
 $V_f$  not given. Assume  $V_f = 0$



$$\text{KCL: } \frac{-(6 - V_x)}{5k} + \frac{V_x}{3k} + \frac{V_x - (-3)}{10k} = 0$$

$$-36 + 6V_x + 10V_x + 3V_x + 9 = 0$$

$$19V_x = 27 \Rightarrow V_x = 1.42V$$

$$I_D = \frac{1.42V}{3k} = \boxed{474\mu A}$$

$$V_D = 26mV \ln\left(\frac{474\mu A}{2\mu A} + 1\right) = \boxed{142.3mV}$$