

March 21st 2013

NAME: SOLUTION SET.

MAXIMUM POINTS: 100

EECE 322: Electronics-II (Spring 2013, University of New Mexico)
MID TERM EXAMINATION-I

RULES:


- Write your name on the top left corner
- Time Allotted = 75 Minutes
- Closed Book and Closed Notes
- You are allowed one single sided 8.5 x 11 page of formulae
- You may use a calculator
- Write your answers on the question paper. You may use additional sheets if needed.

HINTS:

- Please read the questions carefully and only provide only the information that is requested. This will save you time.
- If you are stuck in a particular question, move on to the next and come back to the question later. Solving the easy problems will give you confidence to solve the more challenging questions.

Section A: Conceptual Questions (60 Points)

1. Consider the transistor shown below.

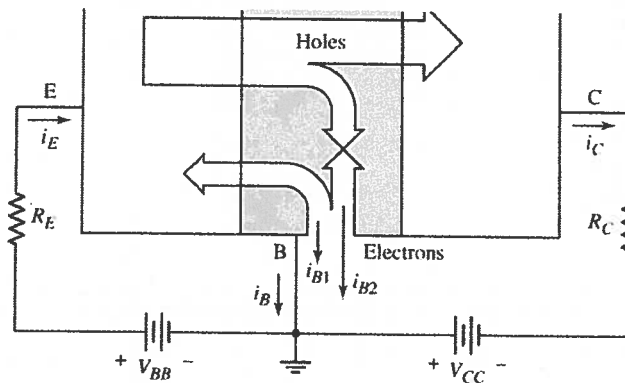

4 Points

Which of these statements about this transistor is true?

- a. npn transistor in the forward active mode
- b. pnp transistor in the inverse active mode
- c. pnp transistor in the forward active mode
- d. pnp transistor in the cut-off mode


2 The common emitter current gain is defined as ratio of

5 Points

- a. Collector current to Emitter Current
- b. Emitter current to Collector Current
- c. Collector current to Base Current
- d. Base current to Emitter Current

3 Thevenize the circuit shown below at the dotted line. Calculate the value for R_{TH} and V_{TH} ?

8 Points

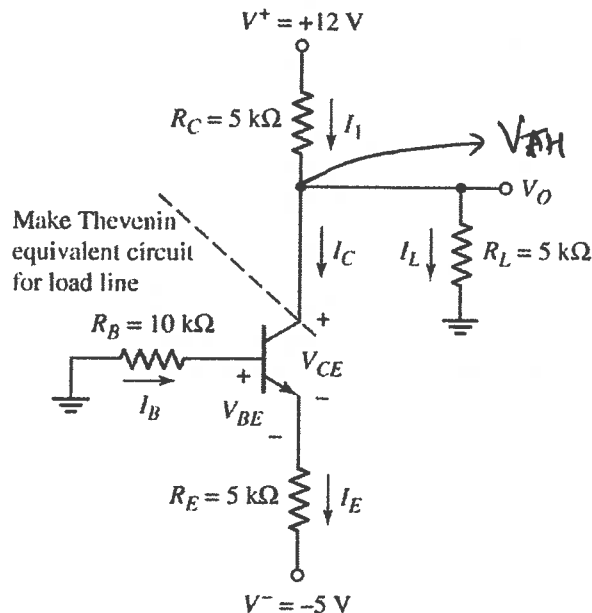

$$R_{TH} = 5k\Omega \parallel 5k\Omega = 2.5k\Omega$$
$$V_{TH} = 12 \times \frac{5k}{5k+5k} = 6V$$

4. If the h-parameter, h_{fe} , of the transistor is 100 and the diffusion resistance is $1k\Omega$, then the transconductance (g_m) is equal to

5 Points

(A) 10mA/V

(B) 100mA/V

(C) 1mA/V

(D) 0.1 mA/V


$$h_{fe} = \beta = 100$$

$$g_m r_{\pi} = \beta$$

$$g_m = \frac{100}{1k\Omega} = 100mA/V$$

5. Consider the figure below. Write an expression for the overall gain for the amplifier (v_o/v_s), including the loading effect.


7 Points

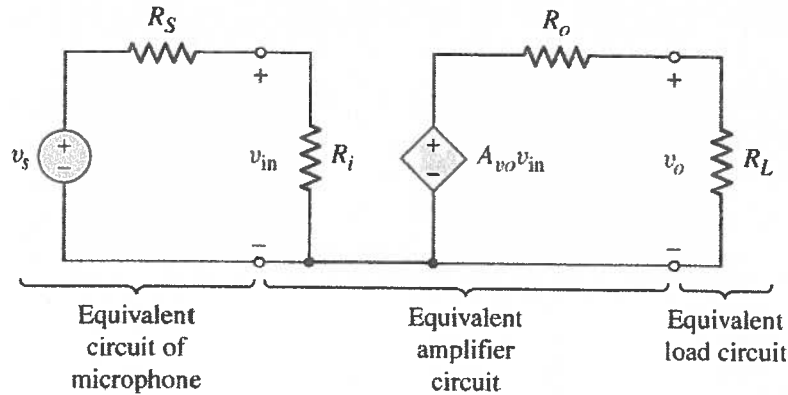

$$\frac{v_o}{v_s} = \left(\frac{R_i}{R_i + R_s} \right) A_{v_o} \left(\frac{R_L}{R_o + R_L} \right)$$

6. In the circuit below, calculate the slope of the AC and the DC load line.


8 Points

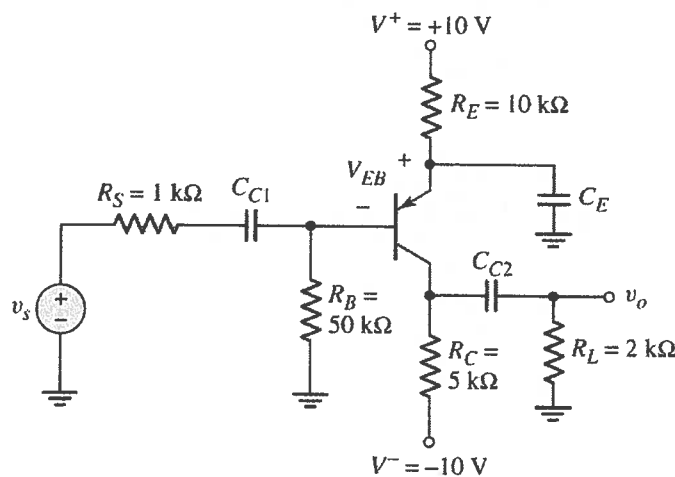

Slope of DC load line $= -\frac{1}{R_E + R_C} = -\frac{1}{15 \text{ k}\Omega}$

Slope of AC load line $= -\frac{1}{R_C \parallel R_L} = -\frac{1}{1.43 \text{ k}\Omega}$

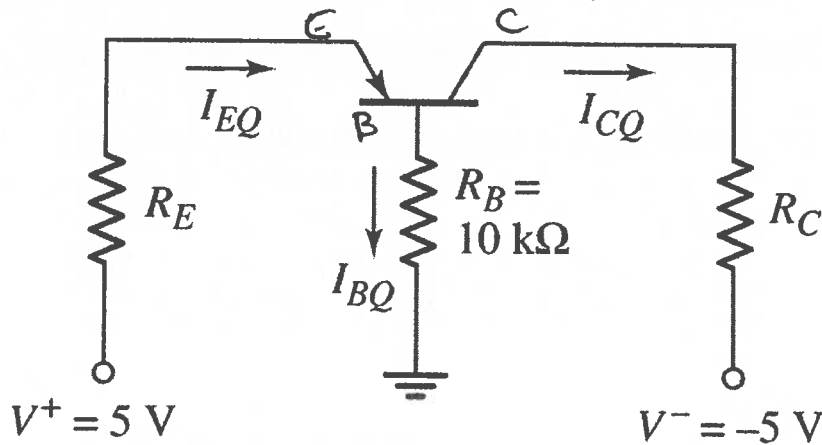7. Calculate the values for R_E and R_C , such that $I_{EQ}=0.5\text{mA}$ and $V_{ECQ}=4.0\text{V}$. The transistor parameters are $\beta=120$ and $V_{EB}(\text{on})=0.7\text{V}$.



8 Points

KVL on E-B loop.

$$V^+ - I_{EQ} R_E - V_{EB(\text{on})} - \frac{I_{EQ} R_B}{(1+\beta)} = 0$$

$$\underline{R_E = 8.52 \text{ k}\Omega}$$

$$I_{CQ} = I_{EQ} \frac{\beta}{(1+\beta)} = 0.496 \text{ mA}$$


KVL on E-C loop

$$V^+ - I_{EQ} R_E - V_{ECQ} - I_{CQ} R_C - V^- = 0$$

$$\underline{R_C = 3.51 \text{ k}\Omega}$$

8. Consider the AC equivalent circuit shown below.

5 Points

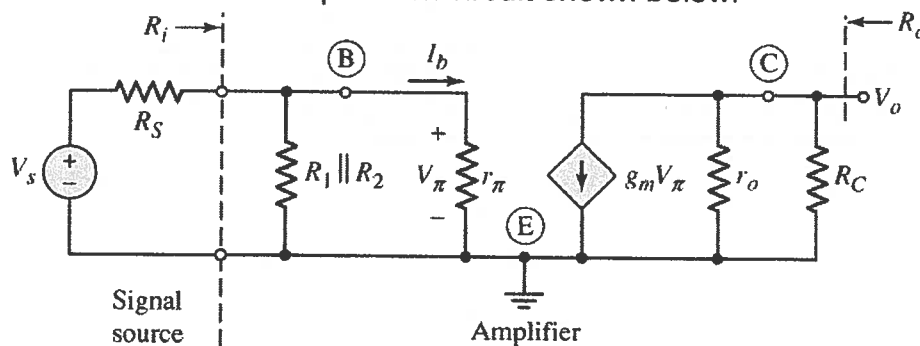


The output voltage is

- a. $-g_m V_\pi (r_o // R_C)$
- b. $-g_m V_\pi (R_C)$
- c. $+g_m V_\pi (r_o // R_C)$
- d. $-g_m V_\pi (r_o // R_C) (R_i / R_i + R_s)$

9. Write an expression for the input resistance, R_i , of the circuit shown below.

5 Points

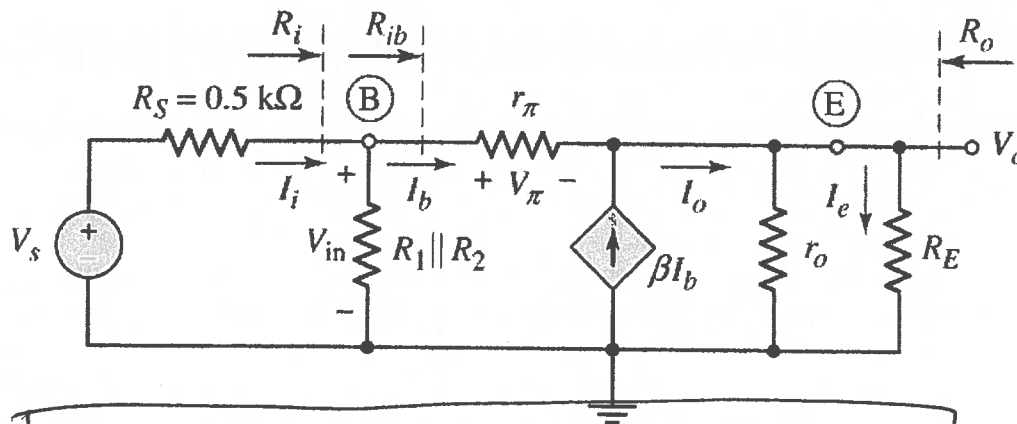

$$R_{ib} = r_{\pi} + (1 + \beta) r_o \parallel R_E$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

10. In circuit in problem 9, assume that $R_S = 0$. Write an expression for the output resistance, R_o .

5 Points


$$R_o = R_E \parallel r_o \parallel \frac{r_{\pi}}{1 + \beta}$$

Section B: Problems (40 Points)

20 Points

B.1. Consider the circuit below. Assume $\beta = 50$.

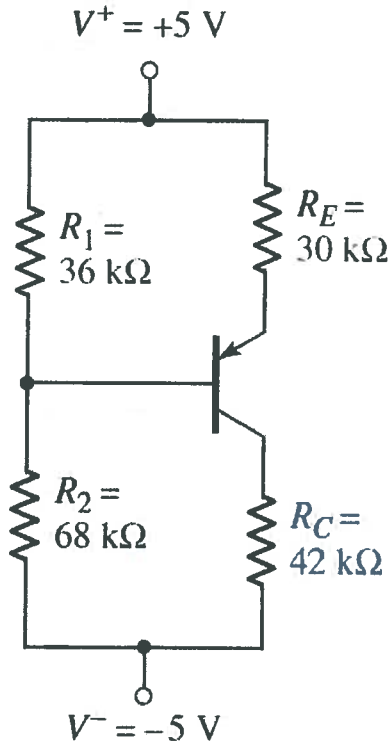- Calculate R_{TH} and V_{TH} .
- Calculate I_{CQ}
- Calculate V_{ECQ}
- Draw the DC load line and label I_{Cmax} , V_{CEmax} and the Q-point.



$$\textcircled{a} R_{TH} = 36k\Omega \parallel 68k\Omega = 23.5k\Omega$$

$$V_{TH} = \left(\frac{68}{36+68} \right) 10 - 5 = 1.54V$$

\textcircled{b} KVL on $B-E$ loop

$$V_{TH} - I_{BQ} R_{TH} - V_{BE(on)} - I_{BQ} (1+\beta) R_E = 0$$

$$5V - I_{BQ} (1+\beta) R_E - V_{BE(on)} - I_{BQ} R_{TH} = 0$$

$$I_{BQ} = 1.78\mu A$$


$$I_{CQ} = 0.0888mA \quad I_{EQ} = 0.0906mA$$

\textcircled{c} KVL on $E-C$ loop


$$10 - (0.0906)(30) - V_{ECQ} - (0.0888)(42) = 0$$

$$V_{ECQ} = 3.55V$$

\textcircled{d}

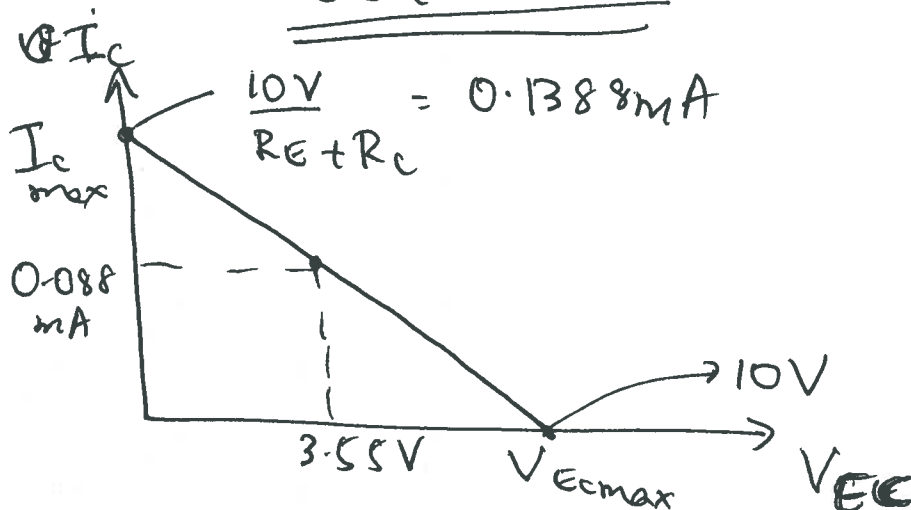


B.2 In the circuit below with transistor parameters $\beta = 180$ and $V_A = \infty$. Design the bias resistors (i.e. determine R_1 and R_2) to achieve maximum symmetrical swing in the output voltage and to maintain a bias-stable circuit. The total instantaneous C-E voltage is to remain in the range $0.5 \leq v_{CE} \leq 4.5$ V and the total instantaneous collector current is to be $i_C \geq 0.25$ mA.

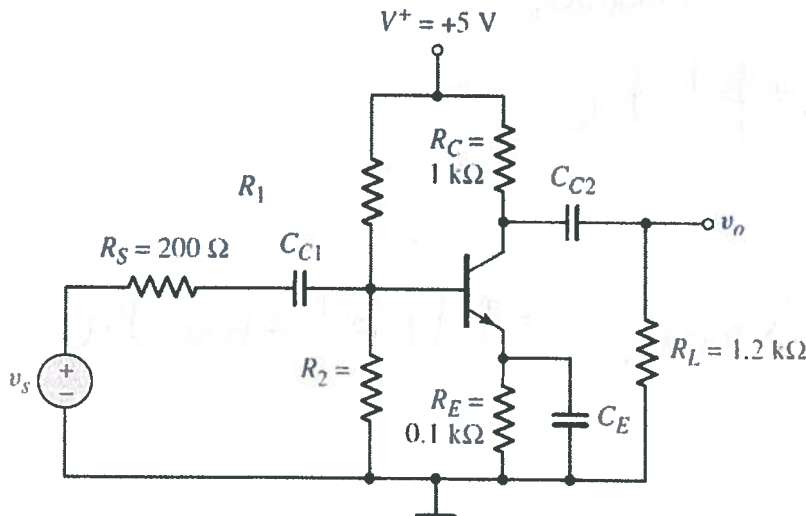

20 Points

Solution

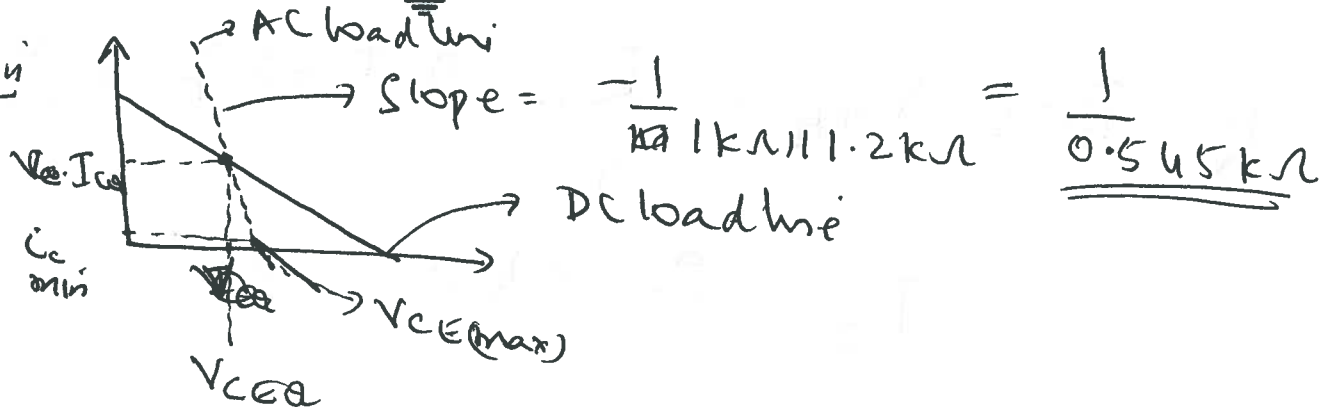

For max symmetrical swing

$$\Delta i_C = I_{CQ} - 0.25$$

$$\Delta v_{CE} = V_{CEQ} - 0.5 \text{ V} \quad |\Delta i_C| = \frac{1}{0.545 \text{ k}\Omega} |v_{CE}|$$

$$I_{CQ} - 0.25 = \frac{V_{CEQ} - 0.5}{0.545} \quad \text{(A)}$$

KVL on C-E loop

$$5 \text{ V} - I_{CQ}(R_C + R_E) - V_{CEQ} = 0$$

$$V_{CEQ} = 5 - I_{CQ}(1.1) \Rightarrow \text{(B)}$$

Combine (A) & (B) to get

$$I_{CQ} = 2.82 \text{ mA} \quad I_{BQ} = 0.0157 \text{ mA}$$

For bias stable circuit,

$$R_{TH} = (0.1)(1+\beta) R_E$$
$$= \underline{\underline{1.81 \text{ k}\Omega}}$$

KVL on BE loop

$$V_{TH} - I_{BQ} R_{TH} - V_{BE(on)} + (1+\beta) I_{BQ} R_E$$

$$V_{TH} = 1.013 \text{ V}$$

R_1 But $V_{TH} = \frac{R_2}{R_1 + R_2} V^+ \Rightarrow R_1 = \underline{\underline{8.93 \text{ k}\Omega}}$

$$\underline{\underline{R_2 = 2.27 \text{ k}\Omega}}$$