

University of New Mexico
Department of Electrical and Computer Engineering

ECE 321 – Electronics I (Fall 2009)

Exam 3

Name: ANTHONY MANCOSO

Date: Nov. 18, 2009

Note: Only calculator, pencils, and pens are allowed.

1. (10 points) Fill in the blank:

(a) In standard CMOS process, the source and drain are formed by using Active layer masks. (FOL)

(b) The process of manufacturing transistors is called Front end of Line and the process of manufacturing interconnects is called Back end of Line (BOL)

(c) CMP stands for Chemical Mechanically Polished

(d) The effective width of two series NMOS with $W_1=6\mu\text{m}$ and $W_2=3\mu\text{m}$ is $W_T = \frac{W_1 \times W_2}{W_1 + W_2} = \boxed{2}$

(e) Electromigration is Metal atoms swept out of position by 'electron wind'

2. (20 points) You are asked to layout the power and ground bus in the layout of a logic block in a real chip. Assume that the logic block draws 80mA of current and the metal thickness is 0.4 μm . If the maximum current density $J_{\text{max}} = 2 \times 10^6 \text{ A/cm}^2$, determine the minimum width (in micron) of the interconnect that is needed to power the logic block.

$$J_{\text{max}} = \frac{I}{tW}$$

$$t = 0.4 \mu\text{m} = 0.00004 \text{ cm}$$

$$W = \frac{I}{tJ_{\text{max}}} = \frac{80 \text{ mA}}{[0.00004 \text{ cm}] (2 \times 10^6 \text{ A/cm}^2)}$$

$$= 0.001 \text{ cm} = 0.00001 \text{ m}$$

$$= \boxed{10.4 \mu\text{m}}$$

3. (30 points) A three-input CMOS NAND gate is designed as shown below. Assume that $V_{DD}=1.2\text{ V}$, $K'_n=90\text{ }\mu\text{A/V}^2$, $V_{tn}=0.4\text{ V}$, $K'_p=50\text{ }\mu\text{A/V}^2$, and $V_{tp}=-0.5\text{ V}$ in the 100nm technology node.

- Determine the width of NMOS and PMOS transistors in this NAND gate, such that the worst case delay becomes equivalent to a referenced inverter with $W_n=1\text{ }\mu\text{m}$ and $W_p=2\text{ }\mu\text{m}$.
- For the device sizes found in part (a), determine the switching threshold voltage, V_M , when all inputs are tied together.
- Find the maximum I_{DD} current for this NAND gate.

a) $\left(\frac{W}{L}\right)_{nT} = \frac{1\text{ }\mu\text{m}}{100\text{ nm}} = 10$


$\left(\frac{W}{L}\right)_{pT} = \frac{2\text{ }\mu\text{m}}{100\text{ nm}} = 20$

Equivalent ckt:

Worst case: Lowest current drive strength

Worst Case Pull-up: 1 path


 
$\therefore \left(\frac{W}{L}\right)_{pT} = \boxed{20}$ for each A, B, and C



Worst case Pull-Down: All on

$\therefore \left(\frac{W}{L}\right)_{nT} = \left(\left(\frac{W}{L}\right)_n^{-1} + \left(\frac{W}{L}\right)_n^{-1} + \left(\frac{W}{L}\right)_n^{-1}\right)^{-1} = 10$

 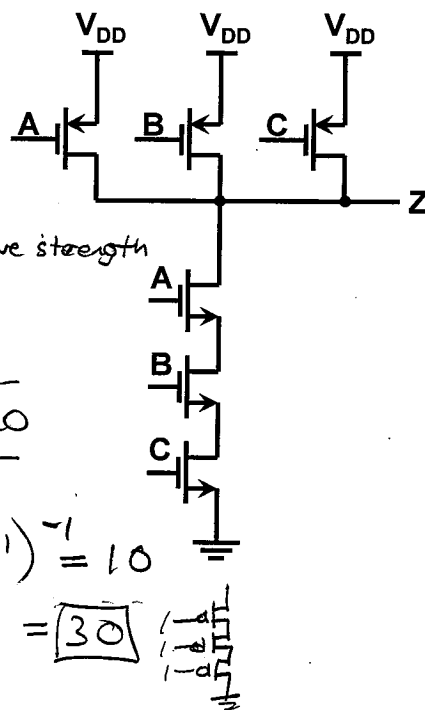$\frac{3}{\left(\frac{W}{L}\right)_n} = \frac{1}{10} \Rightarrow \left(\frac{W}{L}\right)_n = \boxed{30}$



Both transistors in saturation:

$\frac{K'_n}{2} \left(\frac{W}{L}\right)_{nT} (V_M - V_{tn})^2 = \frac{K'_p}{2} \left(\frac{W}{L}\right)_{pT} (V_M - V_{tp})^2$

$\frac{90\text{ }\mu\text{A/V}^2}{2} (10) (V_M - 0.4)^2 = \frac{50\text{ }\mu\text{A/V}^2}{2} (20) (V_M - 0.5)^2$

$V_M = \boxed{0.451\text{ V}}$

(c) $I_{max} = \frac{K'_n}{2} \left(\frac{W}{L}\right)_{nT} (V_M - V_{tn})^2 = \frac{K'_p}{2} \left(\frac{W}{L}\right)_{pT} (V_M - V_{tp})^2$
 $= \frac{90\text{ }\mu\text{A/V}^2}{2} (10) (0.451 - 0.4)^2$
 $= \boxed{1.18\text{ }\mu\text{A}}$

4. (40 points) We would like to design the following circuit such that the worst case propagation delays (t_{pHL} and t_{pLH}) are limited to 2.14 ns. Use Elmore delay equation to determine the W/L for PMOS and NMOS used in the 3-input NAND gate. Assume that $V_{DD}=1.2$ V, $K'_n=90 \mu A/V^2$, $V_{tn}=0.4$ V, $K'_p=50 \mu A/V^2$, and $V_{tp}=-0.5$ V in the 100nm technology node. Also assume that the transistors stay in saturation region for the length of the transition.


$$t_{pHL} = t_{pLH} = 2.14 \text{ ns} = \frac{C_L V_{DD}/2}{I_{avg}} = 0.69 \tau = 0.69 R_{out} C_L, \quad \text{Let } C_L = 100 \text{ fF}$$

$$R_{out} = \frac{t_{pLH}}{0.69 C_L} = \frac{2.14 \text{ ns}}{0.69 (100 \text{ fF})}$$

$$R_{out} = 34.78 \text{ k}\Omega$$

$$\tau_{Di} = \sum_{k=1}^N R_k C_k$$
 
$$\begin{aligned} \tau_{Di} &= (34.78 \text{ k} + 10 \text{ k}) (100 \text{ fF} + 10 \text{ fF} + 20 \text{ fF} + 30 \text{ fF}) \\ &\quad + (34.78 \text{ k} + 10 \text{ k} + 1 \text{ k}) (10 \text{ fF}) \\ &\quad + (34.78 \text{ k} + 10 \text{ k} + 1 \text{ k} + 1 \text{ k}) (20 \text{ fF}) \\ &= 7.165 \text{ ns} + 457.8 \text{ ps} + 935 \text{ ps} \\ &= 8.56 \text{ ns} \end{aligned}$$



$$\frac{C_L V_{DD}/2}{I_{SAT}} = 0.69 \tau_{Di} \Rightarrow I_{SAT} = \frac{C_L V_{DD}/2}{0.69 \tau_{Di}}$$

$$\frac{K'_n}{2} \left(\frac{W}{L}\right)_n (V_{GS} - V_{tn})^2 = \frac{C_L V_{DD}/2}{0.69 \tau_{Di}}$$

$$\frac{K'_n}{2} \left(\frac{W}{L}\right)_n \left(\frac{V_{DD}}{2} - V_{tn}\right)^2 = \frac{C_L V_{DD}/2}{0.69 \tau_{Di}}$$

$$\left(\frac{W}{L}\right)_n = \frac{C_L V_{DD}}{0.69 \tau_{Di} K'_n \left(\frac{V_{DD}}{2} - V_{tn}\right)^2} = \boxed{5.64}$$

$$\left(\frac{W}{L}\right)_p = \frac{C_L V_{DD}}{0.69 \tau_{Di} K'_p \left(\frac{V_{DD}}{2} - V_{tp}\right)^2} = \boxed{22.58}$$