

# **Homework 8 Due Thursday, Apr 4th, 2013 (In Class)**

Problem 6.71

In the common-base circuit shown in Figure P6.71, the transistor is a 2N2907A, with a nominal dc current gain of  $\beta = 80$ . (a) Determine  $I_{CQ}$  and  $V_{ECQ}$ . (b) Using the  $h$ -parameters (assuming  $h_{re} = 0$ ), determine the range in small-signal voltage gain  $A_v = v_o/v_s$ . (c) Determine the range in input and output resistances  $R_i$  and  $R_o$ .

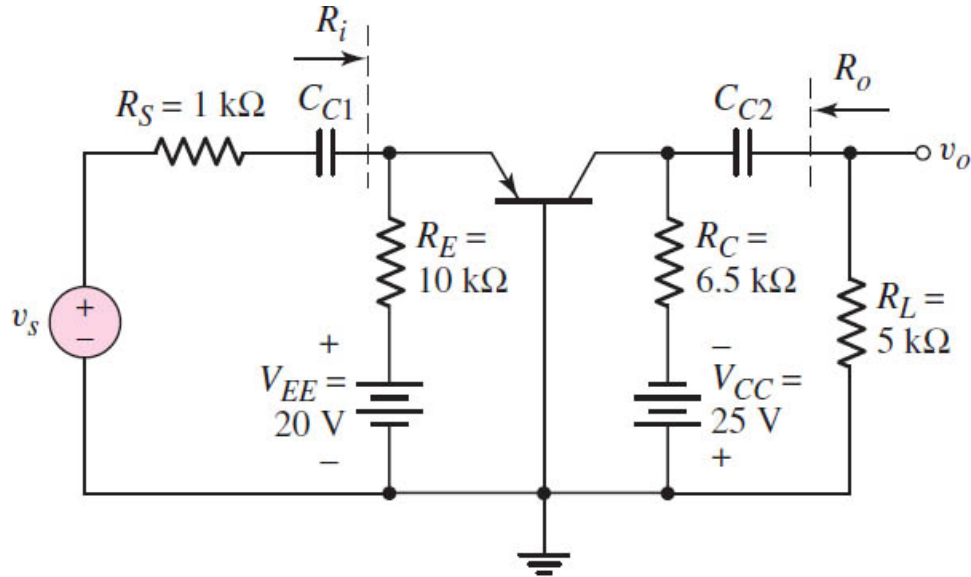


Figure P6.71

### Problem 6.73

Consider the ac equivalent circuit in Figure P6.73. The transistor parameters are  $\beta_1 = 120$ ,  $\beta_2 = 80$ ,  $V_{A1} = V_{A2} = \infty$ , and  $I_{CQ1} = I_{CQ2} = 1 \text{ mA}$ . (a) Find the small-signal voltage gain  $A_{v1} = V_{o1}/V_i$ . (b) Determine the small-signal voltage gain  $A_{v2} = V_{o2}/V_{o1}$ . (c) Find the overall small-signal voltage gain  $A_v = V_{o2}/V_i$ .

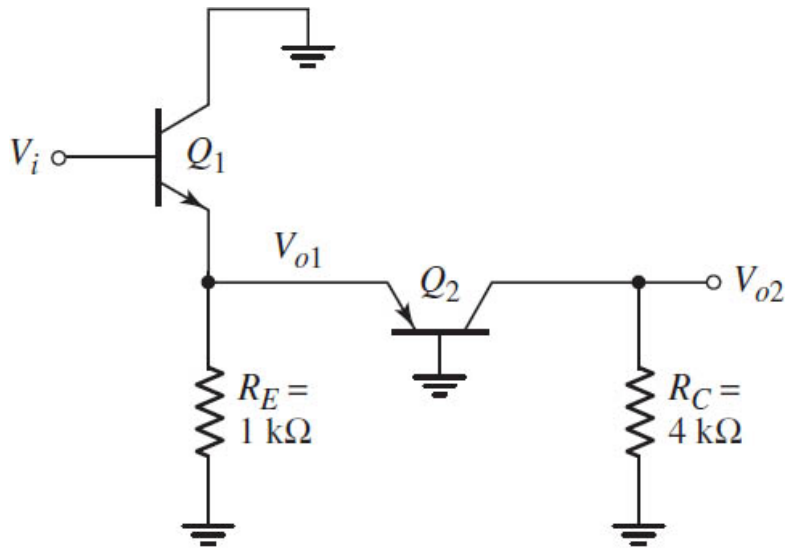


Figure P6.73

### Problem 6.77

The transistor parameters for the circuit in Figure P6.77 are  $\beta_1 = 120$ ,  $\beta_2 = 80$ ,  $V_{BE1}(on) = V_{BE2}(on) = 0.7$  V, and  $V_{A1} = V_{A2} = \infty$ . (a) Determine the quiescent collector current in each transistor. (b) Find the small-signal voltage gain  $A_v = v_o/v_s$ . (c) Determine the input and output resistances  $R_{ib}$  and  $R_o$ .

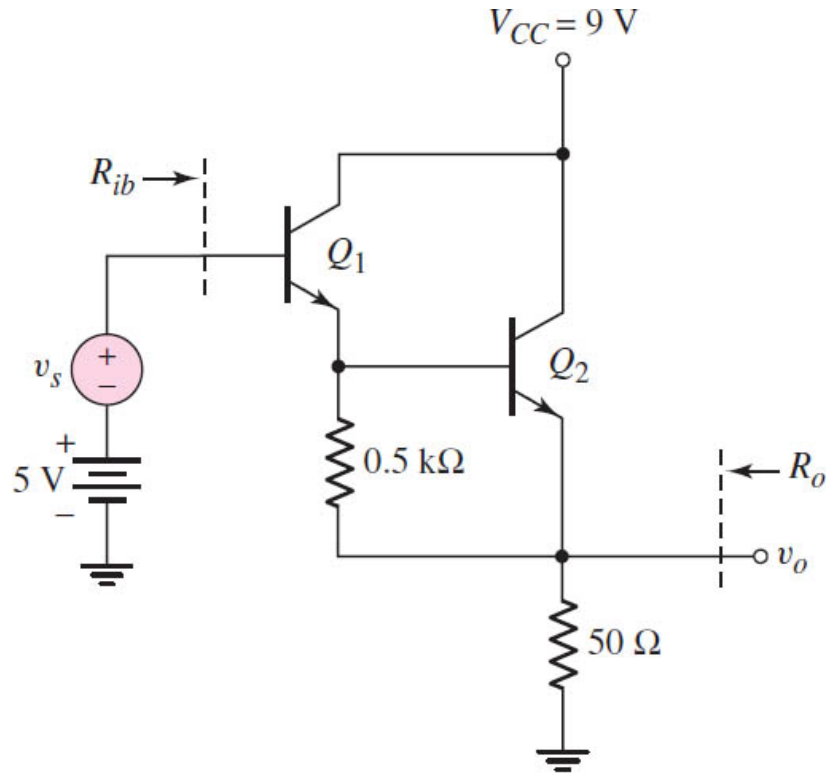


Figure P6.77

### Problem 7.5

Consider the circuit shown in Figure P7.5. (a) What is the value of the voltage transfer function  $V_o/V_i$  at very low frequencies? (b) Determine the voltage transfer function at very high frequencies. (c) Derive the expression for the voltage transfer function  $T(s) = V_o(s)/V_i(s)$ . Put the expression in the form  $T(s) = K(1 + s\tau_A)/(1 + s\tau_B)$ . What are the values of  $K$ ,  $\tau_A$ , and  $\tau_B$ ?

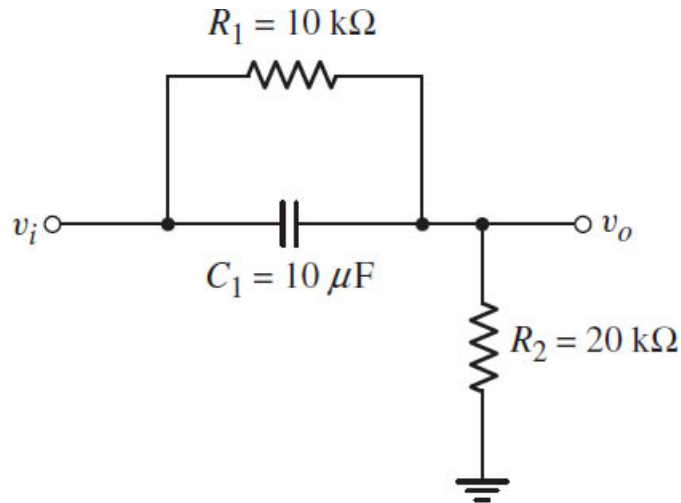


Figure P7.5

### Problem 7.7

A voltage transfer function is given by  $T(f) = 1/(1 + jf/f_T)^3$ . (a) Show that the actual response at  $f = f_T$  is approximately 9 dB below the maximum value. What is the phase angle at this frequency? (b) What is the slope of the magnitude plot for  $f \gg f_T$ ? What is the phase angle in this frequency range?