

Clocked Sequential System Design

Example 1 –
Multipliers
(Gradeschool, Modified Gradeschool)

Multiply Example

```
      10111001   (185)
x   11010111   (215)
-----
      10111001
      10111001
      10111001
      00000000
      10111001
      00000000
      10111001
      10111001
      -----
1001101101011111 (39775)
```

```

      10111001
x   11010111
-----

00000000000000000000  <- Start
                        with zero

```

```

      10111001
x   11010111
-----
      10111001  <- 1st Partial
0000000000000000  Product (PP)

```

```

      10111001
x   11010111
-----
      10111001
0000000010111001 <- sum of Prod, PP

```

```

      10111001
x   11010111
-----
      10111001 <- second PP
0000000010111001

```

```
      10111001
x    11010111
-----
      10111001
0000001000101011 <- running sum
```

```
      10111001
x    11010111
-----
      10111001 <- third PP
0000001000101011
```

```

      10111001
x    11010111
-----
      10111001
0000001100001111 <- running sum


```

```


      10111001
x    11010111
-----
      00000000 <- fourth PP
0000001100001111

```

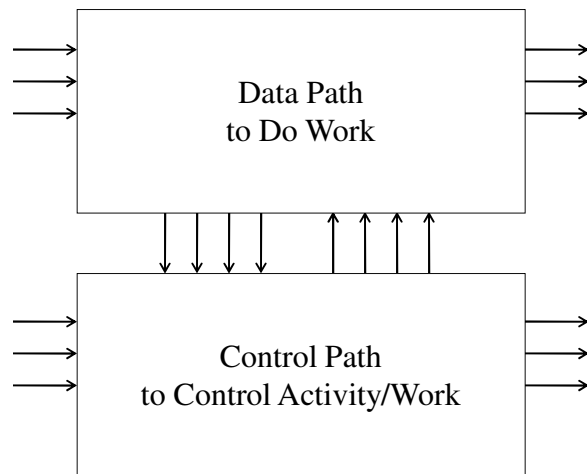
```
      10111001
x    11010111
-----
00000000
0000001100001111 <- running sum
```



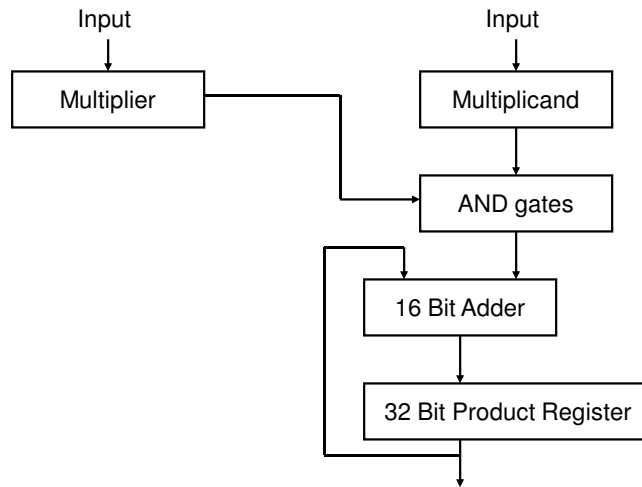
Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)



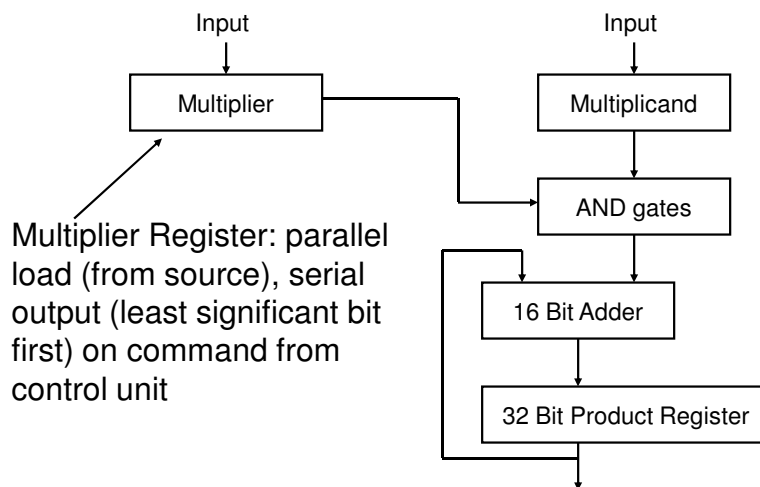
Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)



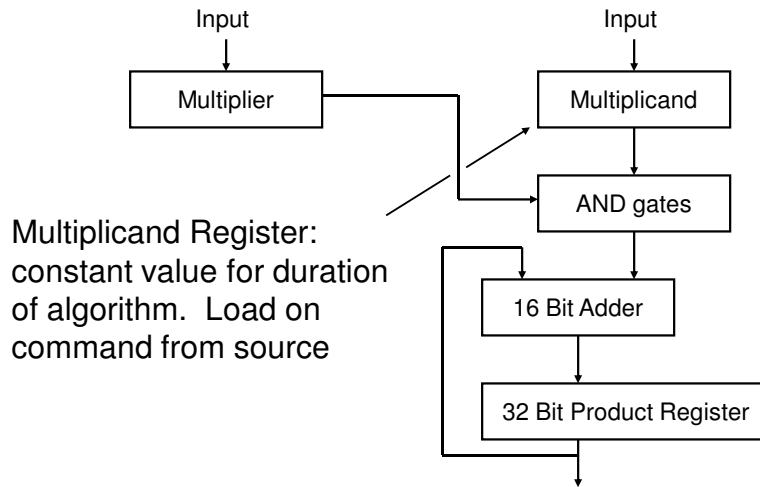
Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)



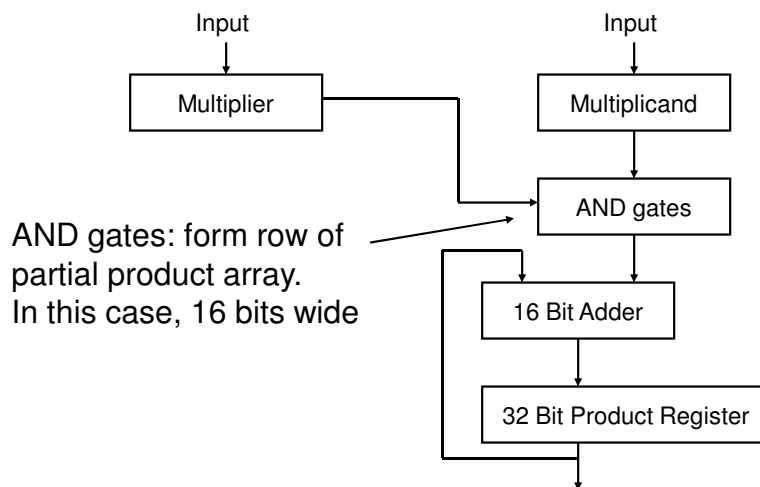
Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)



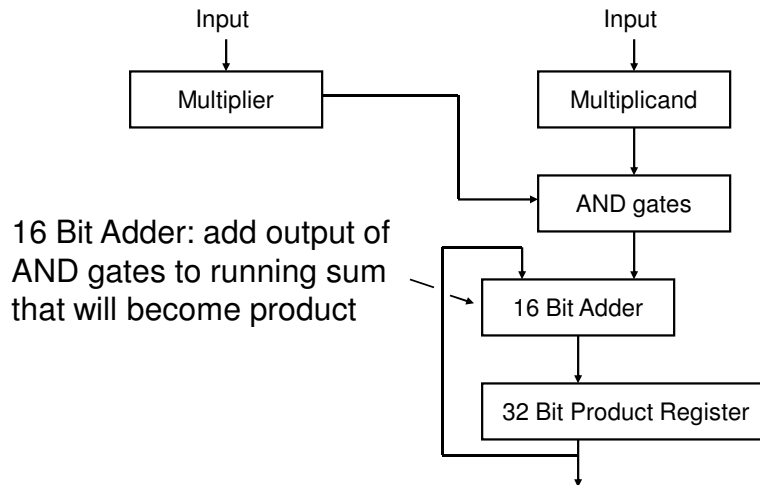
Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)



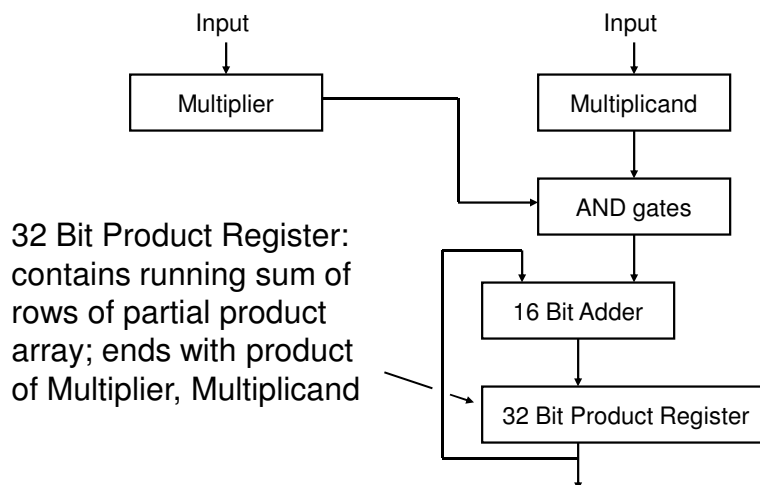Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)



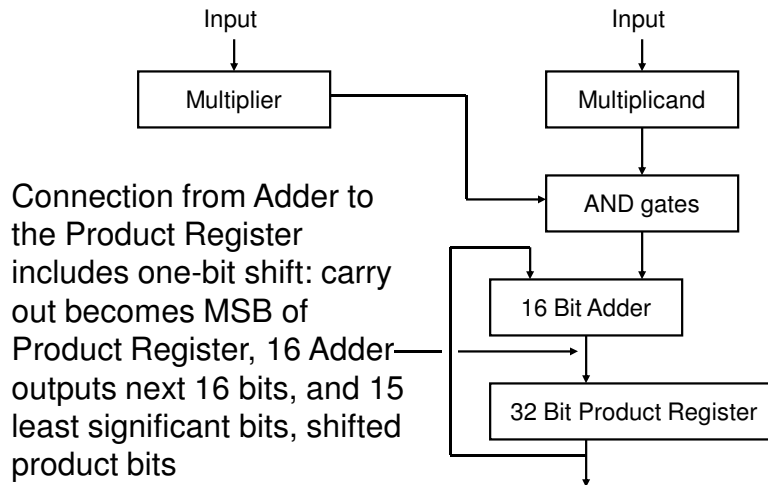Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)



Register: asynchronous and synchronous behavior

```
NAME_OF_PROC:
process ( <clock, reset, set go here> ) is

begin

    if <asynchronous signals tested here> then
        <put set, reset stuff here>
    elsif RISING_EDGE ( clock ) then
        < put synchronous stuff here, in particular... >
        if <enabling condition> then
            <action/activity of register goes here>
        end if;
    end if;

end process NAME_OF_PROC;
```

Multiplication – Simple Gradeschool Algorithm for 16 Bits (32 Bit Result)

Step 1:

Clear Product Register

Clear Counter

Load Multiplicand

Load Multiplier

Step 2: (repeat 16 times)

Increment Counter


Load Product Register

Shift Multiplier

Step 3:


Done

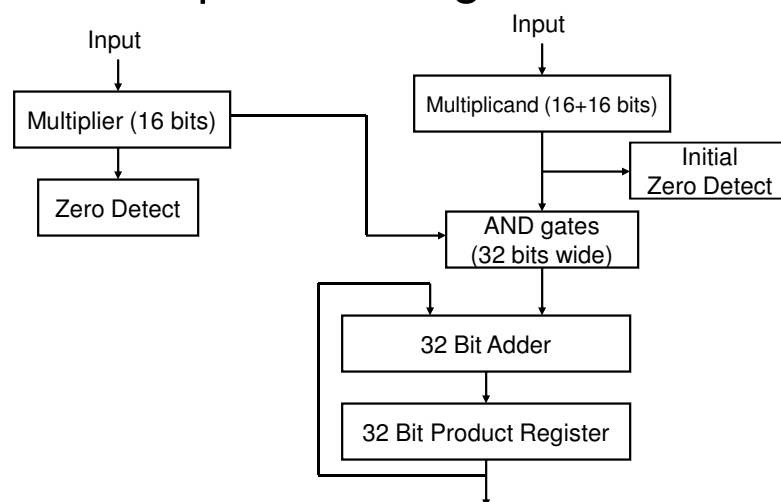Implement the Modified Gradeschool Multiplication Algorithm




[illegible][illegible]

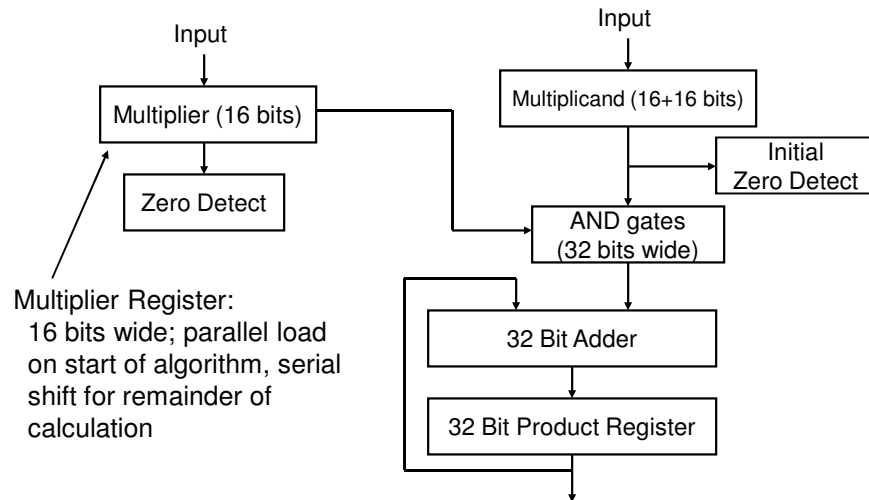
Implement the Modified Gradeschool Multiplication Algorithm



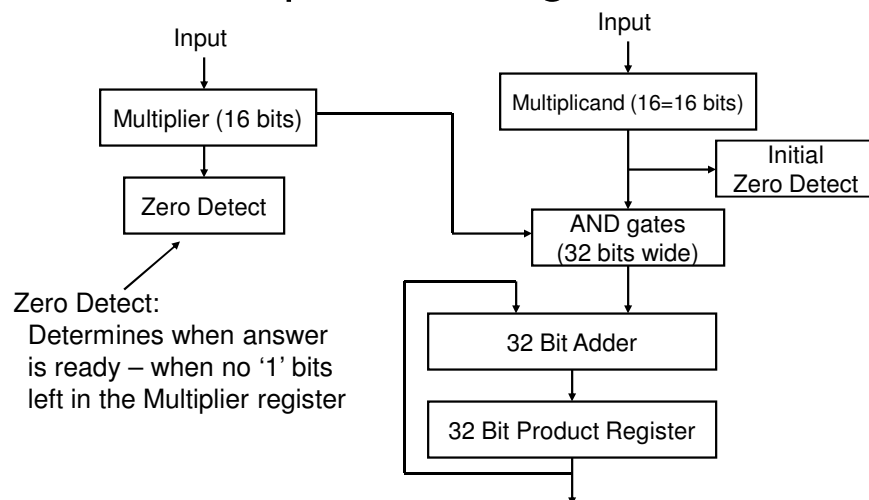
Implement the Modified Gradeschool Multiplication Algorithm



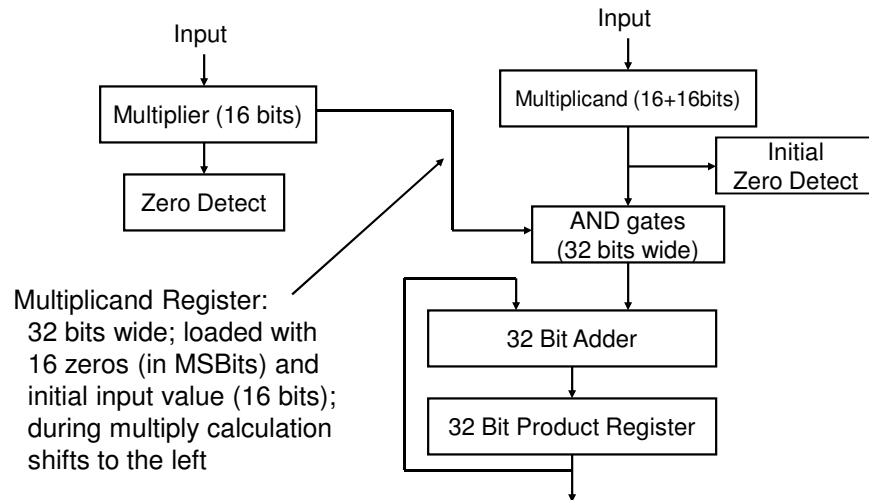
Implement the Modified Gradeschool Multiplication Algorithm



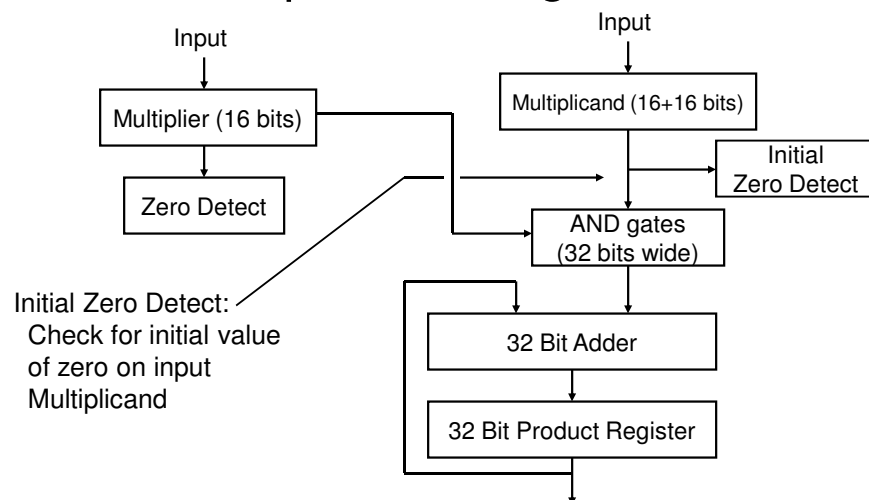
Implement the Modified Gradeschool Multiplication Algorithm



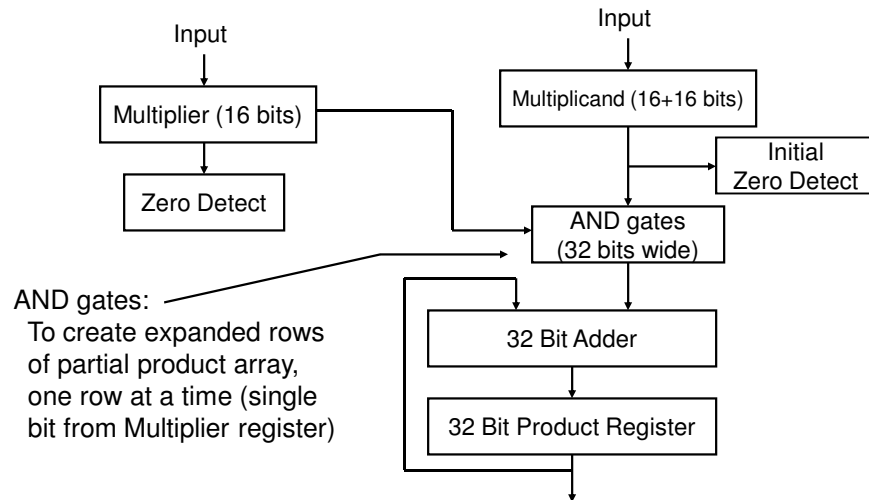
Implement the Modified Gradeschool Multiplication Algorithm



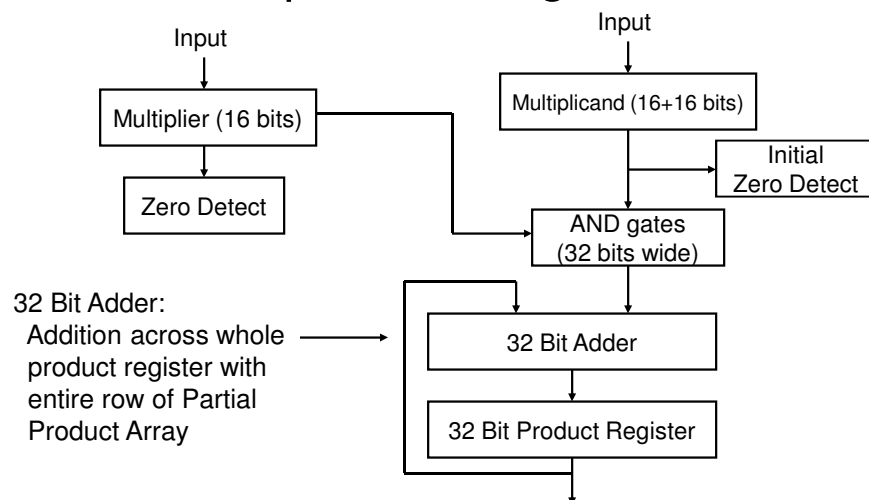Implement the Modified Gradeschool Multiplication Algorithm



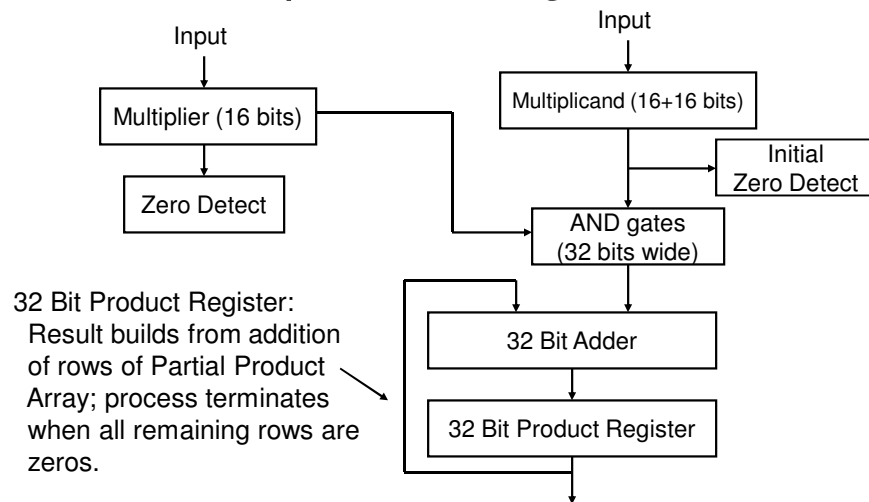Implement the Modified Gradeschool Multiplication Algorithm



Multiplication – Modified Gradeschool Algorithm for 16 Bits (32 Bit Result)

Step 1:

Clear Product Register

Load Multiplicand

Load Multiplier

Step 2:

If MIER = 0 OR MCAND = 0, done

Step 3:

Load Product Register

Shift Multiplier

Step 4:

If MIER = 0, then Done

else Go to Step 3