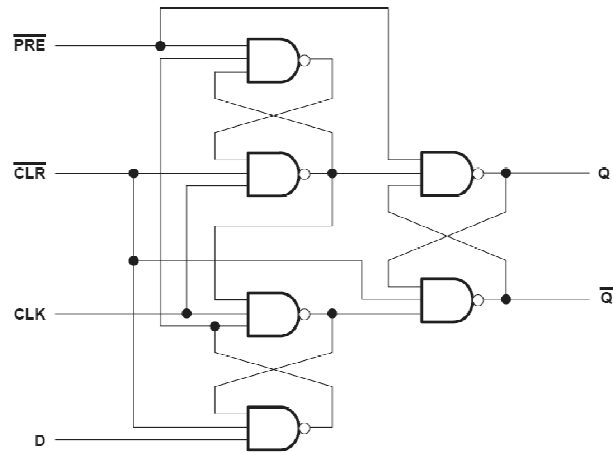


## Asynchronous Design Technique in Reverse → Analysis


### Analysis Technique

- Reverse order for analysis
- Start with logic diagram
- Generate equations
- Put equations in K-Map (Final State Table)
- Determine stable, unstable states
- Generate State Diagram
- Determine behavior


## SN7474 – D-FlipFlop




## Cleaned Up Schematic

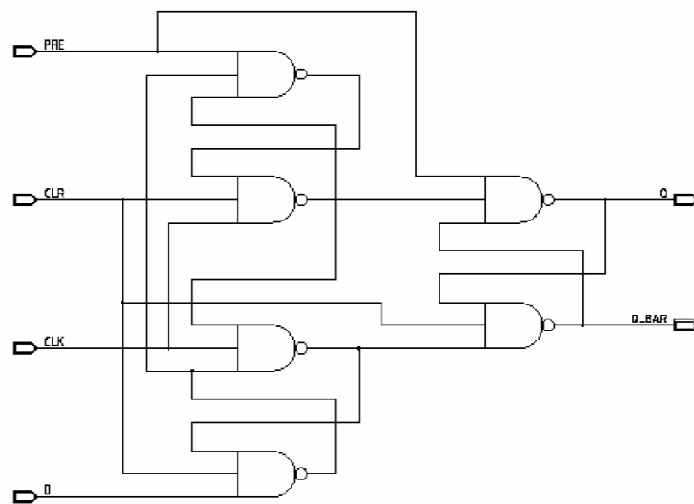


## Cleaned Up Schematic (DeMorgan)

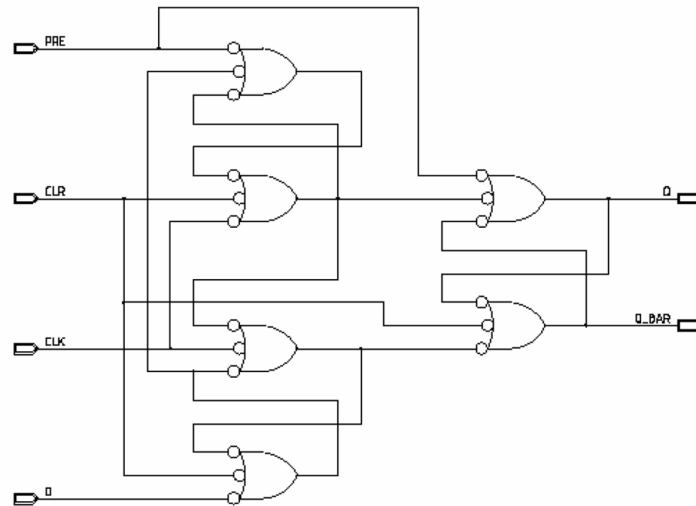


## Don't Worry About Cross Coupled Outs

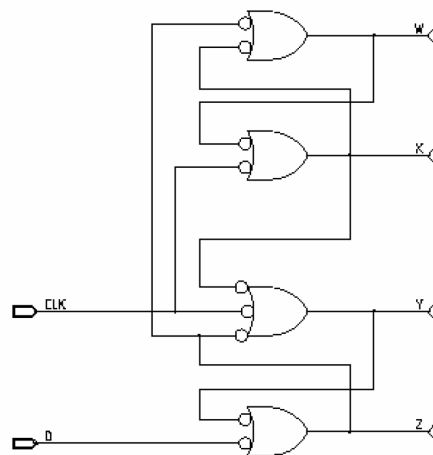


## And Generate Equations

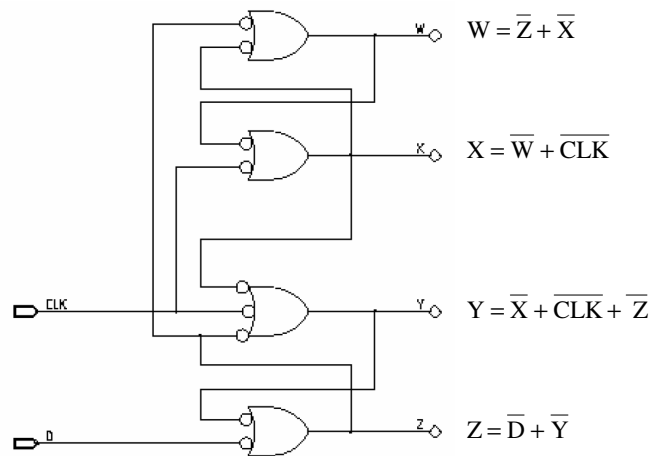


## From Equations – K-Maps

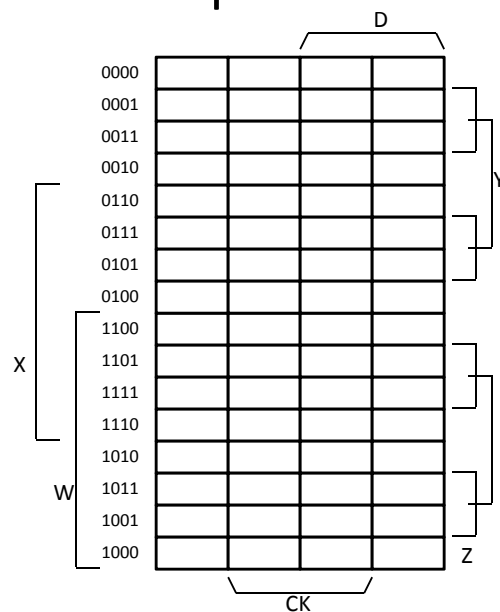

## Patterns for Logic Areas in Map

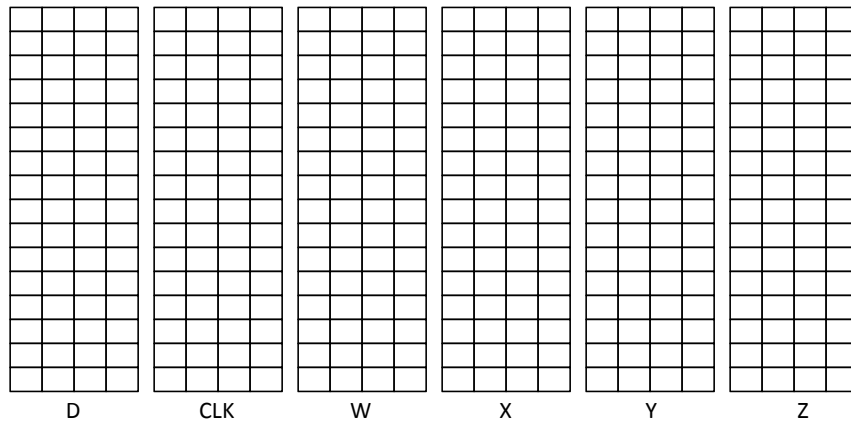

## So, Map for W

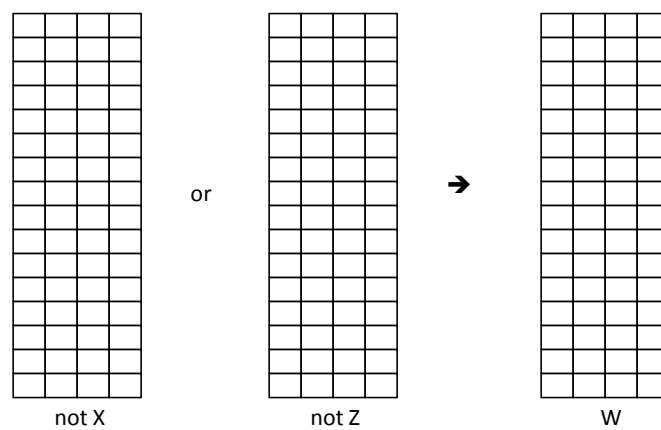


$$W = \bar{X} + \bar{Z}$$

## Put W in the Map

		D				
0000		1---	1---	1---	1---	
0001		1---	1---	1---	1---	
0011		1---	1---	1---	1---	Y
0010		1---	1---	1---	1---	
0110		1---	1---	1---	1---	
0111		0---	0---	0---	0---	
0101		0---	0---	0---	0---	
0100		1---	1---	1---	1---	
X	1100	1---	1---	1---	1---	
	1101	0---	0---	0---	0---	
	1111	0---	0---	0---	0---	Z
	1110	1---	1---	1---	1---	
	1010	1---	1---	1---	1---	
	1011	1---	1---	1---	1---	
	1001	1---	1---	1---	1---	
	1000	1---	1---	1---	1---	
		CK				

## And, Map for X

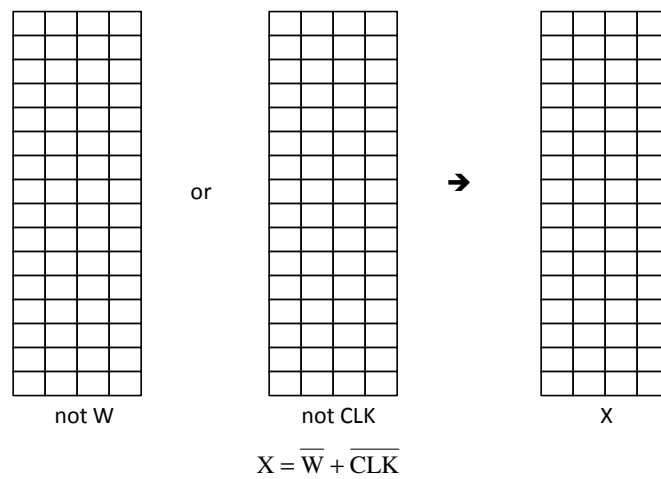


## Add X to the W Map

		D				
0000	11--	11--	11--	11--		
0001	11--	11--	11--	11--		
0011	11--	11--	11--	11--		
0010	11--	11--	11--	11--		
0110	11--	11--	11--	11--		
0111	01--	01--	01--	01--		
0101	01--	01--	01--	01--		
0100	11--	11--	11--	11--		
1100	11--	10--	10--	11--		
1101	01--	00--	00--	01--		
1111	01--	00--	00--	01--		
1110	11--	10--	10--	11--		
1010	11--	10--	10--	11--		
1011	11--	10--	10--	11--		
1001	11--	10--	10--	11--		
1000	11--	10--	10--	11--		
	CK					

X: {0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, 1101, 1111, 1110, 1010, 1011, 1001, 1000}  
 W: {0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, 1101, 1111, 1110, 1010, 1011, 1001, 1000}  
 Y: {0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, 1101, 1111, 1110, 1010, 1011, 1001, 1000}  
 Z: {0111, 0101, 1101, 1111, 1001, 1011, 1100, 1110}

## Now, Map for Y

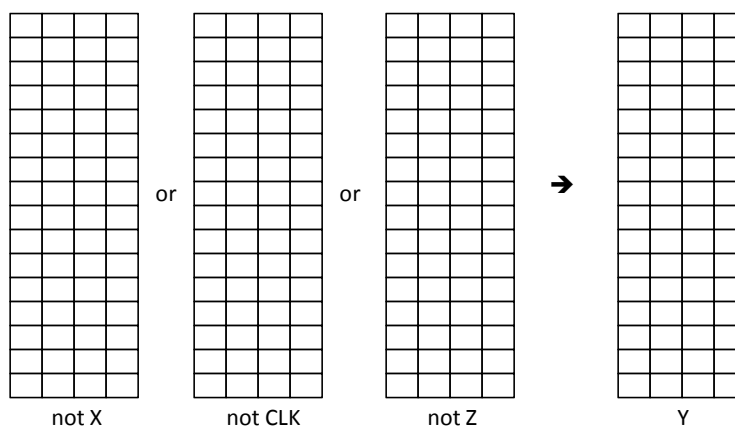


$$Y = \overline{X} + \overline{\text{CLK}} + \overline{Z}$$

## Add Y to the W,X Map

		D			
0000		111-	111-	111-	111-
0001		111-	111-	111-	111-
0011		111-	111-	111-	111-
0010		111-	111-	111-	111-
0110		111-	111-	111-	111-
0111		011-	010-	010-	011-
0101		011-	010-	010-	011-
0100		111-	111-	111-	111-
1100		111-	101-	101-	111-
1101		011-	000-	000-	011-
1111		011-	000-	000-	011-
1110		111-	101-	101-	111-
1010		111-	101-	101-	111-
1011		111-	101-	101-	111-
1001		111-	101-	101-	111-
1000		111-	101-	101-	111-
		CK			

X: {0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, 1101, 1111, 1110, 1010, 1011, 1001, 1000}  
 Y: {0000, 0001, 0011, 0010, 0110, 0111, 0101, 0100, 1100, 1101, 1111, 1110, 1010, 1011, 1001, 1000}  
 Z: {0111, 0101, 0001, 0000, 1011, 1010, 1001, 1000}

## Finally, Map for Z

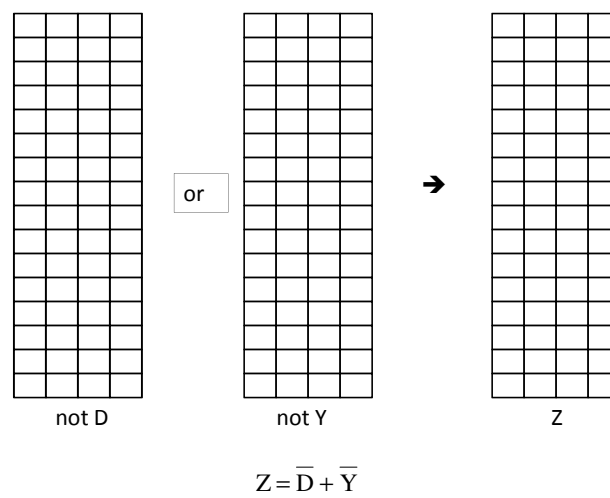



## And At Last, Add Z to the W,X,Y Map

		D			
X	W	0000	1111	1111	1111
		0001	1111	1111	1111
		0011	1111	1111	1110
		0010	1111	1111	1110
		0110	1111	1111	1110
		0111	0111	0101	0110
		0101	0111	0101	0111
		0100	1111	1111	1111
	Z	1100	1111	1011	1011
		1101	0111	0001	0001
		1111	0111	0001	0000
		1110	1111	1011	1010
		1010	1111	1011	1010
		1011	1111	1011	1010
		1001	1111	1011	1011
		1000	1111	1011	1011

CK

## Identify the Stable States

		D			
X	W	0000	1111	1111	1111
		0001	1111	1111	1111
		0011	1111	1111	1110
		0010	1111	1111	1110
		0110	1111	1111	1110
		0111	0111	0101	0110
		0101	0111	0101	0111
		0100	1111	1111	1111
	Z	1100	1111	1011	1011
		1101	0111	0001	0001
		1111	0111	0001	0000
		1110	1111	1011	1110
		1010	1111	1011	1010
		1011	1111	1011	1010
		1001	1111	1011	1011
		1000	1111	1011	1011

CK

### Situation 1: D Stays Low, CK Up, Down

	D				
0000	1111	1111	1111	1111	
0001	1111	1111	1111	1111	
0011	1111	1111	1110	1110	Y
0010	1111	1111	1110	1110	
0110	1111	1111	1110	1110	
0111	0111	0101	0100	0110	Y
0101	0111	0101	0101	0111	
0100	1111	1111	1111	1111	
1100	1111	1011	1011	1111	
1101	0111	0001	0001	0111	
1111	0111	0001	0000	0110	
1110	1111	1011	1010	1110	
1010	1111	1011	1010	1110	
1011	1111	1011	1010	1110	
1001	1111	1011	1011	1111	
1000	1111	1011	1011	1111	Z
	CK				

Diagram illustrating Situation 1: D Stays Low, CK Up, Down. The table shows data values for various X and Y coordinates. The D signal is low (0) for X=0111, 0101, 1011, and 1010. The CK signal is high (1) for X=0111, 0101, 1011, and 1010. The Z signal is high (1) for X=1000.

### Situation 2: CK Stays Low, D Up, Down

	D				
0000	1111	1111	1111	1111	
0001	1111	1111	1111	1111	
0011	1111	1111	1110	1110	Y
0010	1111	1111	1110	1110	
0110	1111	1111	1110	1110	
0111	0111	0101	0100	0110	Y
0101	0111	0101	0101	0111	
0100	1111	1111	1111	1111	
1100	1111	1011	1011	1111	
1101	0111	0001	0001	0111	
1111	0111	0001	0000	0110	
1110	1111	1011	1010	1110	
1010	1111	1011	1010	1110	
1011	1111	1011	1010	1110	
1001	1111	1011	1011	1111	
1000	1111	1011	1011	1111	Z
	CK				

Diagram illustrating Situation 2: CK Stays Low, D Up, Down. The table shows data values for various X and Y coordinates. The CK signal is low (0) for X=0111, 0101, 1011, and 1010. The D signal is high (1) for X=0111, 0101, 1011, and 1010. The Z signal is high (1) for X=1000.

### Situation 3: CK High, D Up,Down

		D				
X	W	0000	1111	1111	1111	1111
		0001	1111	1111	1111	1111
		0011	1111	1111	1110	1110
		0010	1111	1111	1110	1110
		0110	1111	1111	1110	1110
		0111	0111	0101	0100	0110
		0101	0111	0101	0101	0111
		0100	1111	1111	1111	1111
	Z	1100	1111	1011	1011	1111
		1101	0111	0001	0001	0111
		1111	0111	0001	0000	0110
		1110	1111	1011	1010	1110
		1010	1111	1011	1010	1110
		1011	1111	1011	1010	1110
		1001	1111	1011	1011	1111
		1000	1111	1011	1011	1111
		CK				

### Situation 3A: CK High, D Up,Down

		D				
X	W	0000	1111	1111	1111	1111
		0001	1111	1111	1111	1111
		0011	1111	1111	1110	1110
		0010	1111	1111	1110	1110
		0110	1111	1111	1110	1110
		0111	0111	0101	0100	0110
		0101	0111	0101	0101	0111
		0100	1111	1111	1111	1111
	Z	1100	1111	1011	1011	1111
		1101	0111	0001	0001	0111
		1111	0111	0001	0000	0110
		1110	1111	1011	1010	1110
		1010	1111	1011	1010	1110
		1011	1111	1011	1010	1110
		1001	1111	1011	1011	1111
		1000	1111	1011	1011	1111
		CK				

## Situation 4: D High, CK Up, Down

	D				
0000	1111	1111	1111	1111	
0001	1111	1111	1111	1111	
0011	1111	1111	1110	1110	Y
0010	1111	1111	1110	1110	
0110	1111	1111	1110	1110	
0111	0111	0101	0100	0110	Y
0101	0111	0101	0101	0111	
0100	1111	1111	1111	1111	
1100	1111	1011	1011	1111	
1101	0111	0001	0001	0111	Y
1111	0111	0001	0000	0110	
1110	1111	1011	1010	1110	Y
1010	1111	1011	1010	1110	
1011	1111	1011	1010	1110	Y
1001	1111	1011	1011	1111	
1000	1111	1011	1011	1111	Z
	CK				

X

W

## So – Name States, Make Diagram

	D				
0000	1111	1111	1111	1111	
0001	1111	1111	1111	1111	
0011	1111	1111	1110	1110	Y
0010	1111	1111	1110	1110	
0110	1111	1111	1110	1110	
0111	A	0101	0100	0110	Y
0101	0111	B	C	0111	
0100	1111	1111	1111	1111	
1100	1111	1011	1011	1111	
1101	0111	0001	0001	0111	Y
1111	0111	0001	0000	0110	
1110	1111	1011	1010	D	Y
1010	1111	1011	E	1110	
1011	1111	F	1010	1110	Y
1001	1111	1011	1011	1111	
1000	1111	1011	1011	1111	Z
	CK				

X

W

## State Diagram

