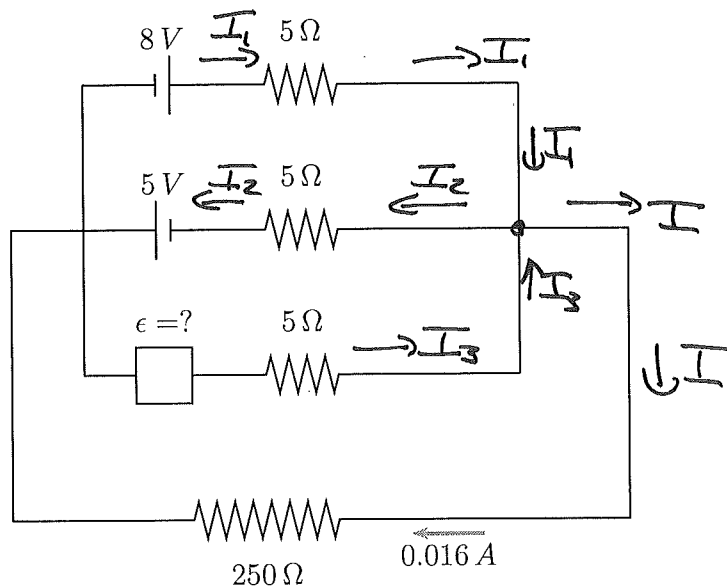


PHYSICS 161 TEST 5

Three batteries, each with internal resistance $5\ \Omega$ are connected in parallel to each other, and then to a $250\ \Omega$ resistor as shown.




- (a) If the current flowing through the $250\ \Omega$ resistor is $0.016\ A$ in the direction shown and two of the batteries have emf values of $8\ V$ and $5\ V$ (and polarities shown), what is the emf of the third battery? Which end of the third battery is at higher potential? (6pts)

GIVEN POLARITIES LABEL I_1, I_2, I_3 AS SHOWN (I_3 IS AGUESS). Let $I = .016\ A$

JUNCTION RULE $\Rightarrow I_1 + I_3 = I_2 + I \Rightarrow I_3 = I + I_2 - I_1$

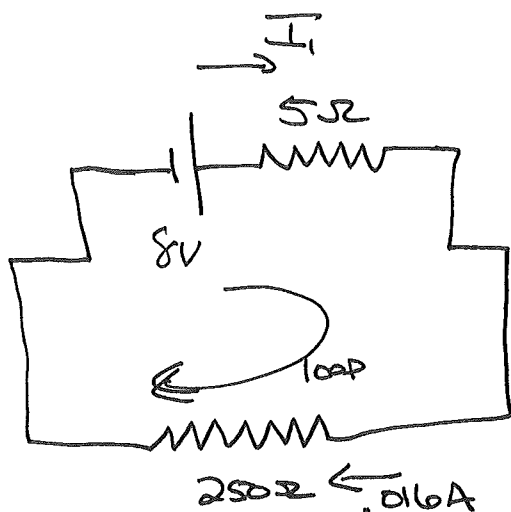
TO FIND I_1 & I_2 DO LOOPS WITH BATTERIES AND $250\ \Omega$



$$8V - I_1(5\Omega) - 0.016A(250\Omega) = 0$$

$$\Rightarrow 8V - I_1(5\Omega) - 4V = 0$$
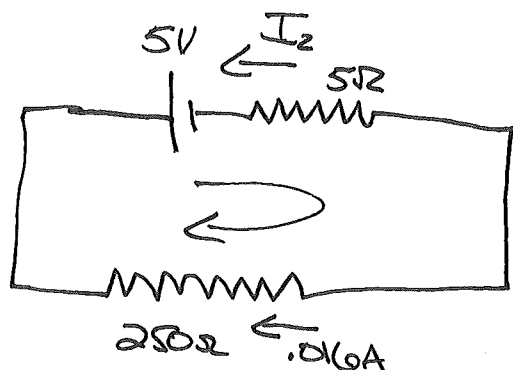
$$\Rightarrow I_1(5\Omega) = 4V \Rightarrow I_1 = 0.8A$$




$$-5V + I_2(5\Omega) - 0.016A(250\Omega) = 0$$

$$\Rightarrow -5V + I_2(5\Omega) - 4V = 0$$

$$\Rightarrow I_2(5\Omega) = 9V \Rightarrow I_2 = 1.8A$$
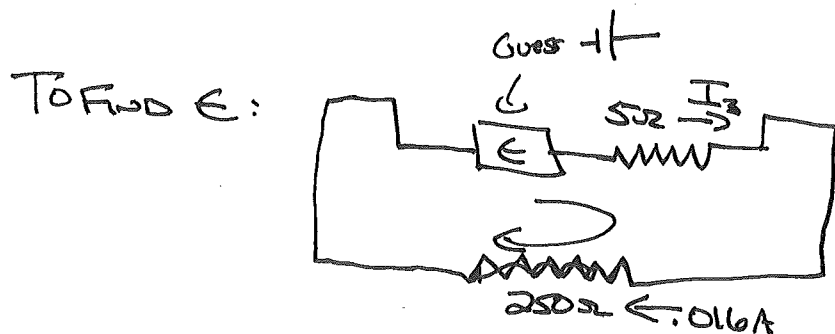
$$I_3 = I + I_2 - I_1 = 0.016A + 1.8A - 0.8A \Rightarrow I_3 = 1.016A \leftarrow \text{guessed Right}$$



$$\epsilon - I_3(5\Omega) - 250\Omega(0.016A) = 0$$


$$\Rightarrow \epsilon - 1.016A(5\Omega) - 4V = 0$$

$$\Rightarrow \epsilon = 5.08V + 4V$$

$$\Rightarrow \boxed{\epsilon = 9.08V}$$

GUESSED CORRECTLY, LEFT SIDE
IS AT LOWER POTENTIAL

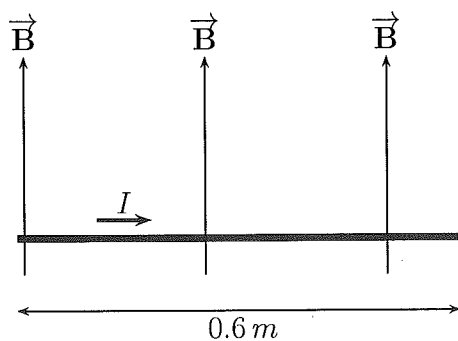- (b) The 0.6 m -long straight wire shown below has 3 A of current flowing through it. If there is an upward-pointing, uniform magnetic field of magnitude 0.6 T . What is the magnitude and direction of the force acting on the wire? (4pts)



STRAIGHT WIRE

$$\Rightarrow \vec{F} = I \vec{L} \times \vec{B}$$

$$\vec{L} = .6\text{ m}, \rightarrow$$

$$\vec{B} = 0.6\text{ T}, \uparrow$$

$$\text{RHR} \Rightarrow \vec{L} \times \vec{B} = LB \sin 90^\circ, \odot$$

$$\Rightarrow \vec{F} = ILB, \odot = (3\text{ A})(.6\text{ m})(.6\text{ T}), \odot$$

$$\Rightarrow \boxed{\vec{F} = 1.08\text{ N}, \odot}$$