

Homework 8 Solutions

Solution 6.71


a.

$$I_{EQ} = \frac{20 - 0.7}{10} = 1.93 \text{ mA}$$

$$I_{CQ} = 1.91 \text{ mA}$$

$$\begin{aligned} V_{ECQ} &= V_{CC} + V_{EB}(\text{on}) - I_C R_C \\ &= 25 + 0.7 - (1.91)(6.5) \Rightarrow \underline{V_{ECQ} = 13.3 \text{ V}} \end{aligned}$$

b.

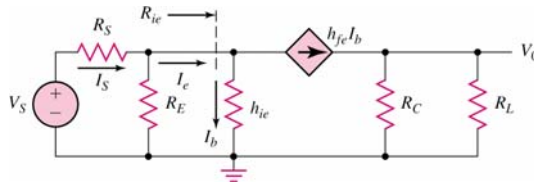

Neglect effect h_{oe}

Assume

$$2.45 \leq h_{ie} \leq 3.7 \text{ k}\Omega$$

$$80 \leq h_{fe} \leq 120$$

$$V_o = (h_{fe} I_b) (R_C \parallel R_L)$$

$$R_{ie} = \frac{h_{ie}}{1 + h_{fe}}, \quad I_e = \left(\frac{R_E}{R_E + R_{ie}} \right) \cdot I_s$$

$$I_b = \left(\frac{I_e}{1 + h_{fe}} \right), \quad I_s = \frac{V_s}{R_S + (R_E \parallel R_{ie})}$$

$$A_v = \left(\frac{h_{fe}}{1 + h_{fe}} \right) (R_C \parallel R_L) \left(\frac{R_E}{R_E + R_{ie}} \right) \left(\frac{1}{R_S + R_E \parallel R_{ie}} \right)$$

High gain device: $h_{ie} = 3.7 \text{ k}\Omega$, $h_{fe} = 120$

$$R_{ie} = \frac{3.7}{121} = 0.0306 \text{ k}\Omega$$

$$R_E \parallel R_{ie} = 10 \parallel 0.0306 = 0.0305 \text{ k}\Omega$$

$$A_v = \left(\frac{120}{121} \right) (6.5 \parallel 5) \left(\frac{10}{10 + 0.0306} \right) \left(\frac{1}{1 + 0.0305} \right) \Rightarrow A_v = 2.711$$

Low gain device: $h_{ie} = 2.45 \text{ k}\Omega$, $h_{fe} = 80$

$$R_{ie} = \frac{2.45}{81} = 0.03025 \text{ k}\Omega$$

$$R_E \parallel R_{ie} = 10 \parallel 0.03025 = 0.0302 \text{ k}\Omega$$

$$A_v = \left(\frac{80}{81} \right) (6.5 \parallel 5) \left(\frac{10}{10 + 0.03025} \right) \left(\frac{1}{1 + 0.0302} \right) \Rightarrow A_v = 2.70$$

$$\underline{2.70 \leq A_v \leq 2.71} \quad \text{So } A_v \cong \text{constant}$$

c.

$$R_i = R_E \parallel R_{ie}$$

We found $\underline{0.0302 \leq R_i \leq 0.0305 \text{ k}\Omega}$

Neglecting h_{oe} , $\underline{R_o = R_C = 6.5 \text{ k}\Omega}$

Solution 6.73

$$(a) \quad g_{m1} = g_{m2} = \frac{1}{0.026} = 38.46 \text{ mA/V}$$

$$r_{\pi 1} = \frac{(120)(0.026)}{1} = 3.12 \text{ k}\Omega, \quad r_{\pi 2} = \frac{(80)(0.026)}{1} = 2.08 \text{ k}\Omega$$

$$A_{v1} = \frac{V_{o1}}{V_i} = \frac{(1 + \beta_1) \left(R_E \parallel \frac{r_{\pi 2}}{1 + \beta_2} \right)}{r_{\pi 1} + (1 + \beta_1) \left(R_E \parallel \frac{r_{\pi 2}}{1 + \beta_2} \right)}$$

$$\text{We find } R_E \parallel \frac{r_{\pi 2}}{1 + \beta_2} = 1 \parallel \frac{2.08}{81} = 0.02504 \text{ k}\Omega$$

$$\text{Then } A_{v1} = \frac{(121)(0.02504)}{3.12 + (121)(0.02504)} = 0.4927$$

$$(b) \quad A_{v2} = \frac{V_{o2}}{V_{o1}} = g_{m2} R_C = (38.46)(4) = 153.8$$

$$(c) \quad A_v = A_{v1} \cdot A_{v2} = (0.4927)(153.8) = 75.8$$


Solution 6.77

$$(a) \quad I_{R2} = \frac{5 - 2(0.7)}{0.050} = 72 \text{ mA}, \quad I_{R1} = \frac{0.7}{0.5} = 1.4 \text{ mA}$$

$$I_{E2} = 72 - 1.4 = 70.6 \text{ mA}, \quad I_{C2} = \left(\frac{80}{81}\right)(70.6) = 69.73 \text{ mA}, \quad I_{B2} = \frac{70.6}{81} = 0.8716 \text{ mA}$$

$$I_{E1} = 1.4 + 0.8716 = 2.2716 \text{ mA}, \quad I_{C1} = \left(\frac{120}{121}\right)(2.2716) = 2.253 \text{ mA}$$

(b)

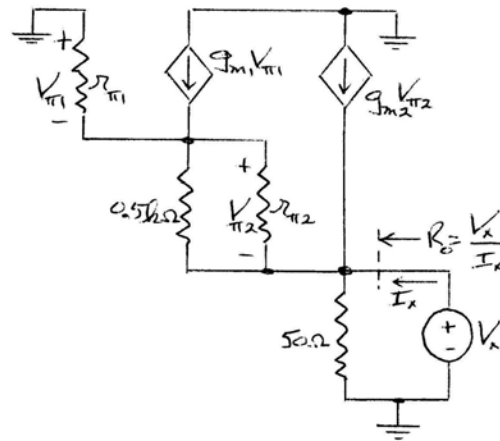

$$g_{m1} = \frac{2.253}{0.026} = 86.65 \text{ mA/V}, \quad g_{m2} = \frac{69.73}{0.026} = 2681.9 \text{ mA/V}$$

$$r_{\pi1} = \frac{(120)(0.026)}{2.253} = 1.385 \text{ k}\Omega, \quad r_{\pi2} = \frac{(80)(0.026)}{69.73} = 0.02983 \text{ k}\Omega$$

$$V_s = V_{\pi1} + V_{\pi2} + V_o$$

$$V_o = \left[\left(\frac{V_{\pi1}}{r_{\pi1}} + g_{m1} V_{\pi1} \right) + g_{m2} V_{\pi2} \right] (0.05)$$

$$V_{\pi2} = \left(\frac{V_{\pi1}}{r_{\pi1}} + g_{m1} V_{\pi1} \right) (0.5 \parallel r_{\pi2}) = V_{\pi1} \left(\frac{1}{1.385} + 86.65 \right) (0.5 \parallel 0.02983) = V_{\pi1} (2.4595)$$

$$V_o = \left[V_{\pi1} \left(\frac{1}{1.385} + 86.65 \right) + (2681.9) V_{\pi1} (2.4595) \right] (0.05) = V_{\pi1} (334.175)$$

$$V_s = V_{\pi1} + V_{\pi2} + V_o = V_{\pi1} + V_{\pi1} (2.4595) + V_o$$

$$\text{So } V_{\pi1} = (V_s - V_o) (0.28906)$$

$$\text{And } V_o = (334.175) (V_s - V_o) (0.28906) = 96.596 (V_s - V_o)$$

$$A_v = \frac{V_o}{V_s} = 0.990$$


(c) For R_{ib} :

We have $V_o = (0.989754)V_s$

$$V_{\pi 1} = (V_s - V_o)(0.28906) = V_s(1 - 0.98975)(0.28906) = V_s(0.0029618)$$

$$R_{ib} = \frac{V_s}{I_s} = \frac{V_s}{\left(\frac{V_{\pi 1}}{r_{\pi 1}}\right)} = \frac{r_{\pi 1}}{0.0029618} \Rightarrow R_{ib} = 467.6 \text{ k}\Omega$$

For R_o :

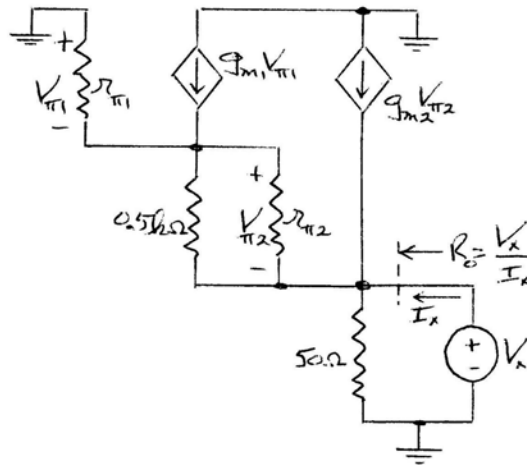

$$(1) V_{\pi 1} + V_{\pi 2} + V_x = 0$$

$$(2) I_x + g_{m2}V_{\pi 2} + \left(\frac{V_{\pi 1}}{r_{\pi 1}} + g_{m1}V_{\pi 1}\right) = \frac{V_x}{0.05}$$

We had $V_{\pi 2} = V_{\pi 1}(2.4595)$

$$(1) V_{\pi 1} + V_{\pi 1}(2.4595) + V_x = 0 \Rightarrow V_{\pi 1} = -V_x(0.28906)$$

$$(2) I_x + g_{m2}V_{\pi 1}(2.4595) + V_{\pi 1}\left(\frac{1}{r_{\pi 1}} + g_{m1}\right) = \frac{V_x}{0.05}$$

$$I_x + V_{\pi 1}\left[(2681.9)(2.4595) + \left(\frac{1}{1.385} + 86.65\right)\right] = \frac{V_x}{0.05}$$

$$I_x - V_x(0.28906)[6683.5] = \frac{V_x}{0.05}$$

$$R_o = \frac{V_x}{I_x} = 0.512 \Omega$$

Problem 7.5

Consider the circuit shown in Figure P7.5. (a) What is the value of the voltage transfer function V_o/V_i at very low frequencies? (b) Determine the voltage transfer function at very high frequencies. (c) Derive the expression for the voltage transfer function $T(s) = V_o(s)/V_i(s)$. Put the expression in the form $T(s) = K(1 + s\tau_A)/(1 + s\tau_B)$. What are the values of K , τ_A , and τ_B ?

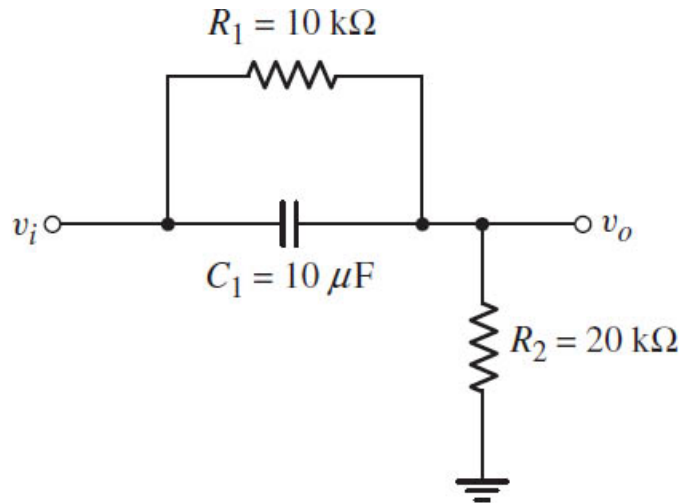


Figure P7.5

Problem 7.7

A voltage transfer function is given by $T(f) = 1/(1 + jf/f_T)^3$. (a) Show that the actual response at $f = f_T$ is approximately 9 dB below the maximum value. What is the phase angle at this frequency? (b) What is the slope of the magnitude plot for $f \gg f_T$? What is the phase angle in this frequency range?