

Lecture 40 (Transformers)




Physics 161-01 Spring 2012

Douglas Fields

CPS 40-1

In an L - R - C series circuit as shown, the current has a very small amplitude if the ac source oscillates at a very high frequency. Which circuit element causes this behavior?

(a) L - R - C series circuit

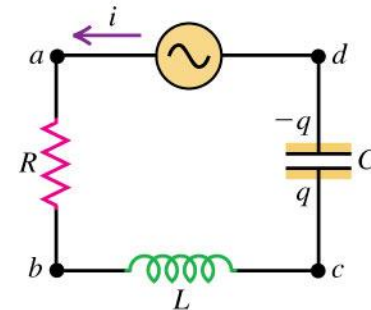


© 2012 Pearson Education, Inc.

- A. the resistor R
- B. the inductor L
- C. the capacitor C
- D. Misleading question—the current actually has a very *large* amplitude if the frequency is very high

CPS 40-1

In an L - R - C series circuit as shown, the current has a very small amplitude if the ac source oscillates at a very high frequency. Which circuit element causes this behavior?

(a) L - R - C series circuit

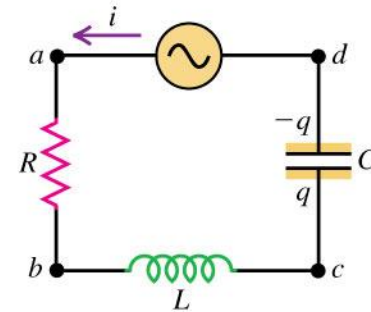


© 2012 Pearson Education, Inc.

- ✓ A. the resistor R
- B. the inductor L
- C. the capacitor C
- D. Misleading question—the current actually has a very *large* amplitude if the frequency is very high

CPS 40-2

In an L - R - C series circuit as shown, there is a phase angle between the instantaneous current through the circuit and the instantaneous voltage v_{ad} across the entire circuit. For what value of the phase angle is the *greatest power* delivered to the resistor?

(a) L - R - C series circuit

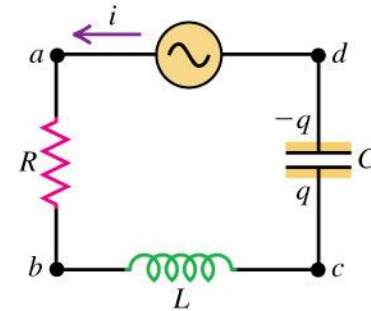


© 2012 Pearson Education, Inc.

- A. zero
- B. 90°
- C. 180°
- D. 270°
- E. none of the above

CPS 40-2

In an L - R - C series circuit as shown, there is a phase angle between the instantaneous current through the circuit and the instantaneous voltage v_{ad} across the entire circuit. For what value of the phase angle is the *greatest power* delivered to the resistor?

(a) L - R - C series circuit

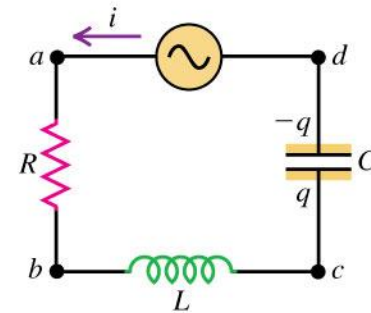

© 2012 Pearson Education, Inc.



A. zero

B. 90°

C. 180°


D. 270°

E. none of the above

CPS 40-3

In an L - R - C series circuit as shown, suppose that the angular frequency of the ac source equals the resonance angular frequency. In this case, the circuit impedance

(a) L - R - C series circuit

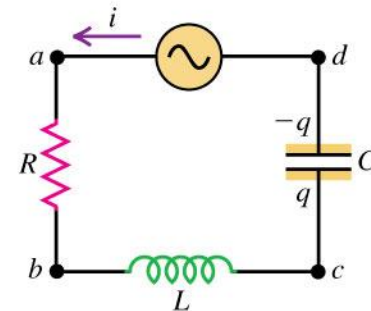


© 2012 Pearson Education, Inc.

- A. is maximum.
- B. is minimum, but not zero.
- C. is zero.
- D. is neither a maximum nor a minimum.
- E. not enough information give to decide

CPS 40-3

In an L - R - C series circuit as shown, suppose that the angular frequency of the ac source equals the resonance angular frequency. In this case, the circuit impedance

(a) L - R - C series circuit

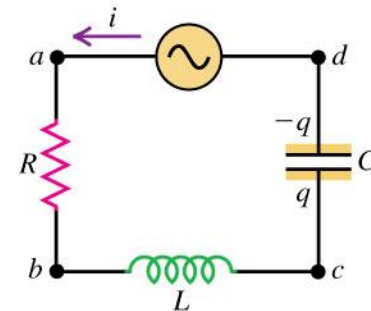

© 2012 Pearson Education, Inc.

- ✓ A. is maximum.
- B. is minimum, but not zero.
- C. is zero.
- D. is neither a maximum nor a minimum.
- E. not enough information give to decide

Transformers

- For long-distance transmission, it is important to have high voltages and low currents to reduce i^2R losses in the lines.
- But, you don't want 500,000V in your household appliances, right?
- Because we use alternating EMFs, it is relatively simple to transform a high potential to a lower one (or vice versa).



Transformers


- A typical transformer is just two coils wrapped around a common core.
- If one assumes that all of the magnetic field stays inside the core, then the same magnetic flux passes through each coil.
- Then, using Faraday's law:

$$\mathcal{E}_1 = -N_1 \frac{d\Phi_B}{dt}$$

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_B}{dt}$$

The induced emf *per turn* is the same in both coils, so we adjust the ratio of terminal voltages by adjusting the ratio of turns:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

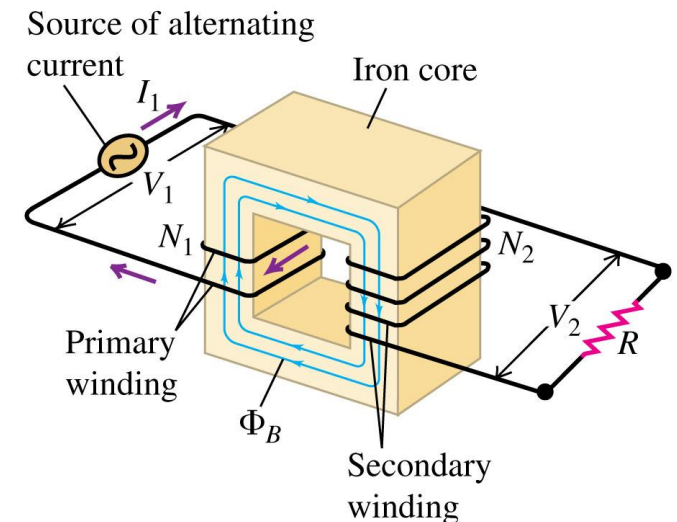

© 2012 Pearson Education, Inc.

Transformers

- Since the flux (and how it changes) is the same through both coils, then you can divide these two equations to get:

$$\mathcal{E}_1 = -N_1 \frac{d\Phi_B}{dt}$$

÷


$$\mathcal{E}_2 = -N_2 \frac{d\Phi_B}{dt}$$

$$\frac{\mathcal{E}_1}{\mathcal{E}_2} = \frac{N_1}{N_2} \Rightarrow$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

The induced emf *per turn* is the same in both coils, so we adjust the ratio of terminal voltages by adjusting the ratio of turns:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

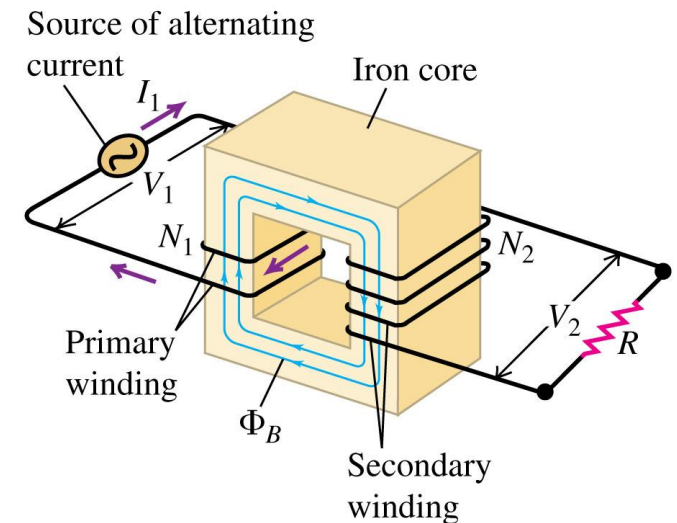

© 2012 Pearson Education, Inc.

Transformers


- So, the potential at the secondary coil can be stepped down, or up, depending on the ratio of the number of coils:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \Rightarrow$$

$$V_2 = \frac{N_2}{N_1} V_1$$

The induced emf *per turn* is the same in both coils, so we adjust the ratio of terminal voltages by adjusting the ratio of turns:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

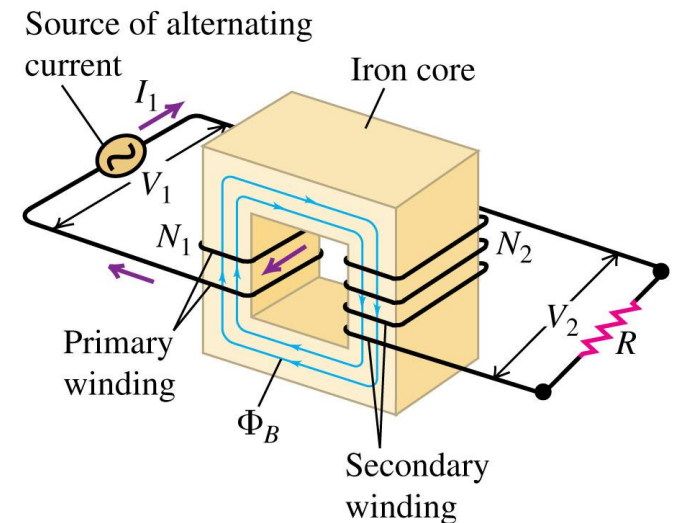

Power (Energy) Conservation

- Assuming for a moment that there is no energy lost in the transformer, then the power input to the transformer must be equal to the power output of the transformer:

$$V_1 I_1 = V_2 I_2$$



Transformers


- When the voltage is stepped up, the current is stepped down, and vice versa.

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \Rightarrow$$

$$V_2 = \frac{N_2}{N_1} V_1$$

$$V_1 I_1 = V_2 I_2 \Rightarrow$$


$$\frac{V_1}{V_2} = \frac{I_2}{I_1}$$

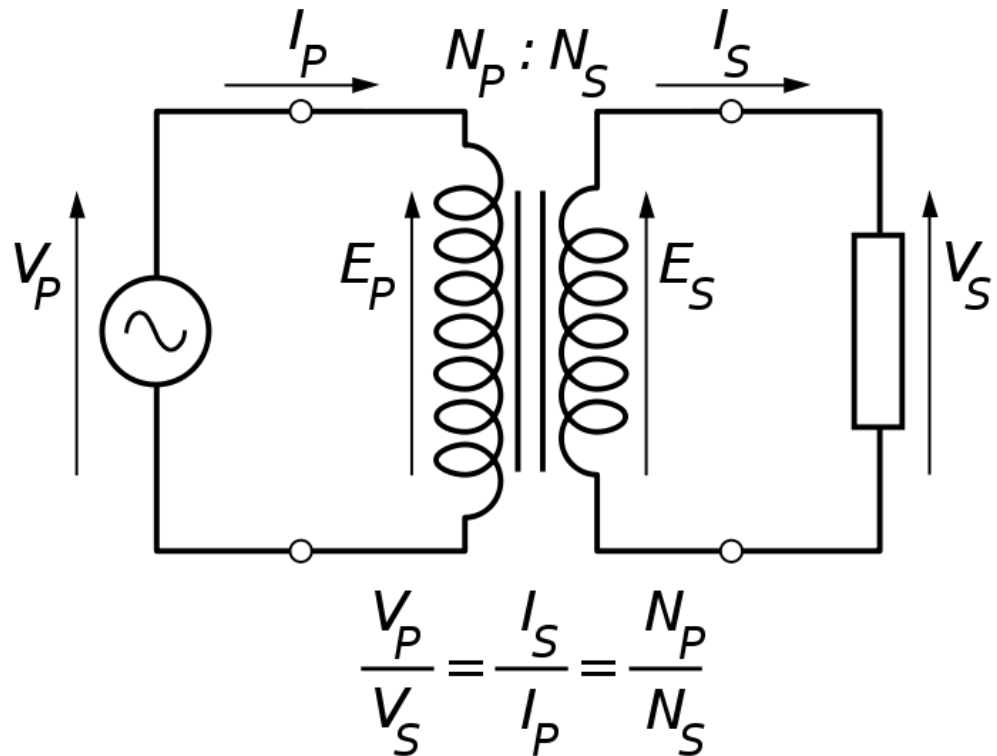


Reducing Eddy Currents

- In the real transformer, energy can be lost through heating the core, from eddy currents.
- In order to lose less energy in the transformer, we can segment the core to reduce the eddy currents, and hence the i^2R losses.


(a) Schematic transformer

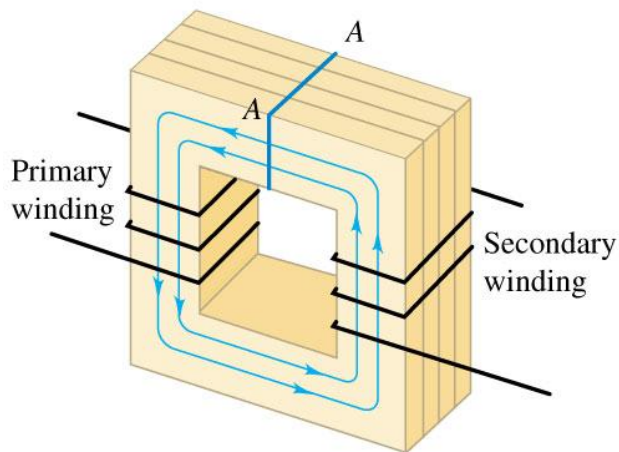

(b) Large eddy currents in solid core

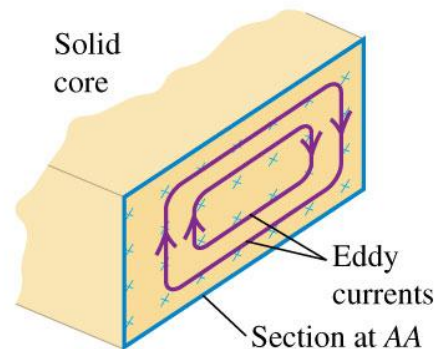


(c) Smaller eddy currents in laminated core

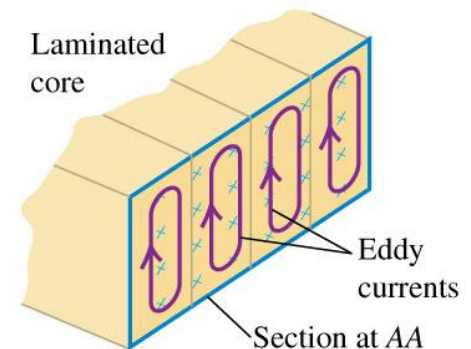

CPS 40-4

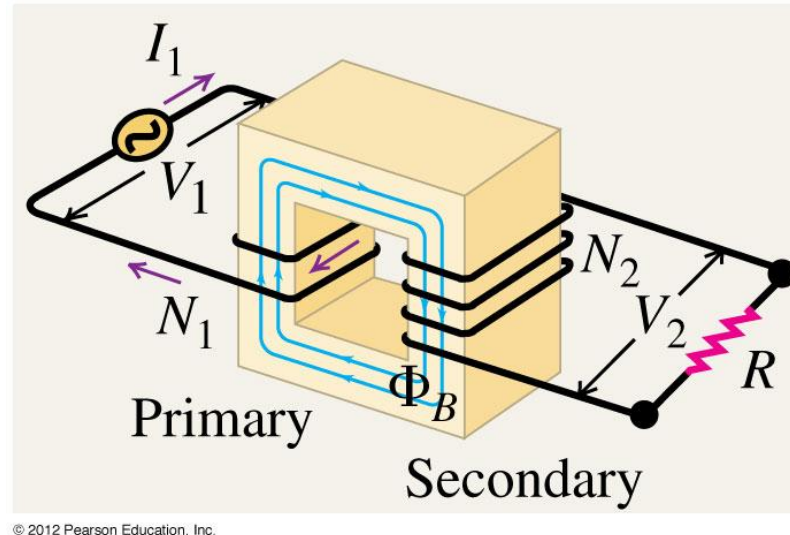
In the transformer shown in the drawing, there are more turns in the secondary than in the primary. In this situation, the *voltage amplitude* is



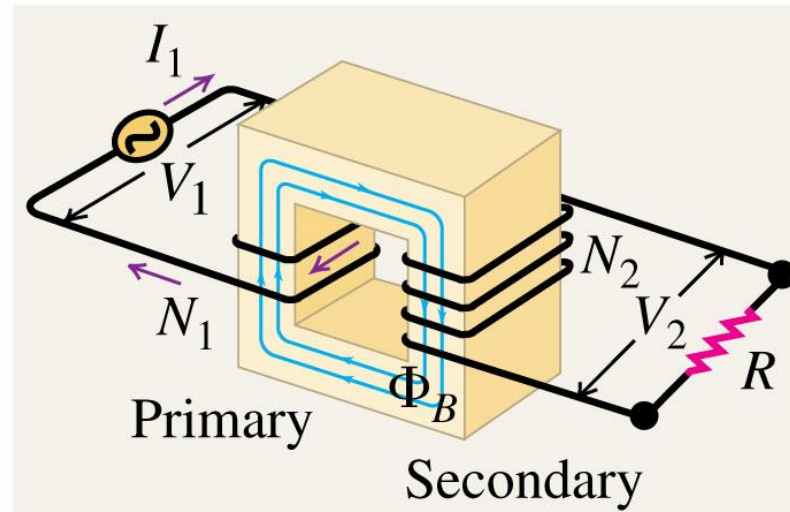- A. greater in the primary than in the secondary.
- B. smaller in the primary than in the secondary.
- C. the same in the primary and in the secondary.
- D. not enough information given to decide

CPS 40-4


In the transformer shown in the drawing, there are more turns in the secondary than in the primary. In this situation, the *voltage amplitude* is



- ✓ A. greater in the primary than in the secondary.
- B. smaller in the primary than in the secondary.
- C. the same in the primary and in the secondary.
- D. not enough information given to decide

CPS 40-5

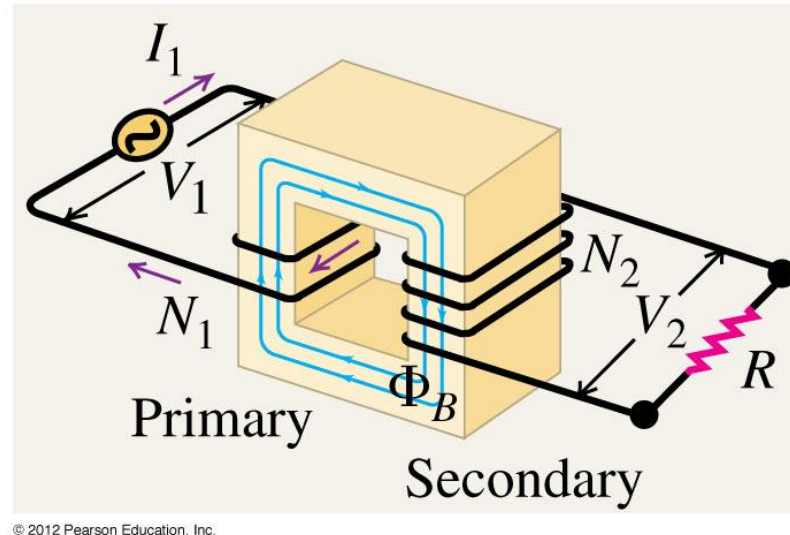
In the transformer shown in the drawing, there are more turns in the secondary than in the primary. In this situation, the *current amplitude* is



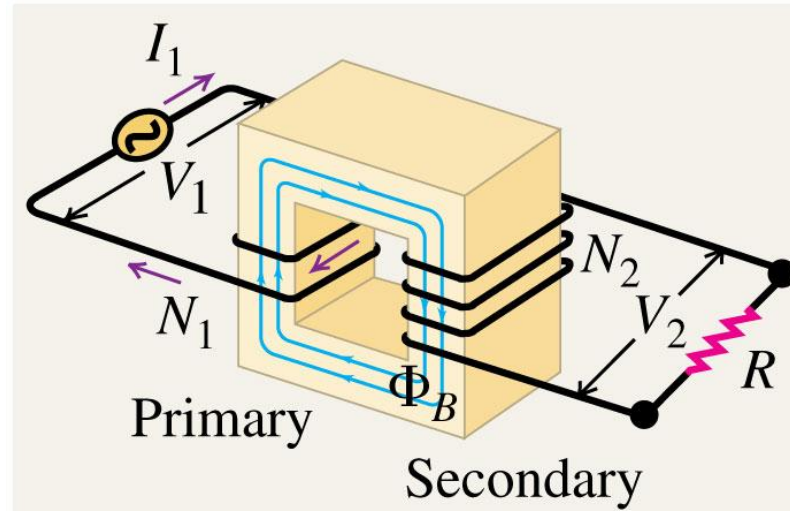- A. greater in the primary than in the secondary.
- B. smaller in the primary than in the secondary.
- C. the same in the primary and in the secondary.
- D. not enough information given to decide

CPS 40-5

In the transformer shown in the drawing, there are more turns in the secondary than in the primary. In this situation, the *current amplitude* is



© 2012 Pearson Education, Inc.



- A. greater in the primary than in the secondary.
- B. smaller in the primary than in the secondary.
- C. the same in the primary and in the secondary.
- D. not enough information given to decide